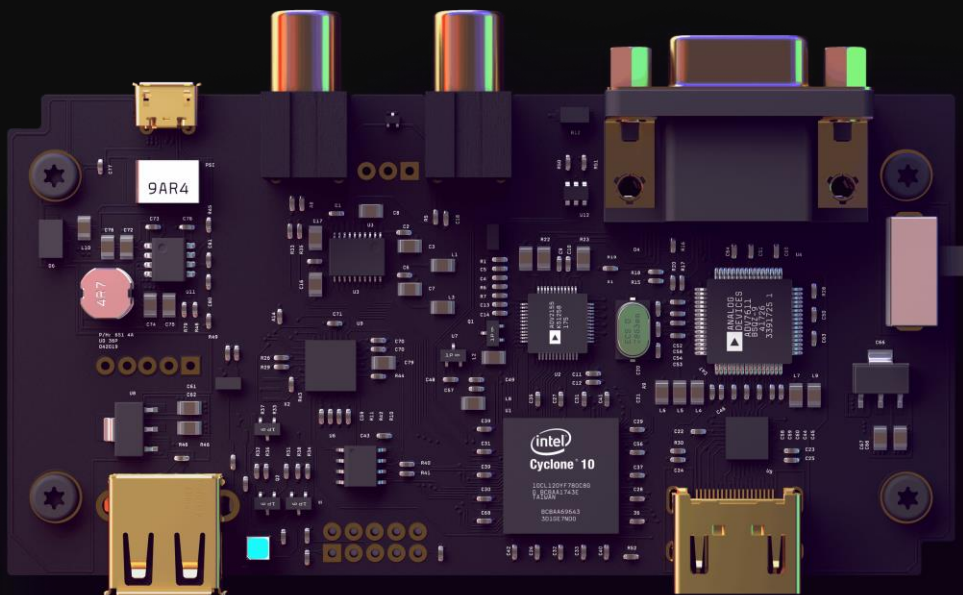


EC205

Analog Electronics Lab

Lab – 10



Utkarsh R Mahajan 201EC164


Sannan Ali 201EC159

Experiment 9: Study of Comparator and Schmitt Triggers


Aim: To design and study a $\mu A741$ based Comparator, Inverting Schmitt trigger and non-inverting Schmitt trigger circuits.

1. Test the comparator for $V_{in} = 5 \sin(200\pi t)$ and $V_{ref} = 0 \text{ V}$, 2 V and -3 V . (In hardware lab: Observe the transfer characteristic of the circuit by setting the DSO in X-Y mode.)


Circuit Diagram:

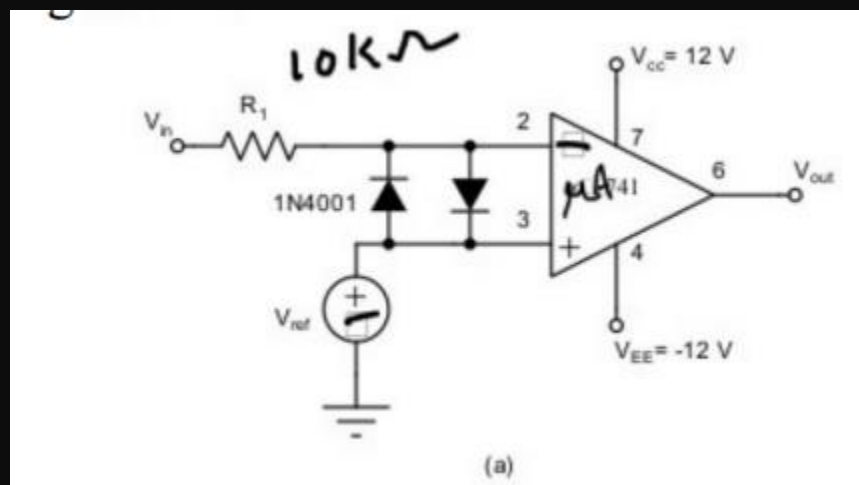

Circuit in LTspice:

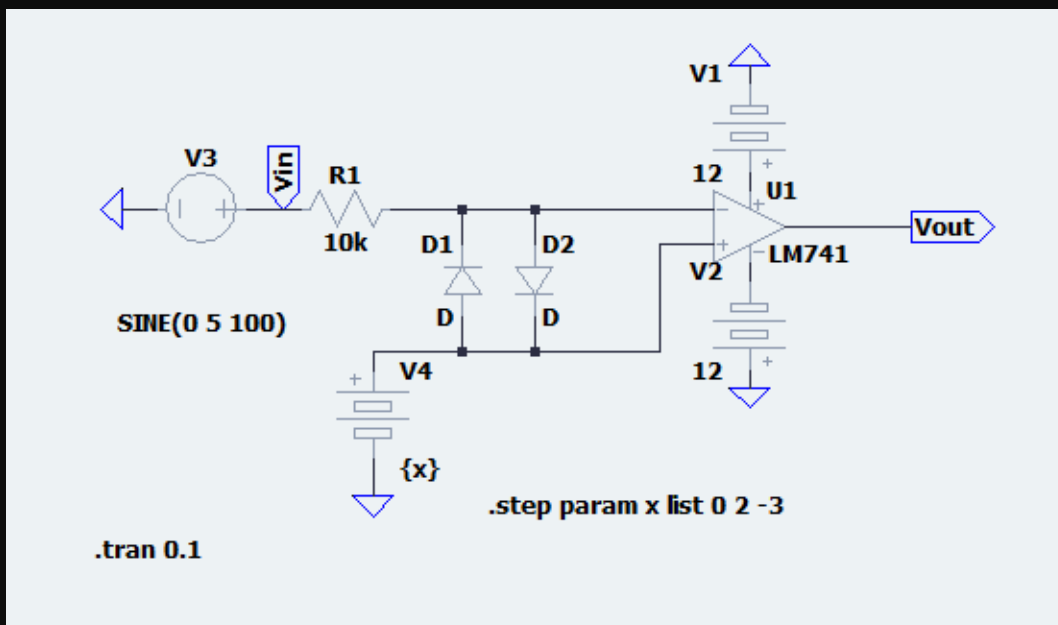


Waveform:

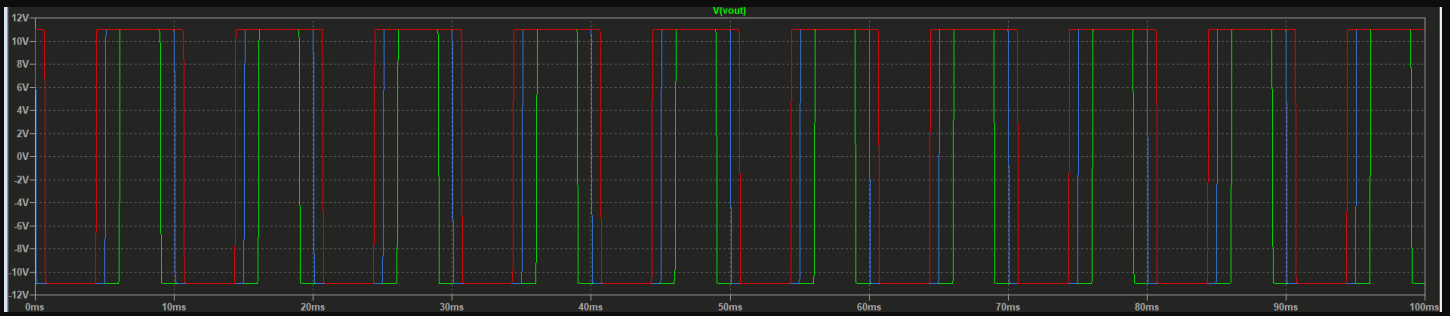


Only for $V_{ref}=0v$:

Circuit in LTspice:

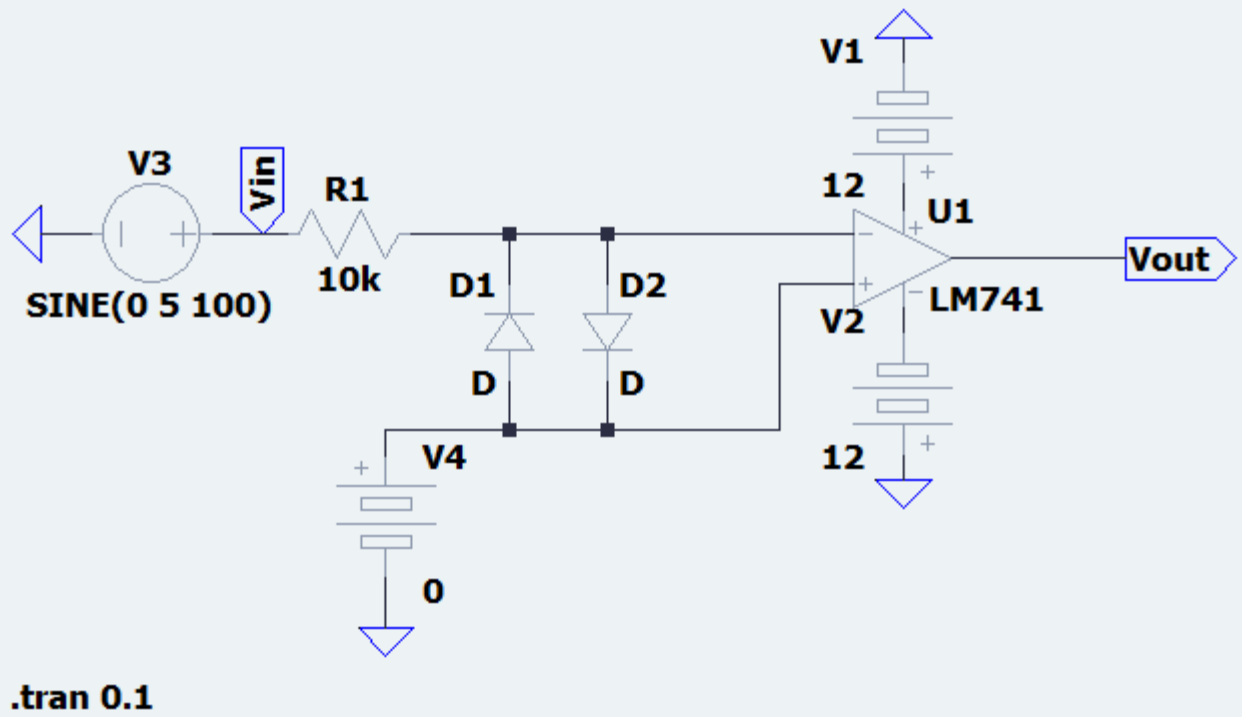


Waveform:

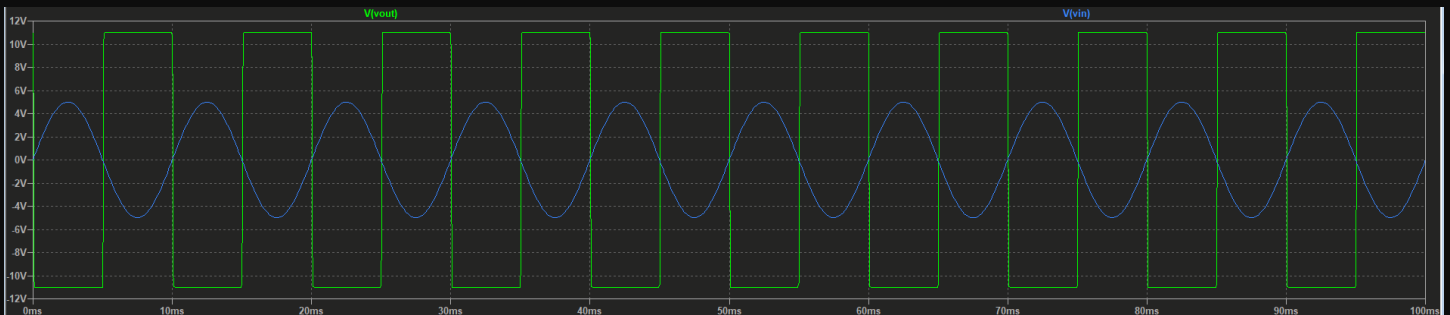


Only for $V_{ref}=2v$:

Circuit in LTspice:

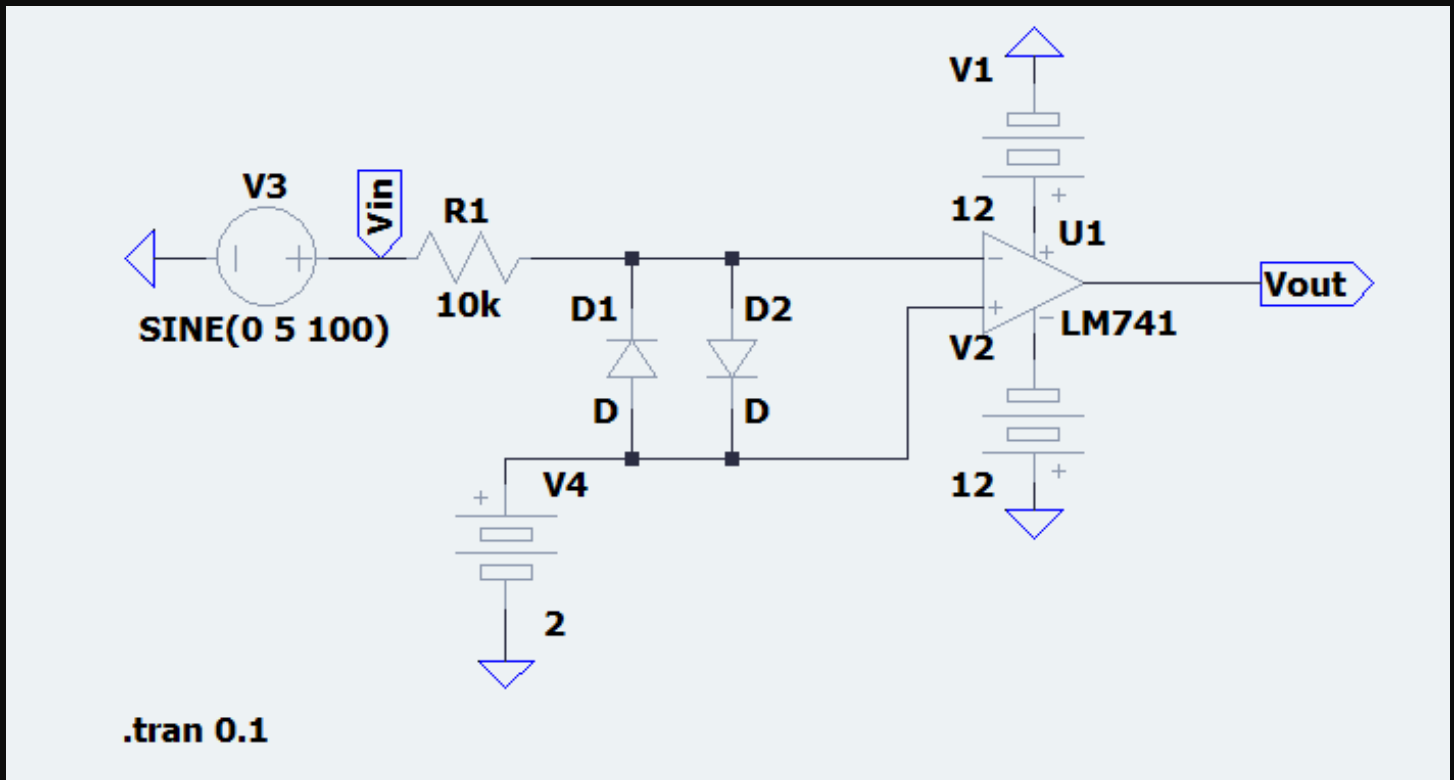


Waveform:

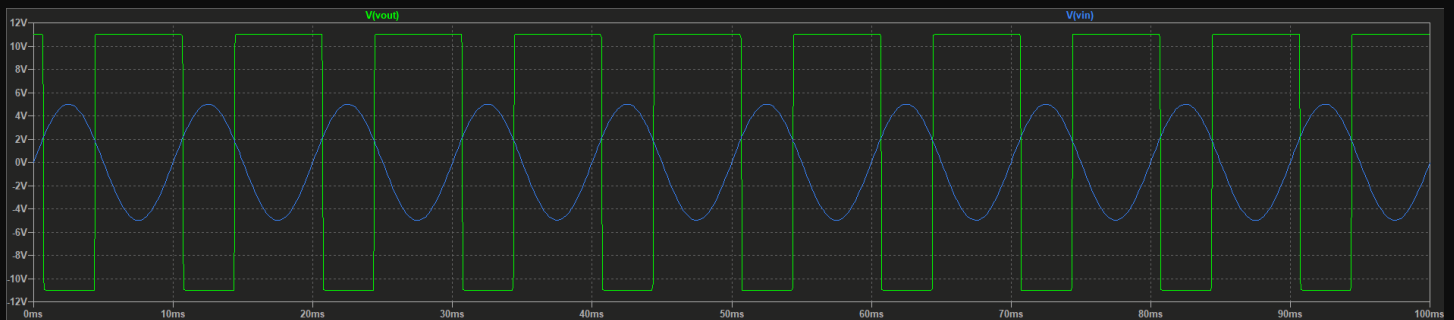

Only for $V_{ref}=-3v$:

Circuit in LTspice:

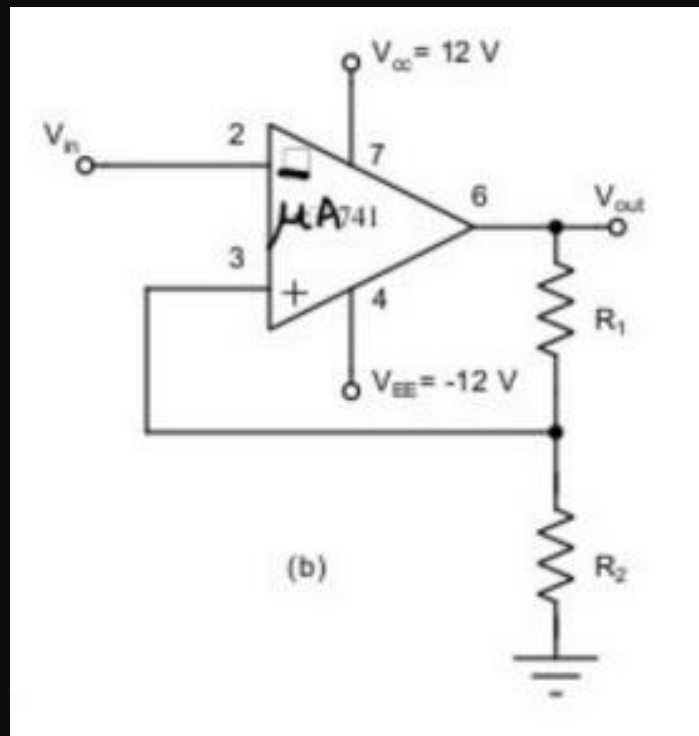

Considering $V_{cc} = 13V$.

Given $V_{sat} = V_{cc} - 1$,

Knowing that for inverting Schmitt trigger,

$$V_{UT} = \frac{R_2}{R_2 + R_1} V_{sat}$$


$$V_{LT} = \frac{R_2}{R_2 + R_1} (-V_{sat})$$

Considering $R_2 = 1k\Omega$


Matching the above conditions,

we get $R_1 = 3k\Omega$

Circuit in LTspice:

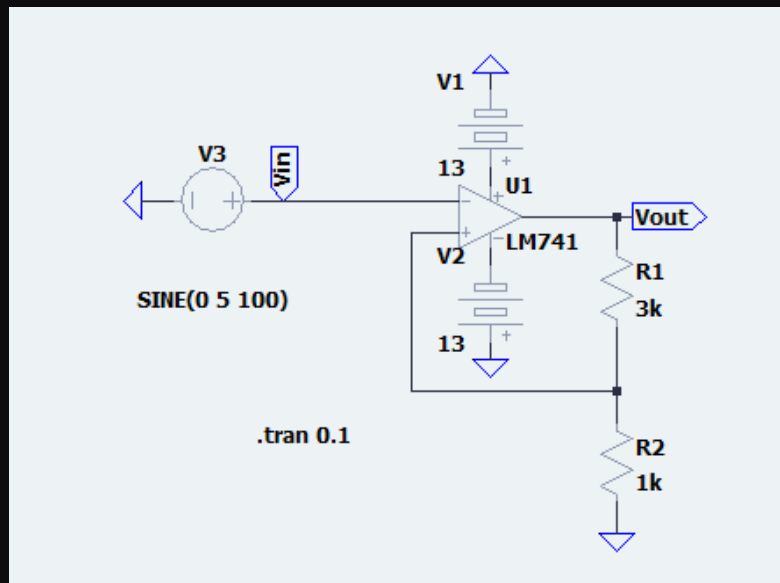


Waveform:

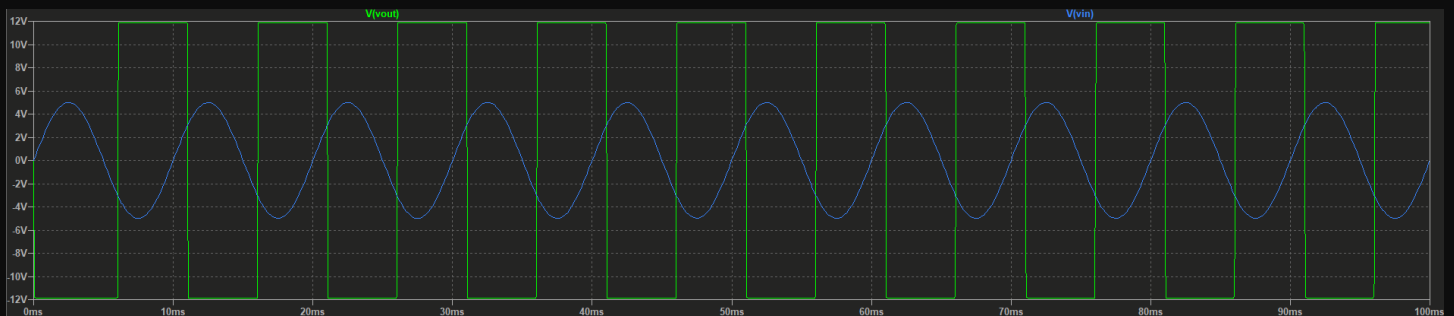


If we take 2V as input, the output will be low since it never the input voltage never crosses the required trigger voltage.

Circuit in LTspice:

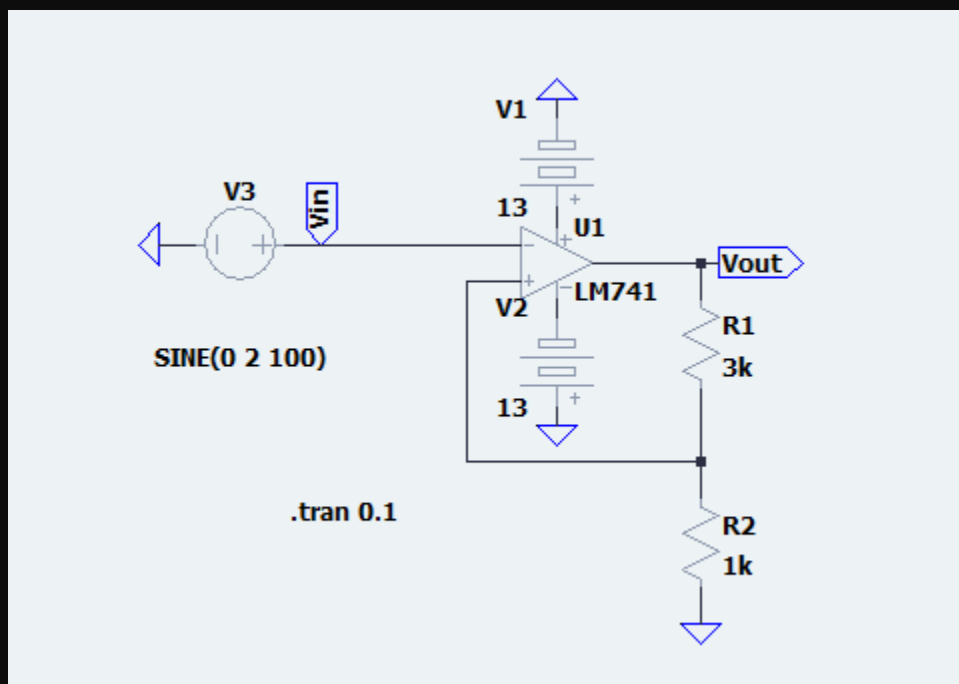

Waveform:

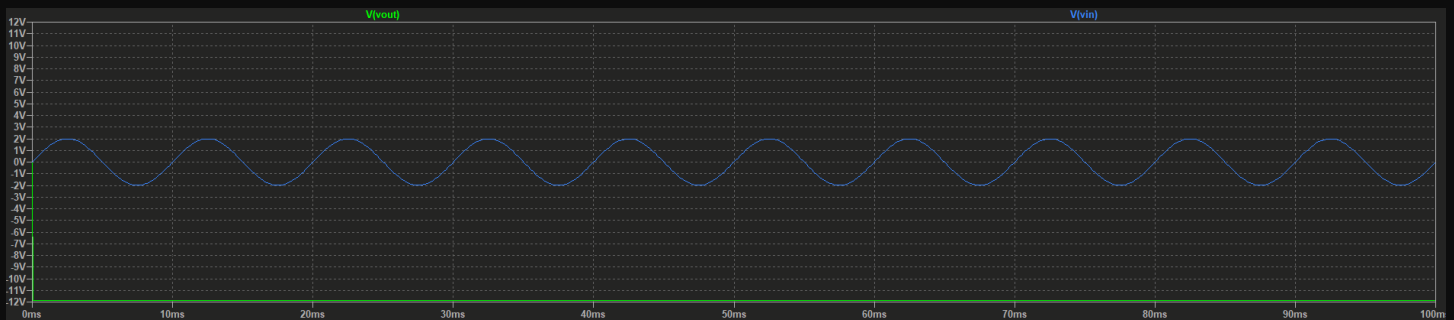


We can see that the waveform is as expected.

3. Design the non-inverting Schmitt trigger circuit for $V_{LT} = -4\text{ V}$ and $V_{UT} = 4\text{ V}$. Assume the saturation voltage, $V_{sat} = V_{cc} - 1\text{ V}$. Observe the input and output waveforms. (In hardware lab: Observe the transfer characteristic of the circuit by setting the DSO in X-Y mode.)

->

Circuit Diagram:

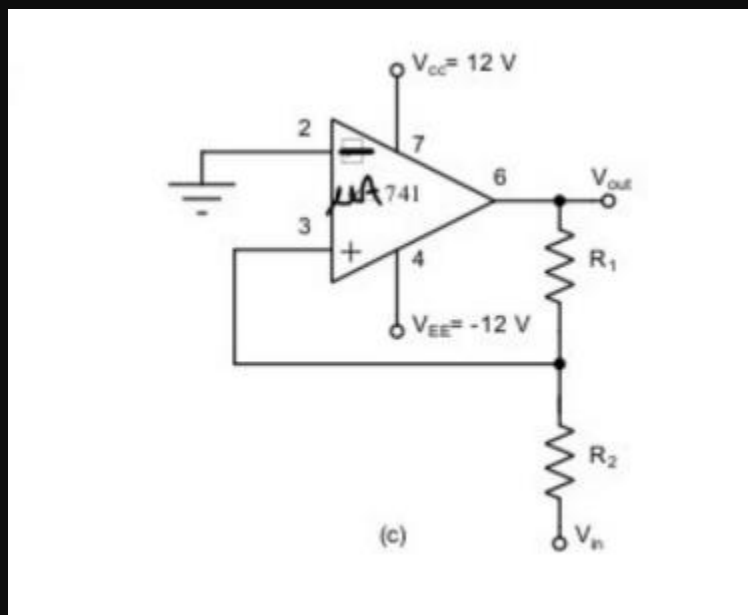

Considering $V_{cc} = 13\text{ V}$.

Given $V_{sat} = V_{cc} - 1$,

Knowing that for inverting Schmitt trigger,

$$V_{UT} = \frac{R_2}{R_1} V_{sat} = 4\text{ V}$$

$$V_{LT} = \frac{R_2}{R_1}(-V_{sat}) = -4V$$


Considering $R_2 = 1k\Omega$

Matching the above conditions,


we get $R_1 = 3k\Omega$

For 5V amplitude:

Circuit in LTspice:

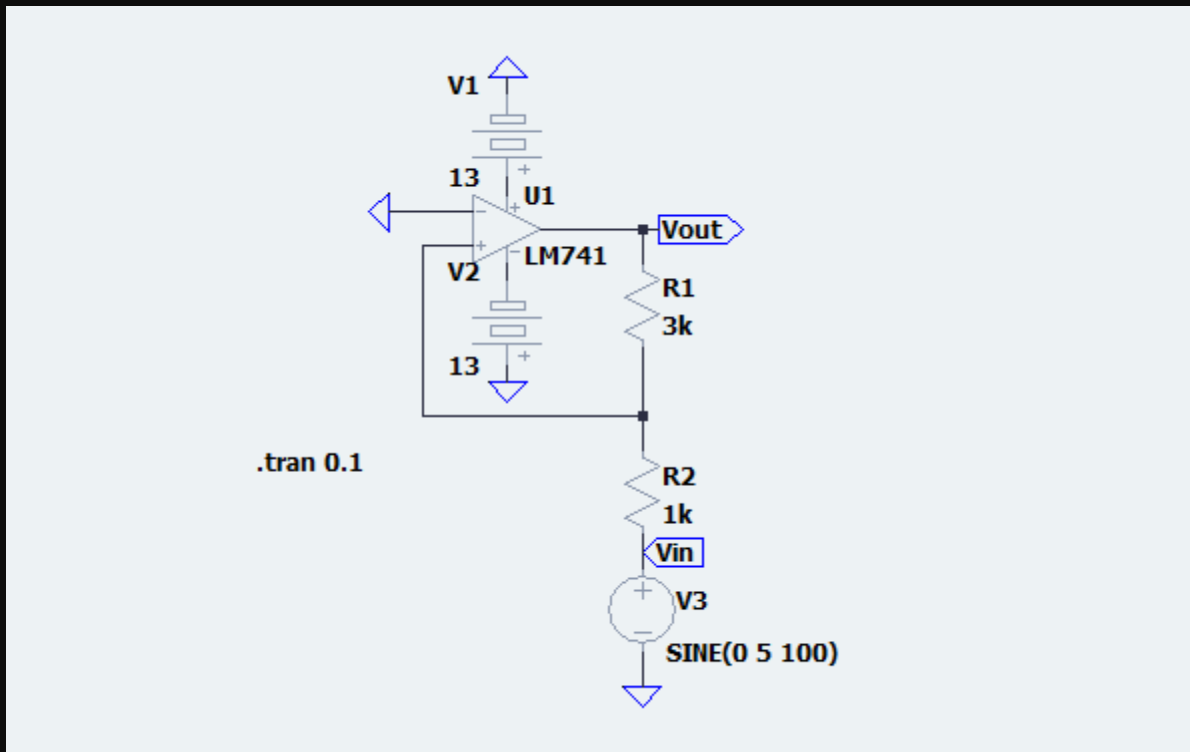


Waveform:

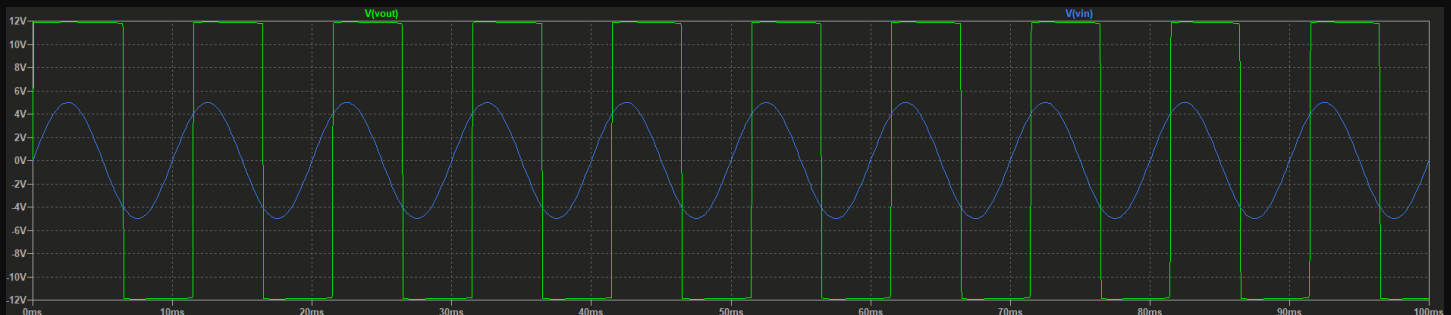


For 2V amplitude:

Circuit in LTspice:

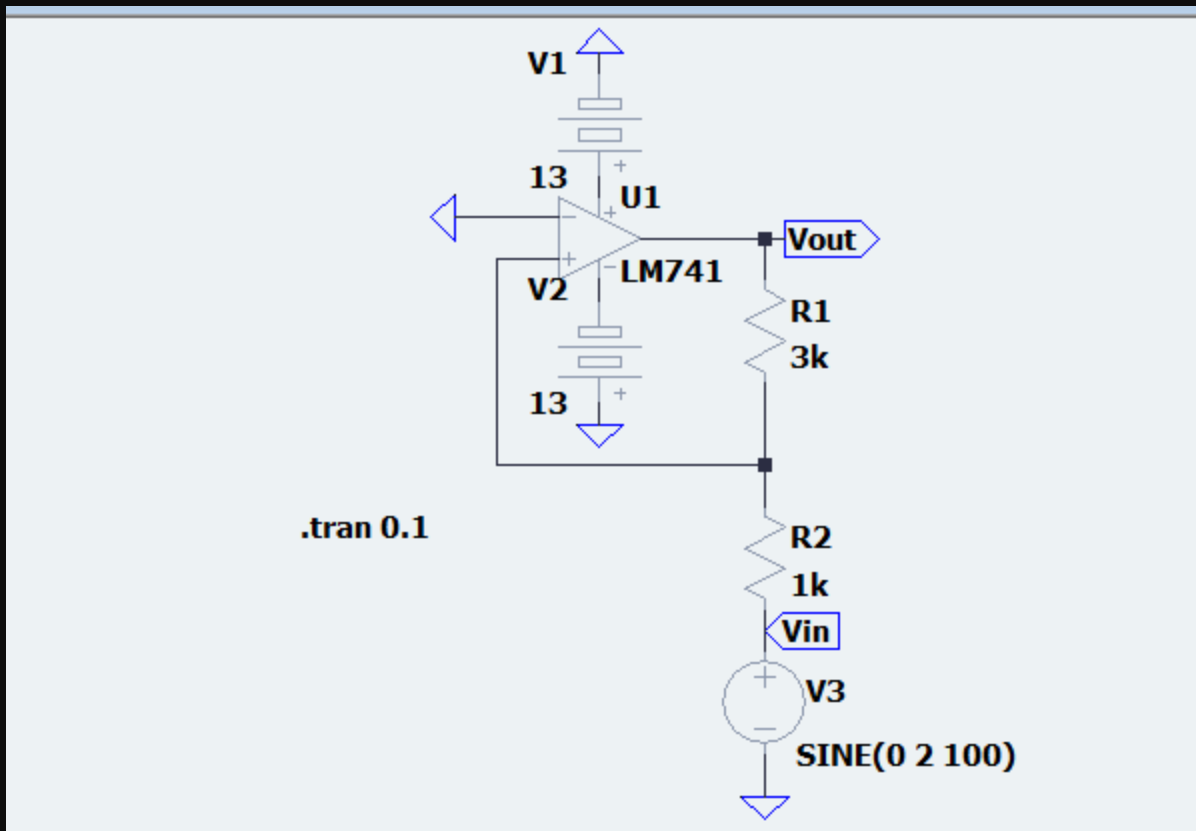

Waveform:

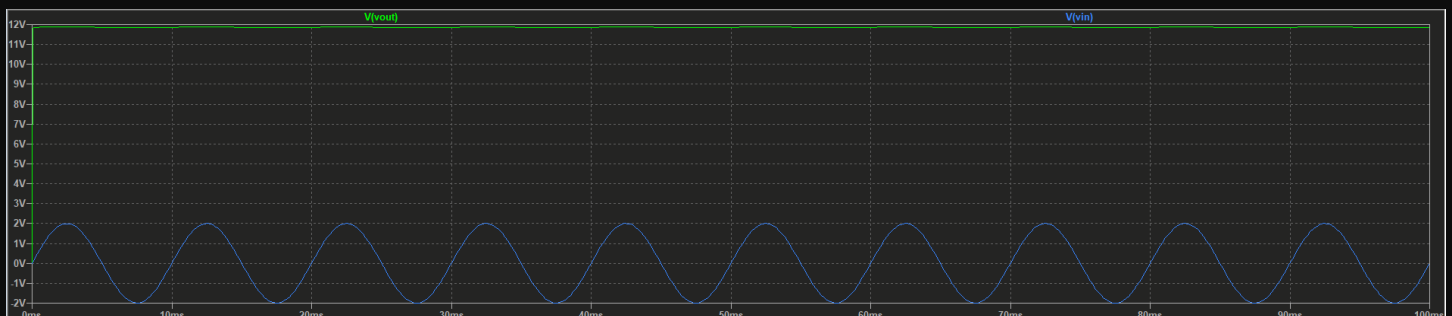

Think about these:

What happens if the input terminals of op-amp in comparator circuit are interchanged?

-> Since we will be just switching the input terminal from the negative to output, we will get an inverted output compared to the output of the original circuit.

Can you design a Schmitt trigger circuit where $|V_{LT}| \neq |V_{UT}|$ If yes, how? Design any one circuit.

-> Yes, we can design Schmitt trigger circuit with unequal thresholds. We can do it in many ways. For Inverting circuit, we can do it by using an additional Vref source or using additional resistor with diodes for having different resistance for opposite current flow.

We will build a circuit for the 2nd method.

Considering $V_{cc} = 13V$.

Given $V_{sat} = V_{cc} - 1 = 12V$,

Knowing that for inverting Schmitt trigger,

$$V_{UT} = \frac{R_2}{R_2 + R_1} V_{sat}$$

$$V_{LT} = \frac{R_3}{R_3 + R_1} (-V_{sat})$$


Considering $R_1 = 3k\Omega$

We will set $V_{UT} = 6V$ and $V_{LT} = 3V$,


Matching the above conditions,

we get $R_2 = 3k\Omega$ and $R_3 = 1k\Omega$

Circuit in LTspice:

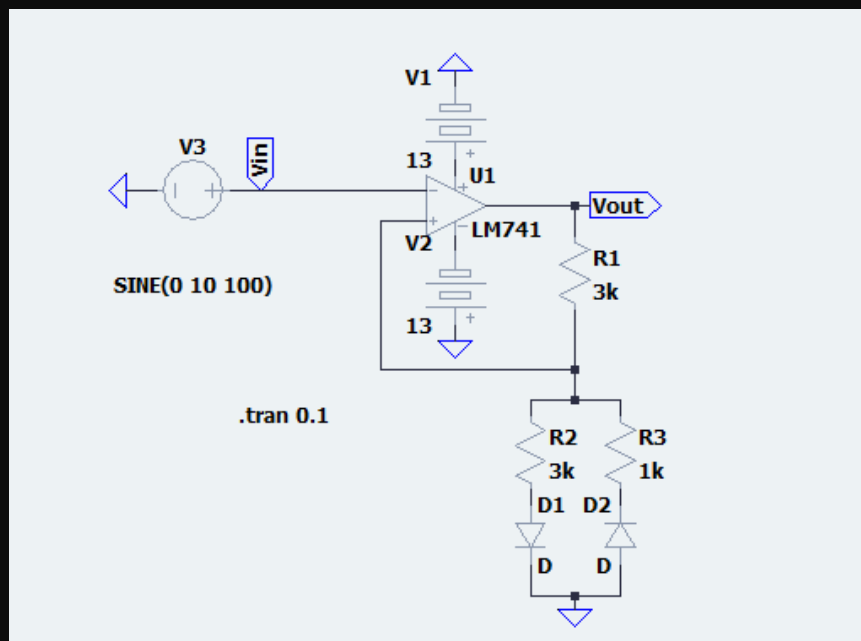


Waveform:

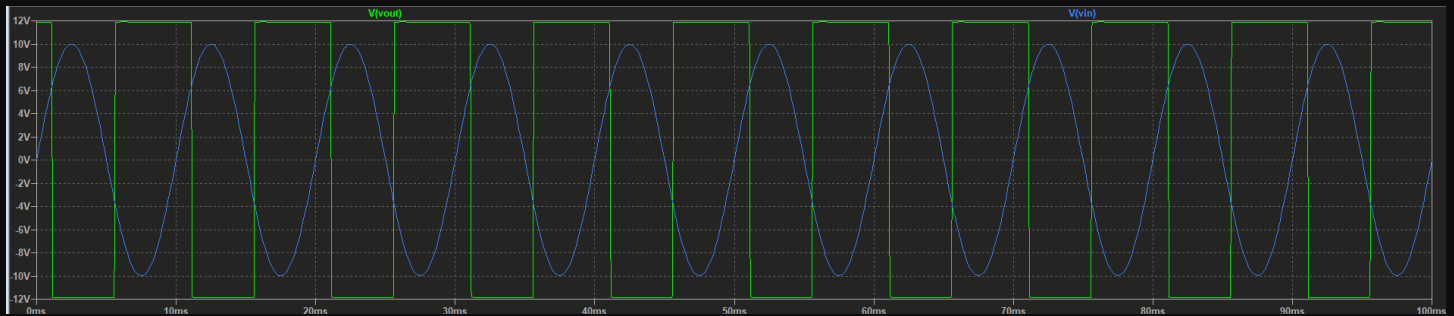

For 5V amplitude:

Circuit in LTspice:

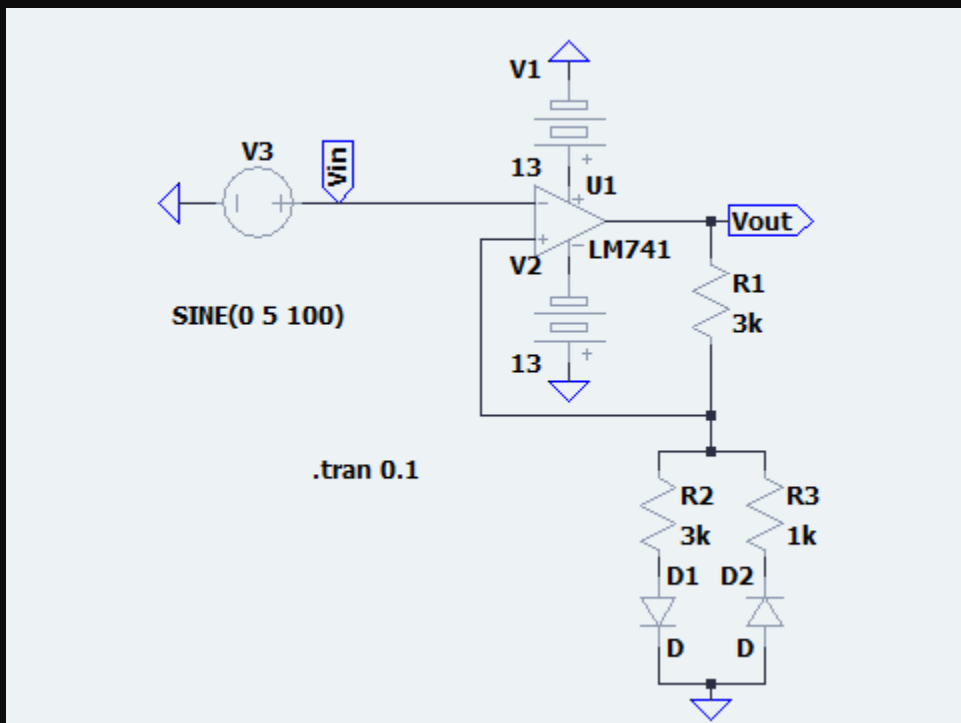

Waveform:

