

EC 205 Analog Electronics Lab

Experiment No. 7

Expt. 7 : Inverting Adder

Aim:

To design an Inverting Adder to add signals.

Circuit Diagram:

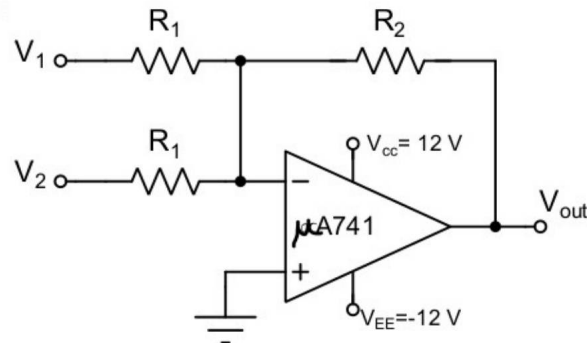


Figure 1: inverting adder

1. Design the inverting adder and test it with two inputs $V_1 = 2\sin(10007rt)$ and $V_2 = 3\text{ V DC}$.

obz>€.ntve

and analyse the output $k^{(xve_+o-rt^r)}$.

Think about these

- What is the impedance seen by each of the input signal source?
- With $R_1 = R_2 = 10\text{ k}\Omega$, apply a sinusoidal input of 10 V peak-to-peak and frequency 1 kHz at V_1 and set V_2 to zero. You should observe an inverted sine wave of 10 V peak-to-peak at the output. Now slowly start increasing the input frequency upto 1 MHz. What do you notice? Can you justify the observation?
- Now, decrease the input to 2 V peak-to-peak and repeat the experiment. What do you observe and why?
- Take a μA741 opamp and short circuit both the inverting and non-inverting terminals of the opamp to ground. What voltage do you expect at the output when the opamp is powered and what do you actually see? **imp** **nt** **cxzrxd** **output offset** **Vp** **ltage**