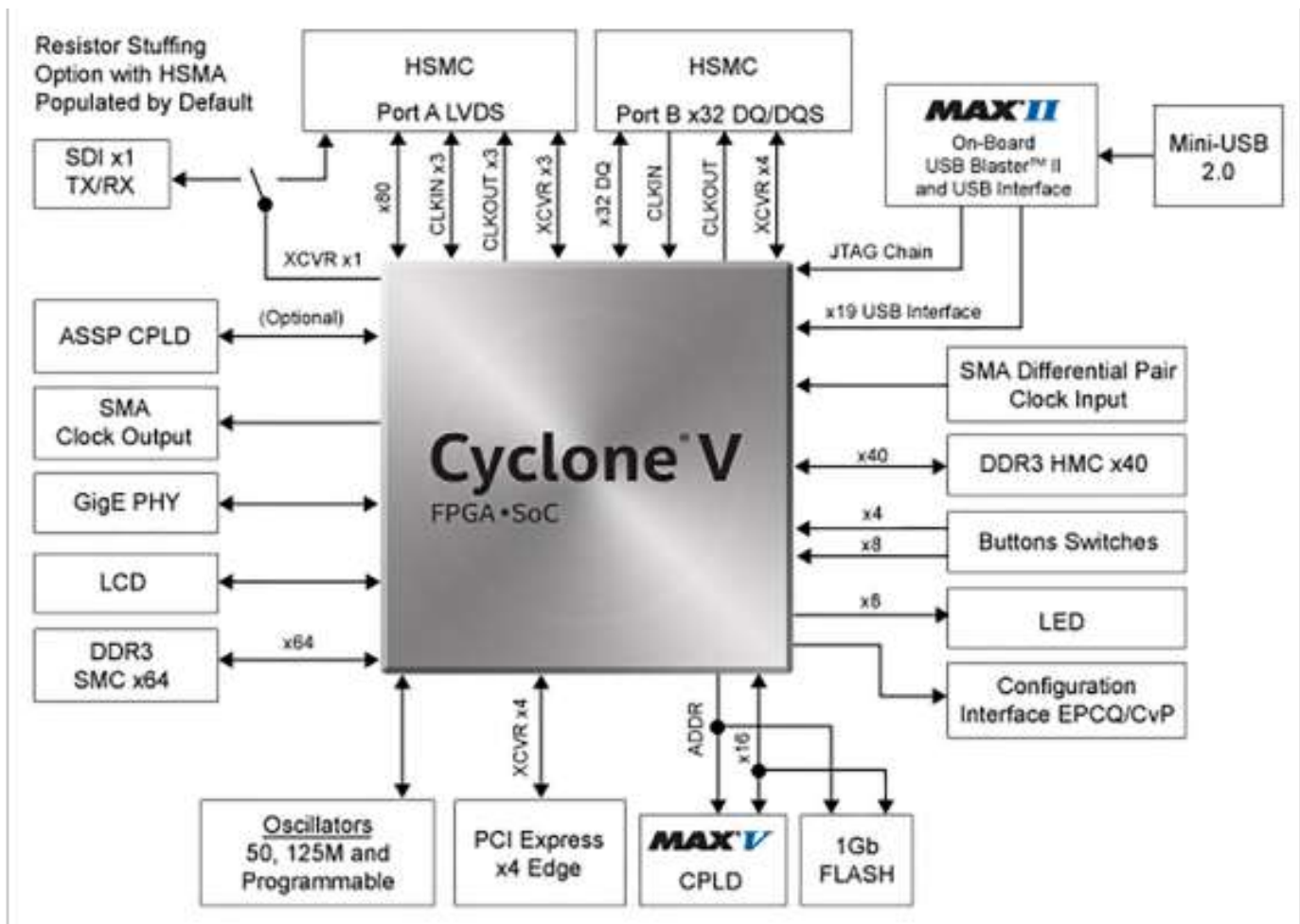



EC-340

COMPUTER ORGANIZATION AND ARCHITECTURE



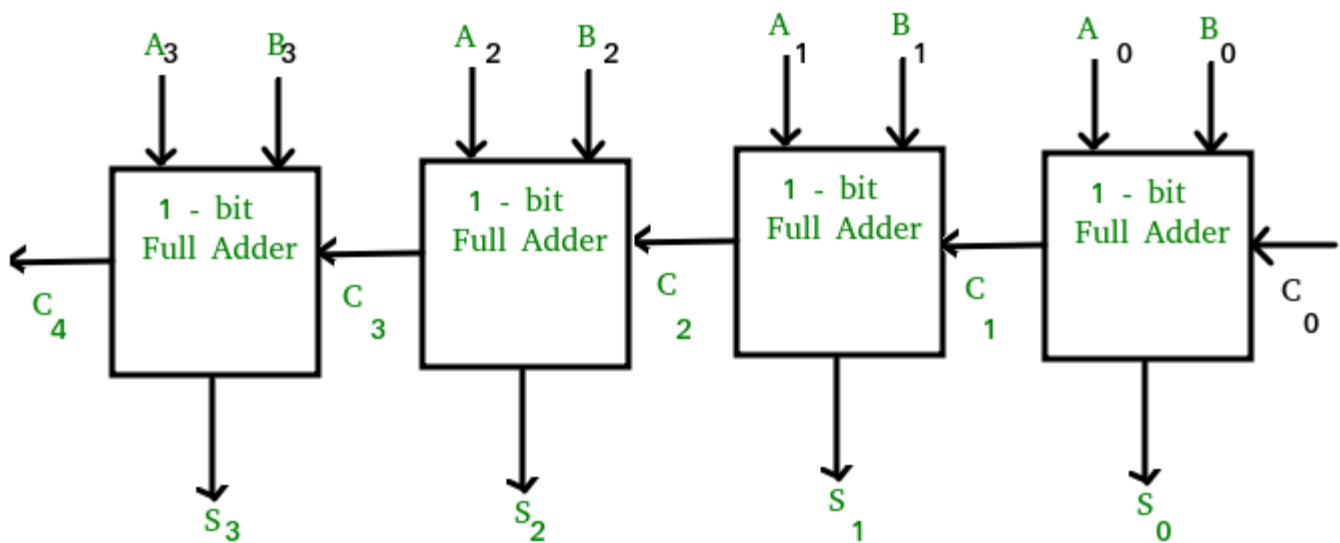1. (a) 8 bit ripple carry adder

It is a combinational circuit for adding 2 binary numbers requiring N full adders for N bit adder. Here for 8 bits, we will take 8 full adders, connect the cin to the first cin of first full adder and then cout of the first adder to the cin of the next and so on. While inputs $a[i]$, $b[i]$ to the i 'th full adder. And take output of each full adder as $s[i]$. considering the cout of the last full adder as the output cout.



(Image from GFG)

Verilog Code for the module:

```
module ripple_carry_adder (input [7:0] a , b, input cin, output [7:0] s,
output cout);
wire [8:0] c;
assign c[0] = cin;
assign cout = c[8];
genvar i;
generate
    for (i=0; i<8; i= i+1) begin: full_adders
        full_adder fa(.a(a[i]), .b(b[i]), .cin(c[i]), .s(s[i]),
.cout(c[i+1]));
    end
endgenerate
endmodule
```

Verilog code for the full adder:

```
module full_adder(input a, b, cin, output s, cout);
assign {cout, s} = a + b + cin;
endmodule
```

Verilog code for the test bench:


```
module ripple_carry_adder (input [7:0] a , b, input cin, output [7:0] s,
output cout);
wire [8:0] c;
assign c[0] = cin;
assign cout = c[8];
genvar i;
    generate
        for (i=0; i<8; i= i+1) begin: full_adders
            full_adder fa(.a(a[i]), .b(b[i]), .cin(c[i]), .s(s[i]),
.cout(c[i+1]));
        end
    endgenerate
endmodule
```

Device Utilization Statistics:


Flow summary:

| | |
|---------------------------------|---|
| Flow Summary | |
| <<Filter>> | |
| Flow Status | Successful - Thu Feb 17 04:56:54 2022 |
| Quartus Prime Version | 21.1.0 Build 842 10/21/2021 SJ Lite Edition |
| Revision Name | ripple_carry_adder |
| Top-level Entity Name | ripple_carry_adder |
| Family | Cyclone V |
| Device | 5CSEMA5F31C6 |
| Timing Models | Final |
| Logic utilization (in ALMs) | 21 / 32,070 (< 1 %) |
| Total registers | 0 |
| Total pins | 26 / 457 (6 %) |
| Total virtual pins | 0 |
| Total block memory bits | 0 / 4,065,280 (0 %) |
| Total DSP Blocks | 0 / 87 (0 %) |
| Total HSSI RX PCSs | 0 |
| Total HSSI PMA RX Deserializers | 0 |
| Total HSSI TX PCSs | 0 |
| Total HSSI PMA TX Serializers | 0 |
| Total PLLs | 0 / 6 (0 %) |
| Total DLLs | 0 / 4 (0 %) |

Resource usage summary:
 
| Analysis & Synthesis Resource Usage Summary | | |
|--|---|------------|
|  <<Filter>> | | |
| | Resource | Usage |
| 1 | Estimate of Logic utilization (ALMs needed) | 20 |
| 2 | | |
| 3 | ▼ Combinational ALUT usage for logic | 40 |
| 1 | -- 7 input functions | 0 |
| 2 | -- 6 input functions | 0 |
| 3 | -- 5 input functions | 3 |
| 4 | -- 4 input functions | 13 |
| 5 | -- <=3 input functions | 24 |
| 4 | | |
| 5 | Dedicated logic registers | 0 |
| 6 | | |
| 7 | I/O pins | 26 |
| 8 | | |
| 9 | Total DSP Blocks | 0 |
| 10 | | |
| 11 | Maximum fan-out node | a[2]~input |
| 12 | Maximum fan-out | 10 |
| 13 | Total fan-out | 168 |
| 14 | Average fan-out | 1.83 |

Block Diagram (Technology map viewer):

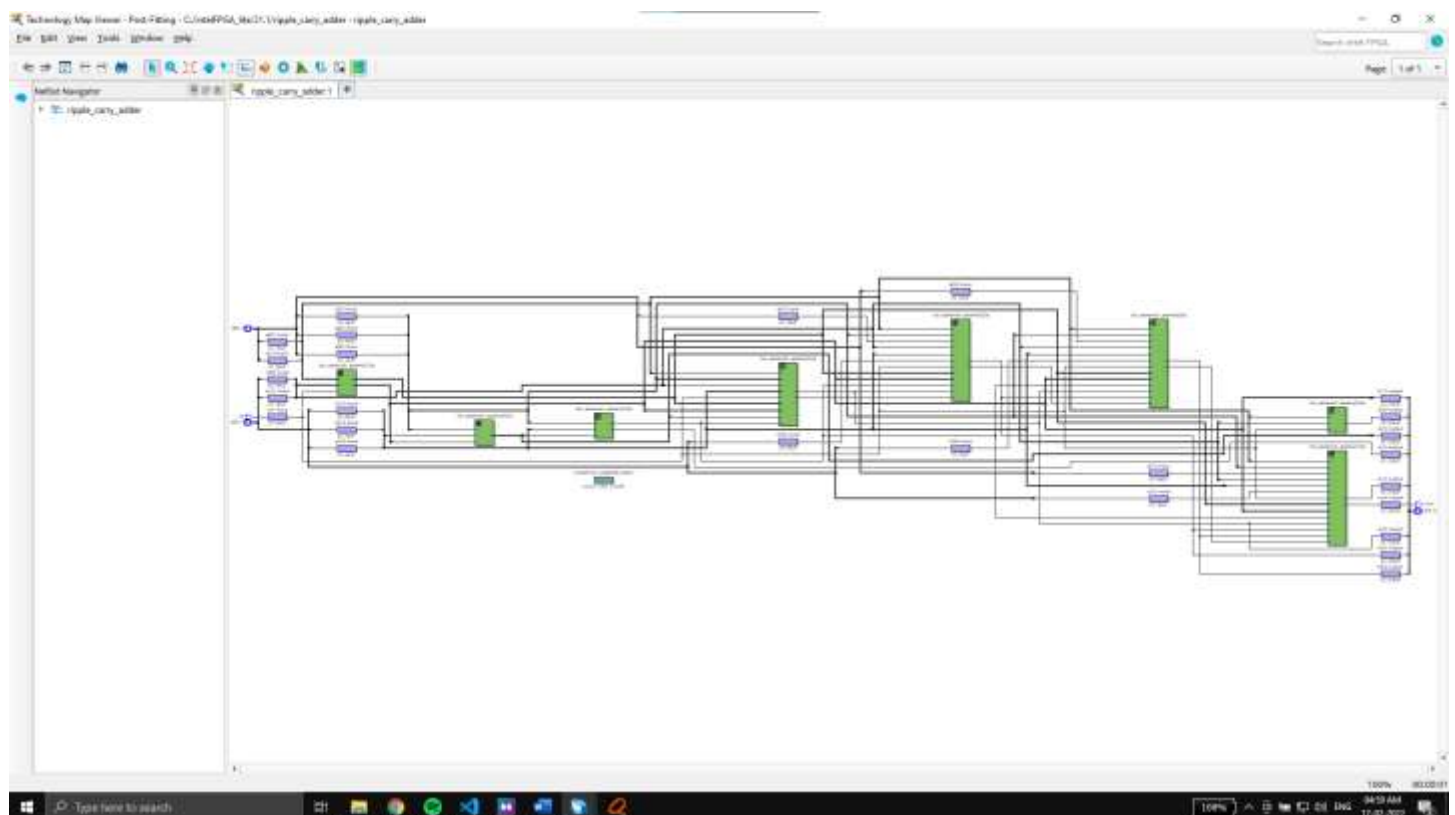

Timing reports:

Clocks

No clocks to report.

Slow 1100mV 85C Model Fmax Summary

No paths to report.

Unconstrained Paths Summary

<<Filter>>

| | Property | Setup | Hold |
|---|---------------------------------|-------|------|
| 1 | Illegal Clocks | 0 | 0 |
| 2 | Unconstrained Clocks | 0 | 0 |
| 3 | Unconstrained Input Ports | 17 | 17 |
| 4 | Unconstrained Input Port Paths | 97 | 97 |
| 5 | Unconstrained Output Ports | 9 | 9 |
| 6 | Unconstrained Output Port Paths | 97 | 97 |

Multicorner Timing Analysis Summary


<<Filter>>

| | Clock | Setup | Hold | Recovery | Removal | Minimum Pulse Width |
|---|------------------|-------|------|----------|---------|---------------------|
| 1 | Worst-case Slack | N/A | N/A | N/A | N/A | N/A |
| 2 | Design-wide TNS | 0.0 | 0.0 | 0.0 | 0.0 | 0.0 |

Simulation in Questa through Quartus:

The screenshot shows the Quartus II IDE interface. The top window is the 'Compilation Progress' dialog, which is currently empty. The bottom window is the 'Messages' pane, displaying the compilation log. The log indicates that the compilation is complete, with no errors or warnings. The status bar at the bottom shows '100%' completion.

Wave:

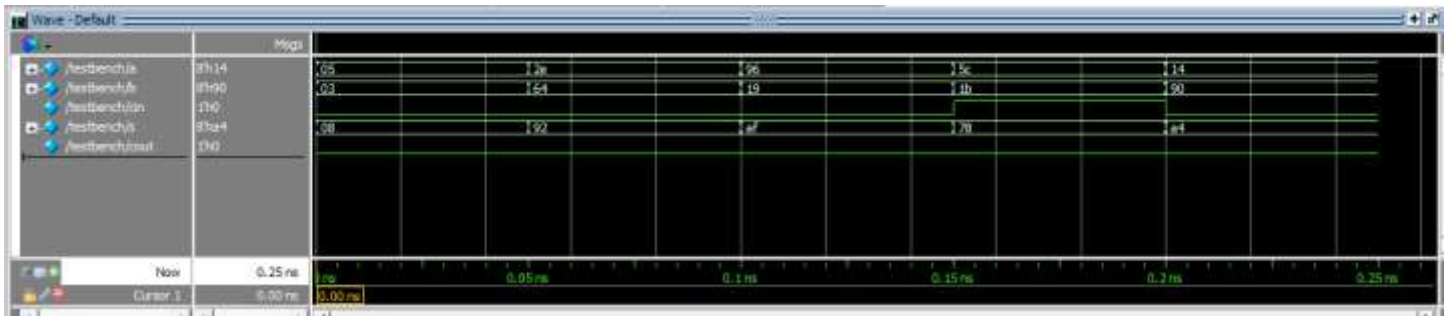


1. (b) 8-bit controllable adder/subtractor

An 8-bit controllable adder/subtractor is capable of both addition and subtraction of binary numbers. We will make use of 8 full adders and XOR gates for designing the circuit with Verilog.

We will have 3 inputs, A and B of width 8 bits. The addition or subtraction operation will be performed on them depending upon the third input K of size 1 bit.

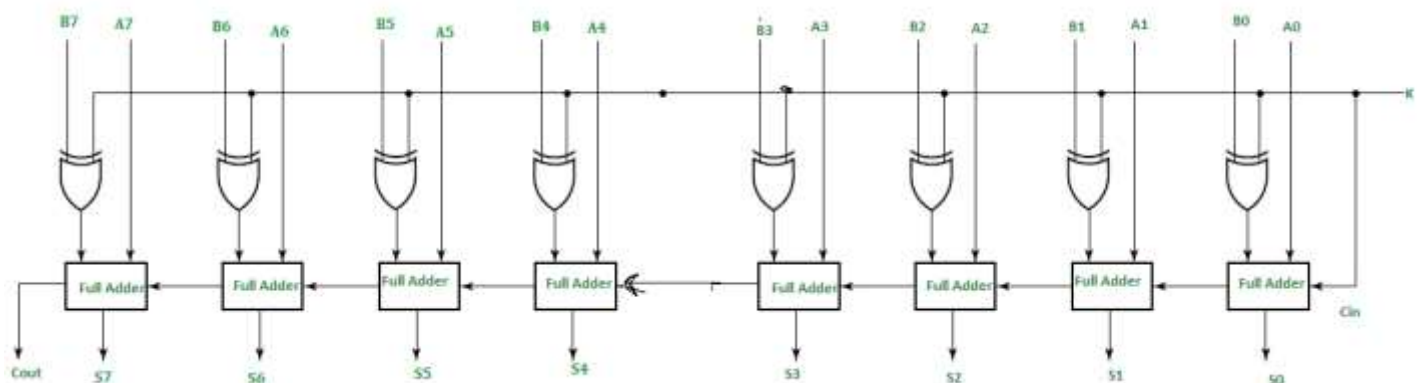If $k=1$, We will perform subtraction and if $k=0$, then we will perform addition.



(Image from GFG(edited))

Verilog Code for the module:

```
module add_sub(input [7:0]a, b, input k, output [7:0]s, output cout);
wire [8:0] c;
genvar i;
assign c[0] = k;
assign cout = c[8];
generate
    for (i=0; i<8; i= i+1) begin: add_sub
        full_adder fa(.a(a[i]), .b(b[i]^k), .cin(c[i]), .s(s[i]),
.cout(c[i+1]));
    end
endgenerate
endmodule
```

Verilog code for the full adder:

```
module full_adder(input a, b, cin, output s, cout);
    assign {cout, s} = a + b + cin;
endmodule
```

Verilog code for the test bench:

```
module testbench();
reg [7:0] a, b;
reg k;
wire [7:0] s;
wire cout;
add_sub asc(a, b, k, s, cout);
initial begin
    a=5; b=3; k=0;
#50 a=46; b=100; k=0;
#50 a=150; b=25; k=0;
#50 a=8'b01011100; b=8'b00011011; k=1;
#50 a=20; b=8'b10010000; k=0; #50;
end
endmodule
```

Device Utilization Statistics:

Flow summary:

| Flow Summary | |
|---------------------------------|---|
| <<Filter>> | |
| Flow Status | In progress - Thu Feb 17 03:25:49 2022 |
| Quartus Prime Version | 21.1.0 Build 842 10/21/2021 SJ Lite Edition |
| Revision Name | add_sub |
| Top-level Entity Name | add_sub |
| Family | Cyclone V |
| Device | 5CSEMA5F31C6 |
| Timing Models | Final |
| Logic utilization (in ALMs) | N/A |
| Total registers | 0 |
| Total pins | 26 |
| Total virtual pins | 0 |
| Total block memory bits | 0 |
| Total DSP Blocks | 0 |
| Total HSSI RX PCSs | 0 |
| Total HSSI PMA RX Deserializers | 0 |
| Total HSSI TX PCSs | 0 |
| Total HSSI PMA TX Serializers | 0 |
| Total PLLs | 0 |
| Total DLLs | 0 |

Resource usage summary:

| Analysis & Synthesis Resource Usage Summary | | |
|---|---|---------|
| <<Filter>> | | |
| | Resource | Usage |
| 1 | Estimate of Logic utilization (ALMs needed) | 21 |
| 2 | | |
| 3 | ▼ Combinational ALUT usage for logic | 42 |
| 1 | -- 7 input functions | 0 |
| 2 | -- 6 input functions | 0 |
| 3 | -- 5 input functions | 3 |
| 4 | -- 4 input functions | 16 |
| 5 | -- <=3 input functions | 23 |
| 4 | | |
| 5 | Dedicated logic registers | 0 |
| 6 | | |
| 7 | I/O pins | 26 |
| 8 | | |
| 9 | Total DSP Blocks | 0 |
| 10 | | |
| 11 | Maximum fan-out node | k~input |
| 12 | Maximum fan-out | 20 |
| 13 | Total fan-out | 182 |
| 14 | Average fan-out | 1.94 |

Block Diagram (Technology map viewer):



Timing reports:

The screenshot shows the 'Compilation Report - add_sub' window. The 'Table of Contents' pane on the left lists the following sections:

- Flow Elapsed Time
- Flow OS Summary
- Flow Log
- Analysis & Synthesis
- Fitter
- Assembler
- Timing Analyzer
 - Summary
 - Parallel Compilation
 - Clocks
 - Slow 1100mV 85C Model
 - Fmax Summary
 - Timing Closure Recommendations
 - Status Summary

The main pane displays the 'Slow 1100mV 85C Model Fmax Summary' section, which contains the text: 'No paths to report.'

Compilation Report - add_sub X

Table of Contents

- Recovery Summary
- Removal Summary
- Minimum Pulse Width Summ
- Metastability Summary
- Fast 1100mV OC Model
 - Setup Summary
 - Hold Summary
 - Recovery Summary
 - Removal Summary
 - Minimum Pulse Width Summ
 - Metastability Summary
- Multicorner Timing Analysis Sum
- Advanced I/O Timing
 - Clock Transfers
 - Report TCCS
 - Report RSKM
- Unconstrained Paths
 - Summary**
 - Setup Analysis
 - Hold Analysis

Unconstrained Paths Summary

<<Filter>>


| | Property | Setup | Hold |
|---|---------------------------------|-------|------|
| 1 | Illegal Clocks | 0 | 0 |
| 2 | Unconstrained Clocks | 0 | 0 |
| 3 | Unconstrained Input Ports | 17 | 17 |
| 4 | Unconstrained Input Port Paths | 96 | 96 |
| 5 | Unconstrained Output Ports | 9 | 9 |
| 6 | Unconstrained Output Port Paths | 96 | 96 |

Simulation in Questa through Quartus:



Wave:

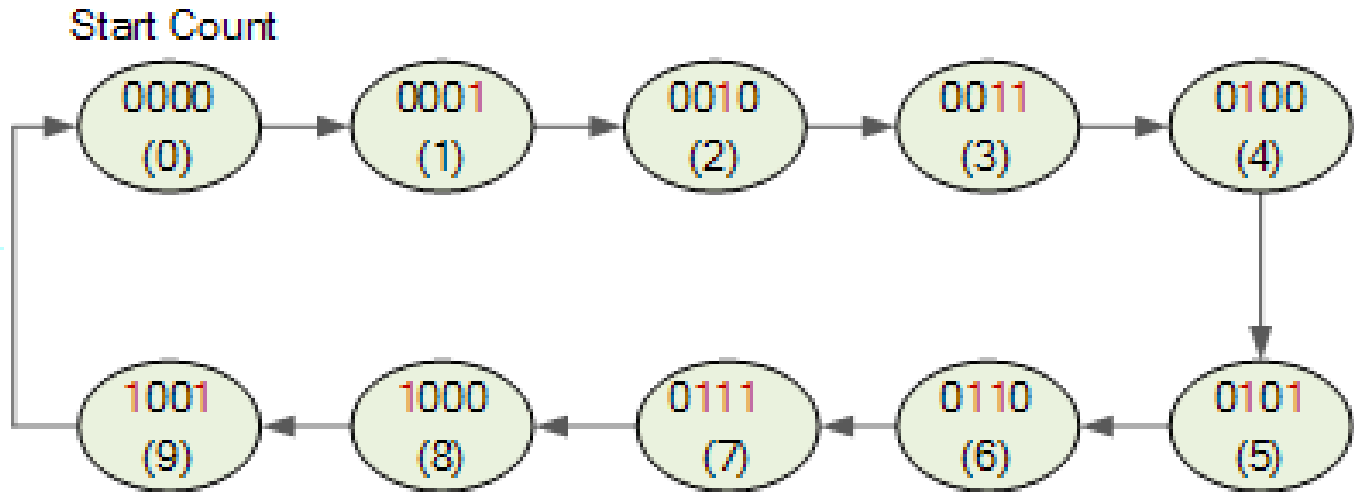We will set TC to 1 for the conditions mentioned above in the question.



Verilog Code for the Decade counter:

```
module decade_counter (count_up, reset, load, counter_on, clk, data_in, count, TC);
input count_up, reset, load, counter_on, clk;
input [3:0] data_in;
output reg [3:0] count;
output reg TC;

localparam [3:0] s0=4'b0000, s1=4'b0001, s2=4'b0010, s3=4'b0011, s4=4'b0100, s5=4'b0101,
s6=4'b0110, s7=4'b0111, s8=4'b1000, s9=4'b1001;
reg [3:0] state, next_state;
always @ (posedge clk or negedge reset) begin
    if(!reset) begin state<= s0; end
    else if(load) begin
        state <= data_in;
    end else if(counter_on) state<= next_state;
end

always @(state) begin
    case(state)
        s0: begin if(count_up) begin next_state <= s1; TC<=0; end
                else begin next_state <= s9; TC<=1; end
                count<= 0;
            end
        s1: begin if(count_up)begin next_state <= s2; end else begin next_state <= s0; end
            count <= 1; TC<=1; end
        s2: begin if(count_up)begin next_state <= s3; end else begin next_state <= s1; end
            count <= 2; TC<=0; end
        s3: begin if(count_up)begin next_state <= s4; end else begin next_state <= s2; end
            count <= 3; TC<=0; end
        s4: begin if(count_up)begin next_state <= s5; end else begin next_state <= s3; end
            count <= 4; TC<=0; end
```

```

    s5: begin if(count_up)begin next_state <= s6; end else begin next_state <= s4; end
count <= 5; TC<=0; end
    s6: begin if(count_up)begin next_state <= s7; end else begin next_state <= s5; end
count <= 6; TC<=0; end
    s7: begin if(count_up)begin next_state <= s8; end else begin next_state <= s6; end
count <= 7; TC<=0; end
    s8: begin if(count_up)begin next_state <= s9; end else begin next_state <= s7; end
count <= 8; TC<=0; end
    s9: begin if(count_up)begin next_state <= s0; TC<=1; end else begin next_state <= s8;
TC<=0; end count <= 9; end
    default: begin next_state <=s0; count <=0; TC=0; end
endcase
end
endmodule

```

Verilog code for the test bench:

```

module testbench_1();
integer i;
reg clk, counter_on, reset, load, count_up;
reg [3:0] data_in;
wire [3:0] count;
wire TC;
decade_counter dc1(count_up, reset, load, counter_on, clk, data_in, count,
TC);
initial
begin
counter_on=1; count_up =1;
reset=1; clk=1; #1; reset=0; #1 reset=1;
load=0; data_in =4'b1000;
for( i=0; i<10; i=i+1)begin
clk =1; #20; clk =0; #20;
end
load =1;
clk =1; #20; clk =0; #20; load =0;
count_up =0;
for( i=0; i<5; i=i+1)begin
clk =1; #20; clk =0; #20;
end
end
endmodule

```

Device Utilization Statistics:

Flow summary:


| Flow Summary | |
|---------------------------------|---|
| <<Filter>> | |
| Flow Status | Successful - Wed Feb 16 15:39:03 2022 |
| Quartus Prime Version | 21.1.0 Build 842 10/21/2021 SJ Lite Edition |
| Revision Name | decade_counter |
| Top-level Entity Name | decade_counter |
| Family | Cyclone V |
| Device | 5CSEMA5F31C6 |
| Timing Models | Final |
| Logic utilization (in ALMs) | 9 / 32,070 (< 1 %) |
| Total registers | 4 |
| Total pins | 14 / 457 (3 %) |
| Total virtual pins | 0 |
| Total block memory bits | 0 / 4,065,280 (0 %) |
| Total DSP Blocks | 0 / 87 (0 %) |
| Total HSSI RX PCSs | 0 |
| Total HSSI PMA RX Deserializers | 0 |
| Total HSSI TX PCSs | 0 |
| Total HSSI PMA TX Serializers | 0 |
| Total PLLs | 0 / 6 (0 %) |
| Total DLLs | 0 / 4 (0 %) |

Resource usage summary:

abc decade_counter.v X


abc testbench_1.v X

Analysis & Synthesis Resource Usage Summary

 <<Filter>>

| | Resource | Usage |
|----|---|----------|
| 1 | Estimate of Logic utilization (ALMs needed) | 9 |
| 2 | | |
| 3 | ▼ Combinational ALUT usage for logic | 14 |
| 1 | -- 7 input functions | 1 |
| 2 | -- 6 input functions | 2 |
| 3 | -- 5 input functions | 4 |
| 4 | -- 4 input functions | 4 |
| 5 | -- <=3 input functions | 3 |
| 4 | | |
| 5 | Dedicated logic registers | 4 |
| 6 | | |
| 7 | I/O pins | 14 |
| 8 | | |
| 9 | Total DSP Blocks | 0 |
| 10 | | |
| 11 | Maximum fan-out node | state[3] |
| 12 | Maximum fan-out | 11 |
| 13 | Total fan-out | 93 |
| 14 | Average fan-out | 2.02 |

Block Diagram (Technology map viewer):

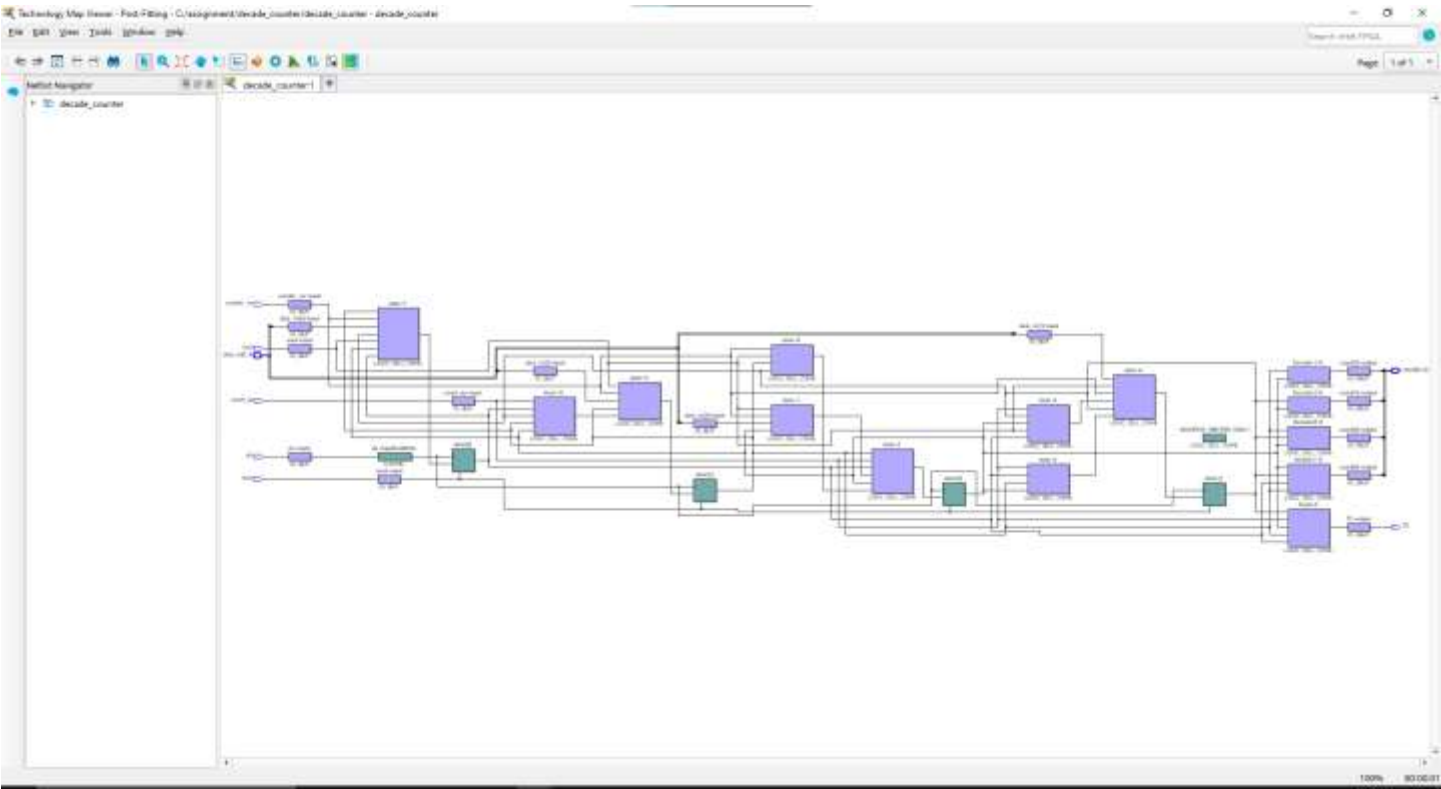

Timing reports:

Compilation Report - decade_counter

Table of Contents

- Flow Summary
- Flow Settings
- Flow Non-Default Global Settings
- Flow Elapsed Time
- Flow OS Summary
- Flow Log
- Analysis & Synthesis
 - Fitter
 - Assembler
 - Timing Analyzer
 - Summary
 - Parallel Compilation
 - Clocks
- Slow 1100mV 85C Model


Clocks


| Clock Name | Type | Period | Frequency | Rise | Fall | Duty Cycle | Divide by | Multiply by | Phase | Offset | Edge List | Edge Shift | Inverted | Master | Source | Targets |
|------------|------|--------|-----------|------------|-------|------------|-----------|-------------|-------|--------|-----------|------------|----------|--------|--------|---------|
| 1 | clk | Base | 1.000 | 1000.0 MHz | 0.000 | 0.500 | | | | | | | | | | { clk } |


| Multicorner Timing Analysis Summary | | | | | | |
|-------------------------------------|--------------------|--------|-------|----------|---------|---------------------|
| <<Filter>> | | | | | | |
| | Clock | Setup | Hold | Recovery | Removal | Minimum Pulse Width |
| 1 | ▼ Worst-case Slack | -0.859 | 0.174 | N/A | N/A | -0.394 |
| 1 | clk | -0.859 | 0.174 | N/A | N/A | -0.394 |
| 2 | ▼ Design-wide TNS | -2.039 | 0.0 | 0.0 | 0.0 | -2.264 |
| 1 | clk | -2.039 | 0.000 | N/A | N/A | -2.264 |

For slow 85C model:


For fast OC model:

| Fast 1100mV OC Model Setup Summary | | | |
|--|-------|-------|---------------|
|  <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.018 | 0.000 |


| Fast 1100mV OC Model Hold Summary | | | |
|--|-------|-------|---------------|
|  <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.174 | 0.000 |

| Fast 1100mV OC Model Minimum Pulse Width Summary | | | |
|--|-------|--------|---------------|
|  <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | -0.081 | -0.324 |

Simulation in Questa through Quartus:

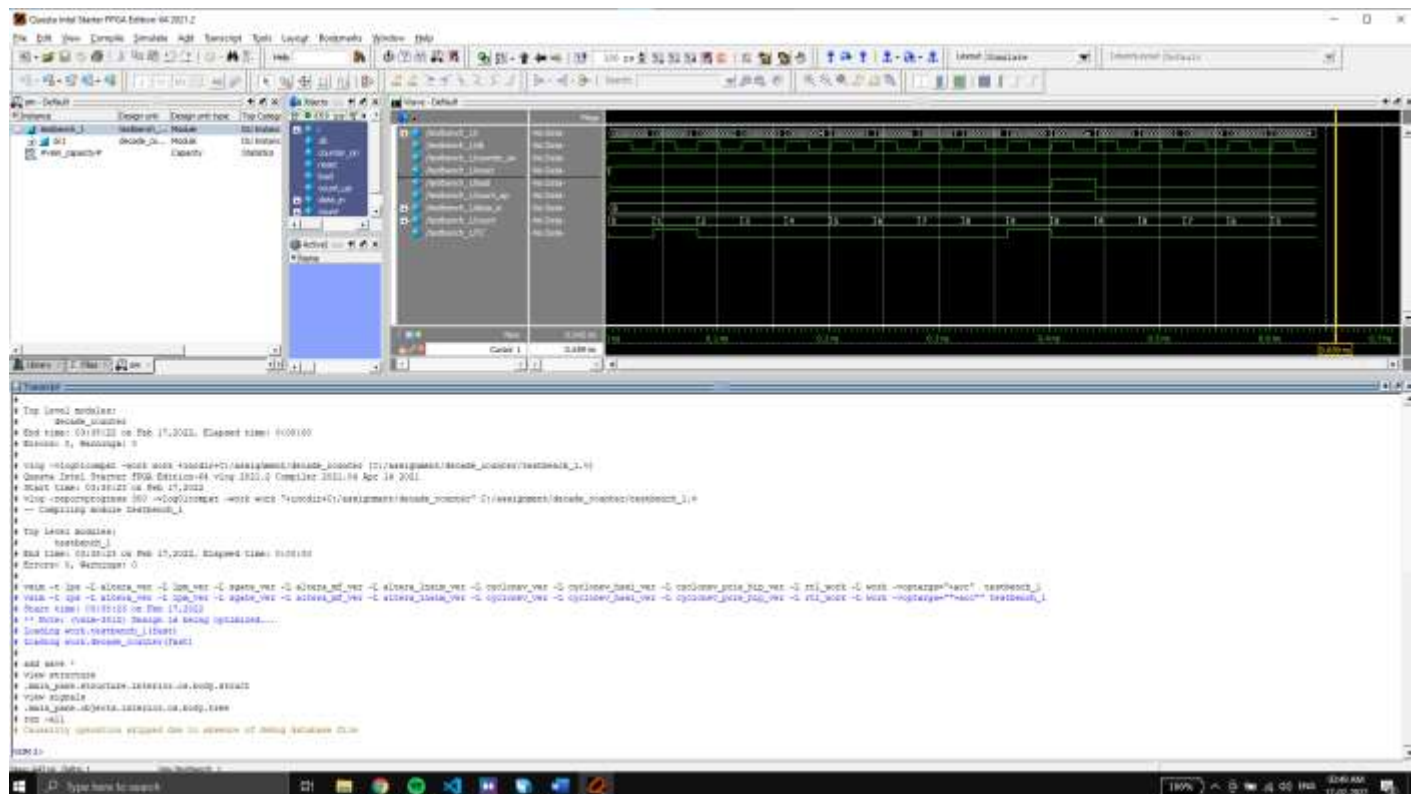

Wave:

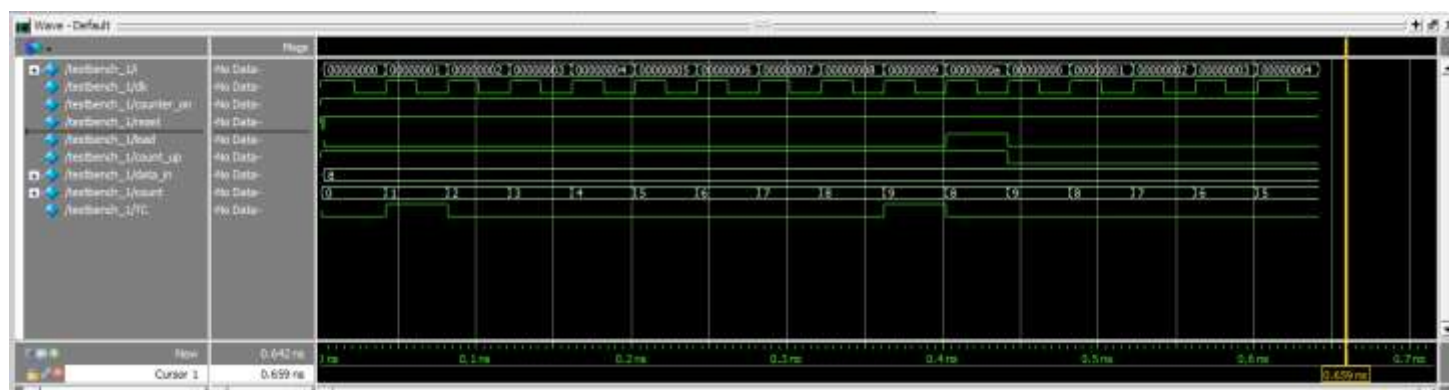

3. Serial adder to add two 8 bit numbers using a single full adder and registers


->Serial adder performs the addition of 2 binary numbers in serial form.

For designing the module, we will use separate submodules:

- 8 Right Shift registers: for inputs a, b and output s (sum)
- D flip flop: for storing carry
- Full adder: for carrying out addition of LSB of both inputs a and b and storing it in the msb of output sum.

We will use output register **done** for indicating the completion of addition. Keeping our FSM positive edge activated with a asynchronous reset.

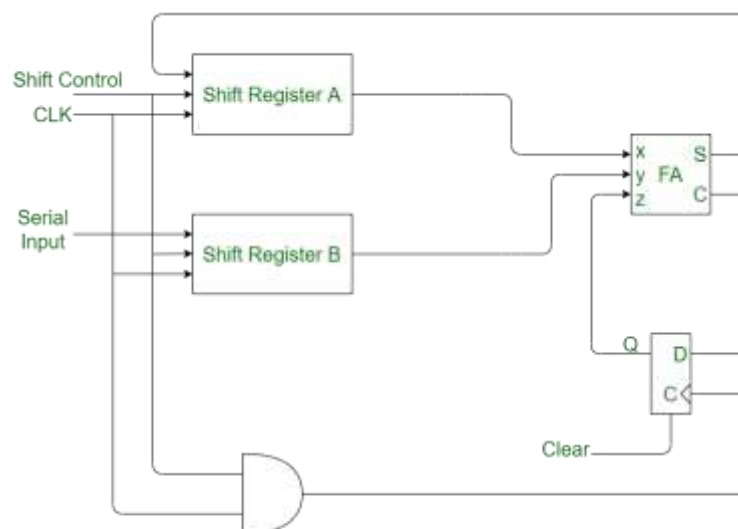We will take inputs at the MSB of inputs A and B and then shift them throughout the shift register, while at the same time we will right shift the sum. after 15 clock cycles we will have completely done taking in the input and adding them and storing it in output shift register sum. At which we will enable done. [\(image from gfg\)](#)



Block Diagram of Serial Binary Adder

Verilog Code for the Serial Adder:

```
// sum output is at output reg sum and the carry of the sum is at output reg c.
module serial_adder(
input ain, bin, clk, start, resetn,
output [7:0] sum, output reg done, output c);
//wires for connecting different modules
wire [7:0] rxQ, ryQ, rsQ; wire fas, fac, dffc;
reg [3:0] count = 4'b1111;
reg [7:0] D = 0;
reg load = 0;
//connecting wires from modules to output registers.
assign sum = rsQ;
assign c = fac;
shiftr regX(.D(D), .load(load), .shiftR(!done),.lin(ain), .clk(clk),
.Q(rxQ));
shiftr regY(.D(D), .load(load), .shiftR(!done),.lin(bin), .clk(clk),
.Q(ryQ));
shiftr regSum(.D(D), .load(load), .shiftR(!done),.lin(fas), .clk(clk),
.Q(rsQ));
fulladder fa(.a(rxQ[0]), .b(ryQ[0]), .cin(dffc), .sum(fas), .cout(fac));
dfflipflop da(.d(fac), .reset(load), .clk(clk), .q(dffc));
//for decrementing counter and making a reset button for entire module.
always @(posedge clk, negedge resetn)
begin
if(!resetn) begin
load<= 1;
count<=15;
done<=0;
end else if(start) begin
load<= 0;
if(count >0) begin done <= 0;
count<= count -1;
end
else done <=1;
end
endmodule
//single bit full adder module required.
module fulladder(input a, b, cin, output sum, cout);
assign sum = cin^(a^b);
assign cout = (a&b) | cin&(a^b);
endmodule
// D flip flop
module dfflipflop(input d, reset, clk, output reg q);
always@(posedge clk, posedge reset)
begin
if(reset) q=0;
```

```

else begin
q=d;
end
end
endmodule
//8 bit shift register with load support.
module shiftreg (input [7:0]D, input load, shiftR, lin, clk, output reg
[7:0]Q);

always @(posedge clk)
begin
if(load) Q<=D;
else if(shiftR) Q <= {lin, Q[7:1]};
end
endmodule

```

Verilog code for the test bench:

```

module tb2();
reg a, b, clk, start, resetn;
wire [7:0]sum;
wire done, c;
reg [7:0] testinputx, testinputy;
integer i;
serial_adder ut(.ain(a), .bin(b), .clk(clk), .start(start),
.resetn(resetn),.sum(sum),
.done(done), .c(c));
initial
begin
//giving starting default values
a=0; b=0; start=1; clk=0;
//setting teh module at reset.
resetn=1; #1; resetn=0; #1; resetn=1;
//input values for x and y, from left to right.
testinputx = 8'b01010110;
testinputy = 8'b10110010;
//cyclic inputs x and y transversing the above values.
for( i=7; i>=0; i=i-1)begin
a = testinputx[i];
b = testinputy[i];
clk =1; #20;
clk =0; #20;
end
//additional cycles for computing the adder result.
for( i=7; i>=0; i=i-1)begin
clk =1; #20;
clk =0; #20;
end
end
endmodule

```

Device Utilization Statistics:


Flow summary:

| Flow Summary | |
|---------------------------------|---|
| <<Filter>> | |
| Flow Status | Successful - Thu Feb 17 04:03:01 2022 |
| Quartus Prime Version | 21.1.0 Build 842 10/21/2021 SJ Lite Edition |
| Revision Name | serial_adder |
| Top-level Entity Name | serial_adder |
| Family | Cyclone V |
| Device | 5CSEMA5F31C6 |
| Timing Models | Final |
| Logic utilization (in ALMs) | 10 / 32,070 (< 1 %) |
| Total registers | 33 |
| Total pins | 15 / 457 (3 %) |
| Total virtual pins | 0 |
| Total block memory bits | 0 / 4,065,280 (0 %) |
| Total DSP Blocks | 0 / 87 (0 %) |
| Total HSSI RX PCSs | 0 |
| Total HSSI PMA RX Deserializers | 0 |
| Total HSSI TX PCSs | 0 |
| Total HSSI PMA TX Serializers | 0 |
| Total PLLs | 0 / 6 (0 %) |
| Total DLLs | 0 / 4 (0 %) |

Resource usage summary:

| Compilation Report - serial_adder ✕ | | |
|---|---|-----------|
| Analysis & Synthesis Resource Usage Summary | | |
| <<Filter>> | | |
| | Resource | Usage |
| 1 | Estimate of Logic utilization (ALMs needed) | 16 |
| 2 | | |
| 3 | ▼ Combinational ALUT usage for logic | 8 |
| 1 | -- 7 input functions | 0 |
| 2 | -- 6 input functions | 0 |
| 3 | -- 5 input functions | 4 |
| 4 | -- 4 input functions | 1 |
| 5 | -- <=3 input functions | 3 |
| 4 | | |
| 5 | Dedicated logic registers | 31 |
| 6 | | |
| 7 | I/O pins | 15 |
| 8 | | |
| 9 | Total DSP Blocks | 0 |
| 10 | | |
| 11 | Maximum fan-out node | clk~input |
| 12 | Maximum fan-out | 31 |
| 13 | Total fan-out | 175 |
| 14 | Average fan-out | 2.54 |

Block Diagram (Technology map viewer):

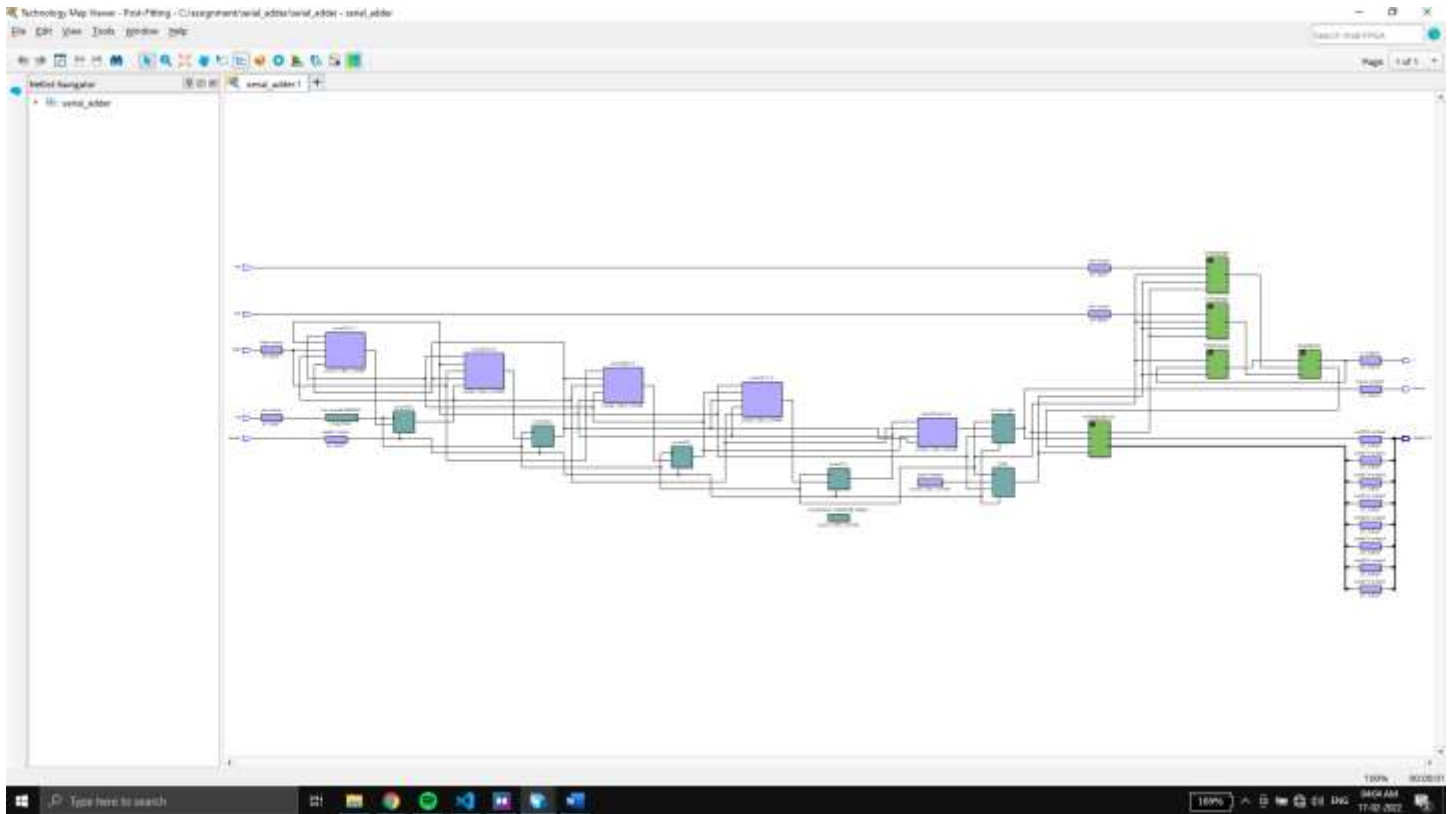

Timing reports:

serial_adder.v X testbench2.v X Compilation Report - serial_adder X

Table of Contents

- Connectivity Checks
- Post-Synthesis Netlist Statistics
- Elapsed Time Per Partition
- Messages
- Fitter
- Assembler
- Timing Analyzer
 - Summary
 - Parallel Compilation
 - Clocks

Clocks

<<Filter>>

| | Clock Name | Type | Period | Frequency | Rise | Fall | Duty |
|---|------------|------|--------|------------|-------|-------|------|
| 1 | clk | Base | 1.000 | 1000.0 MHz | 0.000 | 0.500 | |

Multicorner Timing Analysis Summary

<<Filter>>

| | Clock | Setup | Hold | Recovery | Removal | Minimum Pulse Width |
|---|------------------|---------|-------|----------|---------|---------------------|
| 1 | Worst-case Slack | -0.761 | 0.112 | -0.320 | 0.402 | -0.394 |
| 1 | clk | -0.761 | 0.112 | -0.320 | 0.402 | -0.394 |
| 2 | Design-wide TNS | -19.735 | 0.0 | -0.32 | 0.0 | -19.044 |
| 1 | clk | -19.735 | 0.000 | -0.320 | 0.000 | -19.044 |

For slow 85C model:

| | | | |
|---|------------|-----------------|---------------|
| serial_adder.v X testbench2.v X Compilation Report - serial_adder X | | | |
| Table of Contents | | | |
| Parallel Compilation | | | |
| Clocks | | | |
| Slow 1100mV 85C Model | | | |
| Fmax Summary | | | |
| Slow 1100mV 85C Model Fmax Summary | | | |
| <<Filter>> | | | |
| | Fmax | Restricted Fmax | Clock Name |
| 1 | 567.86 MHz | 567.86 MHz | clk |
| Slow 1100mV 85C Model Setup Summary | | | |
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | -0.761 | -19.735 |
| Slow 1100mV 85C Model Hold Summary | | | |
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.204 | 0.000 |
| Slow 1100mV 85C Model Recovery Summary | | | |
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | -0.320 | -0.320 |
| Slow 1100mV 85C Model Removal Summary | | | |
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.779 | 0.000 |
| Slow 1100mV 85C Model Minimum Pulse Width Summary | | | |
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | -0.394 | -17.578 |

For slow 0C model:

| | | | | |
|--|------------|-----------------|---------------|------|
| Slow 1100mV 0C Model Fmax Summary | | | | |
| <<Filter>> | | | | |
| | Fmax | Restricted Fmax | Clock Name | Note |
| 1 | 589.97 MHz | 589.97 MHz | clk | |
| Slow 1100mV 0C Model Setup Summary | | | | |
| <<Filter>> | | | | |
| | Clock | Slack | End Point TNS | |
| 1 | clk | -0.695 | -18.194 | |
| Slow 1100mV 0C Model Hold Summary | | | | |
| <<Filter>> | | | | |
| | Clock | Slack | End Point TNS | |
| 1 | clk | 0.191 | 0.000 | |
| Slow 1100mV 0C Model Recovery Summary | | | | |
| <<Filter>> | | | | |
| | Clock | Slack | End Point TNS | |
| 1 | clk | -0.261 | -0.261 | |
| Slow 1100mV 0C Model Removal Summary | | | | |
| <<Filter>> | | | | |
| | Clock | Slack | End Point TNS | |
| 1 | clk | 0.723 | 0.000 | |
| Slow 1100mV 0C Model Minimum Pulse Width Summary | | | | |
| <<Filter>> | | | | |
| | Clock | Slack | End Point TNS | |
| 1 | clk | -0.394 | -19.044 | |

For fast 85C model:

| Fast 1100mV 85C Model Setup Summary | | | |
|-------------------------------------|-------|-------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.043 | 0.000 |

| Fast 1100mV 85C Model Hold Summary | | | |
|------------------------------------|-------|-------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.124 | 0.000 |

| Fast 1100mV 85C Model Recovery Summary | | | |
|--|-------|-------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.239 | 0.000 |

| Fast 1100mV 85C Model Removal Summary | | | |
|---------------------------------------|-------|-------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.447 | 0.000 |

| Fast 1100mV 85C Model Minimum Pulse Width Summary | | | |
|---|-------|--------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | -0.084 | -2.718 |

For slow 0C model:

| Fast 1100mV 0C Model Setup Summary | | | |
|------------------------------------|-------|-------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.108 | 0.000 |


| Fast 1100mV 0C Model Hold Summary | | | |
|-----------------------------------|-------|-------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.112 | 0.000 |

| Fast 1100mV 0C Model Recovery Summary | | | |
|---------------------------------------|-------|-------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.296 | 0.000 |


| Fast 1100mV 0C Model Removal Summary | | | |
|--------------------------------------|-------|-------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | 0.402 | 0.000 |

| Fast 1100mV 0C Model Minimum Pulse Width Summary | | | |
|--|-------|--------|---------------|
| <<Filter>> | | | |
| | Clock | Slack | End Point TNS |
| 1 | clk | -0.083 | -2.669 |

Simulation in Questa through Quartus:

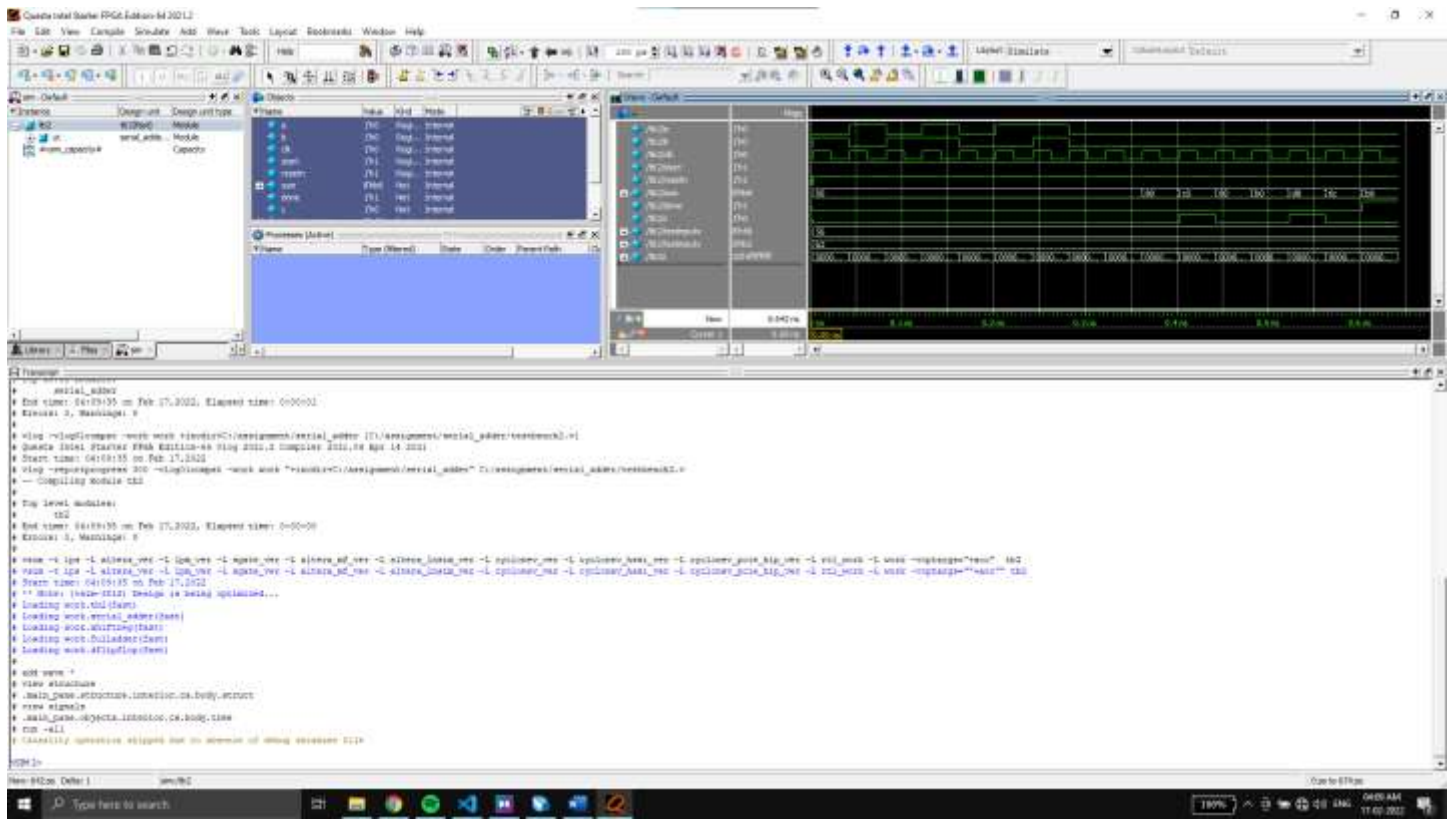

Wave:

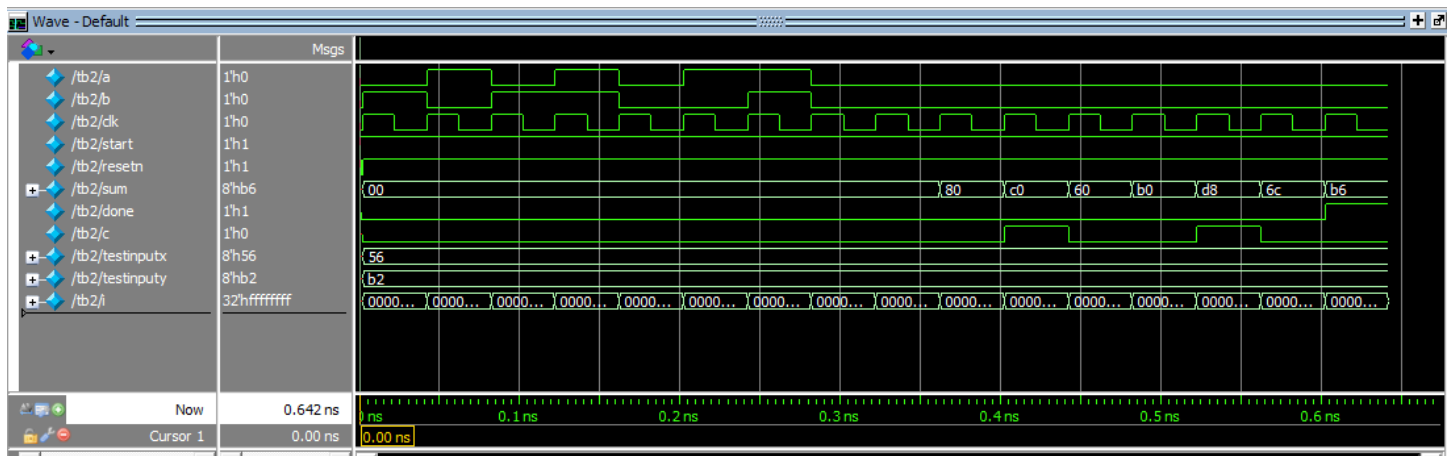

4. Shift and add multiplier in Verilog to multiply two 8 bit numbers using RTL approach. It should be capable of multiplying both positive and negative numbers. Negative numbers are represented in 2'sC representation.

Storing the input values in 8 bit registers A and B we will display the output using a 16bit Register P.

we know that for signed multiplication when multiplicand is negative we need to ignore carry and use 1 as the msb's while adding to the register P when the multiplier bit is 1 while when multiplier is negative we just need to add two's complement in the last step.

We will use 10 states from s0 to s9 indicating value 0 to 9 respectively.

We will make our system positively edge activated with asynchronous reset.

On each state we will be storing the left shifted value of A_q in A_d storing the right shifted value of B_q in B_d.

On each shift to positive edge of the clk(clock), we will update the output pdt_q with the calculated next_output from the 2nd always block according to the method discussed above. We will also updating the shifted values in the A_q and B_q (from A_d and B_d respectively) at that time.

Verilog Code for the Shift and add multiplier:

```
module shift_multiply(input clk, resetn, start, input [7:0]A, B, output
[15:0] P, output reg done);
localparam S0=0, S1=1, S2=2, S3=3, S4=4, S5=5, S6=6, S7=7, S8=8, S9=9;
reg [4:0] state_d, state_q;
reg [7:0] B_d, B_q;
reg [15:0] A_d, A_q, pdt_d, pdt_q;
assign P = pdt_q;
always @ (posedge clk , negedge resetn)
begin
    if(!resetn) state_q <=S0;
    else begin
        state_q <= state_d;
        pdt_q <=pdt_d;
        A_q <= A_d;
        B_q <= B_d;
    end
end

always @(state_q) begin
    state_d = state_q;
    done = 1'b0;
```

```

    case(state_q)
        S0:if(start) state_d=S1;
        S1: state_d=S2;
        S2: state_d=S3;
        S3: state_d=S4;
        S4: state_d=S5;
        S5: state_d=S6;
        S6: state_d=S7;
        S7: state_d=S8;
        S8: state_d=S9;
        S9: begin
            done= 1'b1;
            if(start)state_d =S1;
            end
        default: state_d=S0;
    endcase
end

always @(state_q or pdt_q or A_q or B_q)
begin
    pdt_d = pdt_q; A_d = A_q; B_d = B_q;
    case (state_q)
        S0: begin
            pdt_d = {16{1'b0}};
            A_d = A;
            B_d = B;
        end
        S1: begin
            A_d = A_q << 1;
            B_d = B_q >> 1;
            if (B_q[0] == 1'b1) begin
                if(A[7] == 1'b1) pdt_d = {8'b11111111,A_q[7:0]} +pdt_q;
                else pdt_d = A_q + pdt_q;
            end
        end
        S2: begin
            A_d = A_q << 1;
            B_d = B_q >> 1;
            if (B_q[0] == 1'b1) begin
                if(A[7] == 1'b1) pdt_d = {7'b1111111,A_q[8:1], 1'b0} +pdt_q;
                else pdt_d = A_q + pdt_q;
            end
        end
        S3: begin
            A_d = A_q << 1;
            B_d = B_q >> 1;
            if (B_q[0] == 1'b1) begin
                if(A[7] == 1'b1) pdt_d = {6'b111111,A_q[9:2], 2'b00} +pdt_q;
                else pdt_d = A_q + pdt_q;
            end
        end
    endcase
end

```

```

end
S4: begin
A_d = A_q << 1;
B_d = B_q >> 1;
if (B_q[0] == 1'b1) begin
    if(A[7] == 1'b1) pdt_d = {5'b11111,A_q[10:3], 3'b000} +pdt_q;
    else pdt_d = A_q + pdt_q;
end
end
S5: begin
A_d = A_q << 1;
B_d = B_q >> 1;
if (B_q[0] == 1'b1) begin
    if(A[7] == 1'b1) pdt_d = {4'b1111,A_q[11:4], 4'b0000} +pdt_q;
    else pdt_d = A_q + pdt_q;
end
end
S6: begin
A_d = A_q << 1;
B_d = B_q >> 1;
if (B_q[0] == 1'b1) begin
    if(A[7] == 1'b1) pdt_d = {3'b111,A_q[12:5], 5'b00000} +pdt_q;
    else pdt_d = A_q + pdt_q;
end
end
S7: begin
A_d = A_q << 1;
B_d = B_q >> 1;
if (B_q[0] == 1'b1) begin
    if(A[7] == 1'b1) pdt_d = {2'b11,A_q[13:6], 6'b000000} +pdt_q;
    else pdt_d = A_q + pdt_q;
end
end
S8: begin
A_d = A_q << 1;
B_d = B_q >> 1;
if (B_q[0] == 1'b1) begin
    if(B[3] == 1'b1) pdt_d = {1'b0, (~A+1'b1),7'b0000000} +pdt_q;
    else if(A[3] == 1'b1) pdt_d = {1'b1,A_q[15:8], 7'b0000000} +pdt_q;
    else pdt_d = A_q + pdt_q;
end
end
default: pdt_d = pdt_q;
endcase
end
endmodule

```

Verilog code for the test bench:



```

module test_bench();
reg clk, resetn, start;
reg [7:0] A, B;
wire [15:0] P;
wire done;
integer i;
shift_multiply ut(.clk(clk), .resetn(resetn), .start(start), .A(A), .B(B),
.P(P), .done(done));
initial
begin
    clk=0;resetn=0;
    #2; clk=1;
    A=8'b00101011; B= 8'b01001101;
    #2 resetn=1; clk=0; start=1'b1;
    for(i=0; i<=9;i=i+1) begin
        #20 clk =1; #20 clk=0;
    end
end
endmodule

```

Device Utilization Statistics:


Flow summary:

| X  Compilation Report - shift_multiply X | |
|---|---|
| Flow Summary | |
|  <<Filter>> | |
| Flow Status | Successful - Thu Feb 17 04:16:33 2022 |
| Quartus Prime Version | 21.1.0 Build 842 10/21/2021 SJ Lite Edition |
| Revision Name | shift_multiply |
| Top-level Entity Name | shift_multiply |
| Family | Cyclone V |
| Device | 5CSEMA5F31C6 |
| Timing Models | Final |
| Logic utilization (in ALMs) | 160 / 32,070 (< 1 %) |
| Total registers | 51 |
| Total pins | 36 / 457 (8 %) |
| Total virtual pins | 0 |
| Total block memory bits | 0 / 4,065,280 (0 %) |
| Total DSP Blocks | 0 / 87 (0 %) |
| Total HSSI RX PCSs | 0 |
| Total HSSI PMA RX Deserializers | 0 |
| Total HSSI TX PCSs | 0 |
| Total HSSI PMA TX Serializers | 0 |
| Total PLLs | 0 / 6 (0 %) |
| Total DLLs | 0 / 4 (0 %) |

Resource usage summary:

| Compilation Report - shift_multiply | | |
|---|---|-----------|
| Analysis & Synthesis Resource Usage Summary | | |
| <<Filter>> | | |
| | Resource | Usage |
| 1 | Estimate of Logic utilization (ALMs needed) | 159 |
| 2 | | |
| 3 | ▼ Combinational ALUT usage for logic | 251 |
| 1 | -- 7 input functions | 0 |
| 2 | -- 6 input functions | 52 |
| 3 | -- 5 input functions | 21 |
| 4 | -- 4 input functions | 19 |
| 5 | -- <=3 input functions | 159 |
| 4 | | |
| 5 | Dedicated logic registers | 50 |
| 6 | | |
| 7 | I/O pins | 36 |
| 8 | | |
| 9 | Total DSP Blocks | 0 |
| 10 | | |
| 11 | Maximum fan-out node | clk~input |
| 12 | Maximum fan-out | 50 |
| 13 | Total fan-out | 1124 |
| 14 | Average fan-out | 3.01 |

Block Diagram (Technology map viewer):

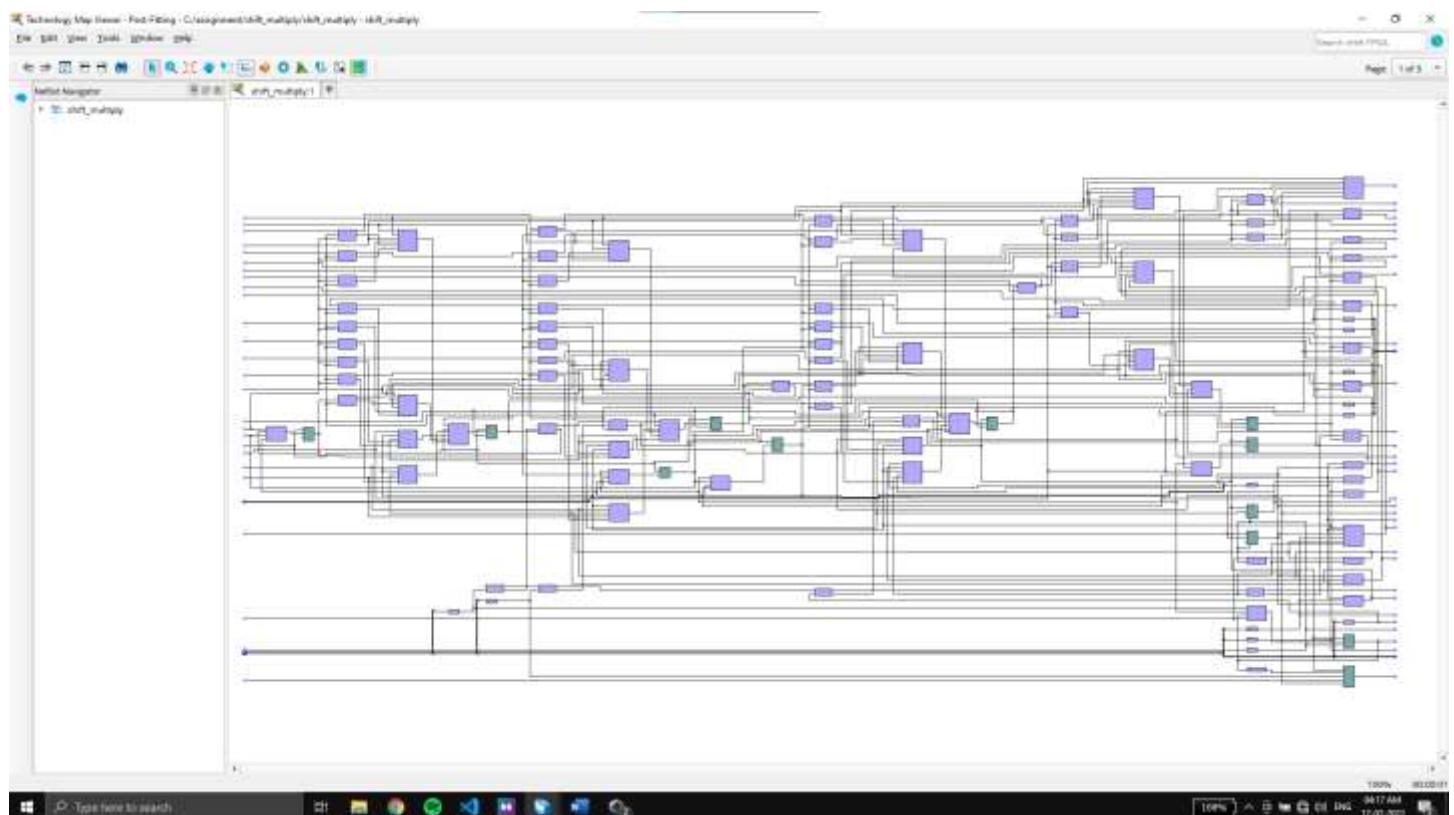

Timing reports:

| Compilation Report - shift_multiply | | | | | | |
|-------------------------------------|------------|------|--------|------------|-------|-------|
| Clocks | | | | | | |
| <<Filter>> | | | | | | |
| | Clock Name | Type | Period | Frequency | Rise | Fall |
| 1 | clk | Base | 1.000 | 1000.0 MHz | 0.000 | 0.500 |

For slow 85C model:

abc shift_multiply.v X

abc test_bench.v X

Compilation Report - shift_multiply X

Table of Contents

Parallel Compilation

Clocks

Slow 1100mV 85C Model

Fmax Summary

Slow 1100mV 85C Model Setup Summary

<<Filter>>

| | Clock | Slack | End Point TNS |
|---|-------|--------|---------------|
| 1 | clk | -3.631 | -99.885 |

Slow 1100mV 85C Model Minimum Pulse Width Summary

<<Filter>>

| | Clock | Slack | End Point TNS |
|---|-------|--------|---------------|
| 1 | clk | -0.394 | -26.960 |

Slow 1100mV 85C Model Fmax Summary

<<Filter>>

| | Fmax | Restricted Fmax | Clock Name | Note |
|---|------------|-----------------|------------|------|
| 1 | 215.94 MHz | 215.94 MHz | clk | |

Slow 1100mV 85C Model Hold Summary

<<Filter>>


| | Clock | Slack | End Point TNS |
|---|-------|-------|---------------|
| 1 | clk | 0.349 | 0.000 |

For slow 0C model:

| Slow 1100mV 0C Model Fmax Summary | | | | | Slow 1100mV 0C Model Setup Summary | | | |
|-----------------------------------|------------|-----------------|---------------|------|--|-------|--------|---------------|
| <<Filter>> | | | | | <<Filter>> | | | |
| | Fmax | Restricted Fmax | Clock Name | Note | | Clock | Slack | End Point TNS |
| 1 | 219.15 MHz | 219.15 MHz | clk | | 1 | clk | -3.563 | -98.060 |
| Slow 1100mV 0C Model Hold Summary | | | | | Slow 1100mV 0C Model Minimum Pulse Width Summary | | | |
| <<Filter>> | | | | | <<Filter>> | | | |
| | Clock | Slack | End Point TNS | | | Clock | Slack | End Point TNS |
| 1 | clk | 0.331 | 0.000 | | 1 | clk | -0.394 | -28.695 |

For fast 85C model:

Wave:

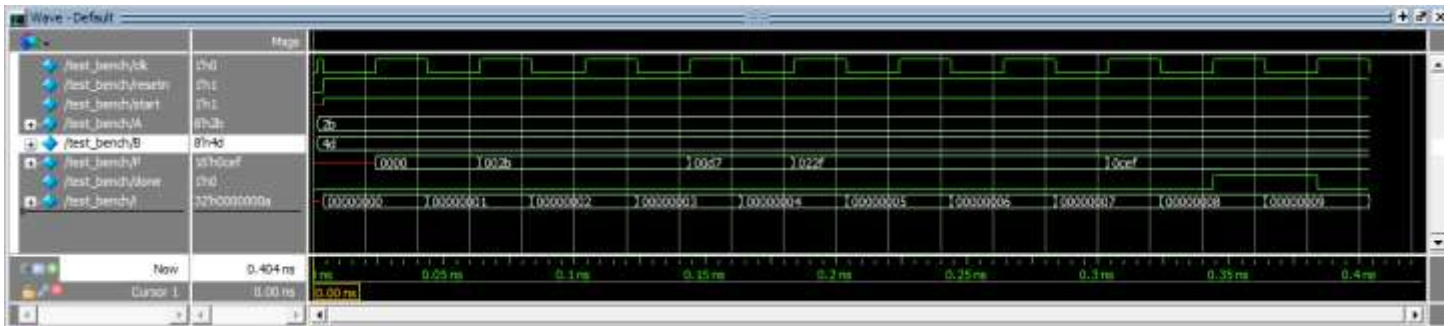

5. To compute the factorial of a 3-bit number using RTL approach.

->

To design a system which calculates factorial of up to 3-bit numbers.

We will consider a 3bit input **a**, of which the factorial has to be computed and it will be displayed on the 13 bits output **out**.

We will consider an FSM with **8 states** with positive edge activated clock and asynchronous reset **resetn**.

In states 0 to 6, we will be multiplying the output with corresponding state value, and storing it in **out_next**.

On switch from negative edge to positive edge of the clock, **out_next** value will get stored in the output register **out**.

On reset, the output will revert to 0 and state to 0.

On completion of necessary factorial calculation, a condition will be met (**count<=state+1**) which will switch the state to **7** at which it will be stuck forever showing the required factorial and a **done** output bit will turn to 1 to indicate the completion of it.

The count register stores the value of input a.

We will assume that the input isn't 0.

Verilog Code for the Factorial calculator:

```
module factorial (input [2:0]a, input clock, resetn, output reg [12:0] out,
output reg done);
reg [3:0] state, next_state;
reg [2:0] count;
reg [12:0] out_next;

always @(posedge clock, negedge resetn)
begin
    if(!resetn) begin out <=1;state<=0; end
    else begin
        state <= next_state;
        out <= out_next;
    end
end

always @ (state) begin
    count <=a;
    case(state)
    0: begin
        if(count<=state+1) begin next_state <= 7; end
        else begin next_state <= 1;
        done <=0;
        out_next <= 1*out;
        end
    end
    1: begin
        if(count<=state+1) begin next_state <= 7; end
        else begin next_state <= 2;
        end
        done <=0;
        out_next <= 2*out;
    end
    2: begin
        if(count<=state+1) begin next_state <= 7; end
        else begin next_state <= 3;
        end
        done <=0;
        out_next <= 3*out;
    end
    3: begin
        if(count<=state+1) begin next_state <= 7; end
        else begin next_state <= 4;
        end
        done <=0;
        out_next <= 4*out;
    end
    4: begin
```

```

        if(count<=state+1) begin next_state <= 7; end
        else begin next_state <= 5;
        end
        done <=0;
        out_next <= 5*out;
    end
5: begin
    if(count<=state+1) begin next_state <= 7; end
    else begin next_state <= 6;
    end
    done <=0;
    out_next <= 6*out;
end
6: begin
    if(count<=state+1) begin next_state <= 7; end
    else begin next_state <= 7;
    end
    done <=0;
    out_next <= 7*out;
end
7: begin
    next_state <= 7;
    done <=1;
end
endcase
end
endmodule

```

Verilog code for the test bench:

```

module testbench();
reg [2:0] a;
reg clock, resetn;
wire [12:0] out;
wire done;
integer i;
factorial faccalc(a, clock, resetn, out, done);
initial begin
a=5;
resetn=1; clock =1;
#5 resetn=0; #5 resetn=1;
for(i=0; i<10; i=i+1)begin
    clock=1;#50; clock=0; #50;
end
end
endmodule


```

Device Utilization Statistics:

Flow summary:

| | |
|----------------------------------|---|
| Compilation Report - factorial X | |
| Flow Summary | |
| <<Filter>> | |
| Flow Status | Successful - Thu Feb 17 04:36:27 2022 |
| Quartus Prime Version | 21.1.0 Build 842 10/21/2021 SJ Lite Edition |
| Revision Name | factorial |
| Top-level Entity Name | factorial |
| Family | Cyclone V |
| Device | 5CSEMA5F31C6 |
| Timing Models | Final |
| Logic utilization (in ALMs) | 55 / 32,070 (< 1 %) |
| Total registers | 16 |
| Total pins | 19 / 457 (4 %) |
| Total virtual pins | 0 |
| Total block memory bits | 0 / 4,065,280 (0 %) |
| Total DSP Blocks | 0 / 87 (0 %) |
| Total HSSI RX PCSs | 0 |
| Total HSSI PMA RX Deserializers | 0 |
| Total HSSI TX PCSs | 0 |
| Total HSSI PMA TX Serializers | 0 |
| Total PLLs | 0 / 6 (0 %) |
| Total DLLs | 0 / 4 (0 %) |


Resource usage summary:



Compilation Report - factorial

X


Analysis & Synthesis Resource Usage Summary



<<Filter>>

| | Resource | Usage |
|----|---|----------|
| 1 | Estimate of Logic utilization (ALMs needed) | 55 |
| 2 | | |
| 3 | ▼ Combinational ALUT usage for logic | 83 |
| 1 | -- 7 input functions | 1 |
| 2 | -- 6 input functions | 25 |
| 3 | -- 5 input functions | 3 |
| 4 | -- 4 input functions | 0 |
| 5 | -- <=3 input functions | 54 |
| 4 | | |
| 5 | Dedicated logic registers | 16 |
| 6 | | |
| 7 | I/O pins | 19 |
| 8 | | |
| 9 | Total DSP Blocks | 0 |
| 10 | | |
| 11 | Maximum fan-out node | state[1] |
| 12 | Maximum fan-out | 21 |
| 13 | Total fan-out | 406 |
| 14 | Average fan-out | 2.96 |

Block Diagram (Technology map viewer):

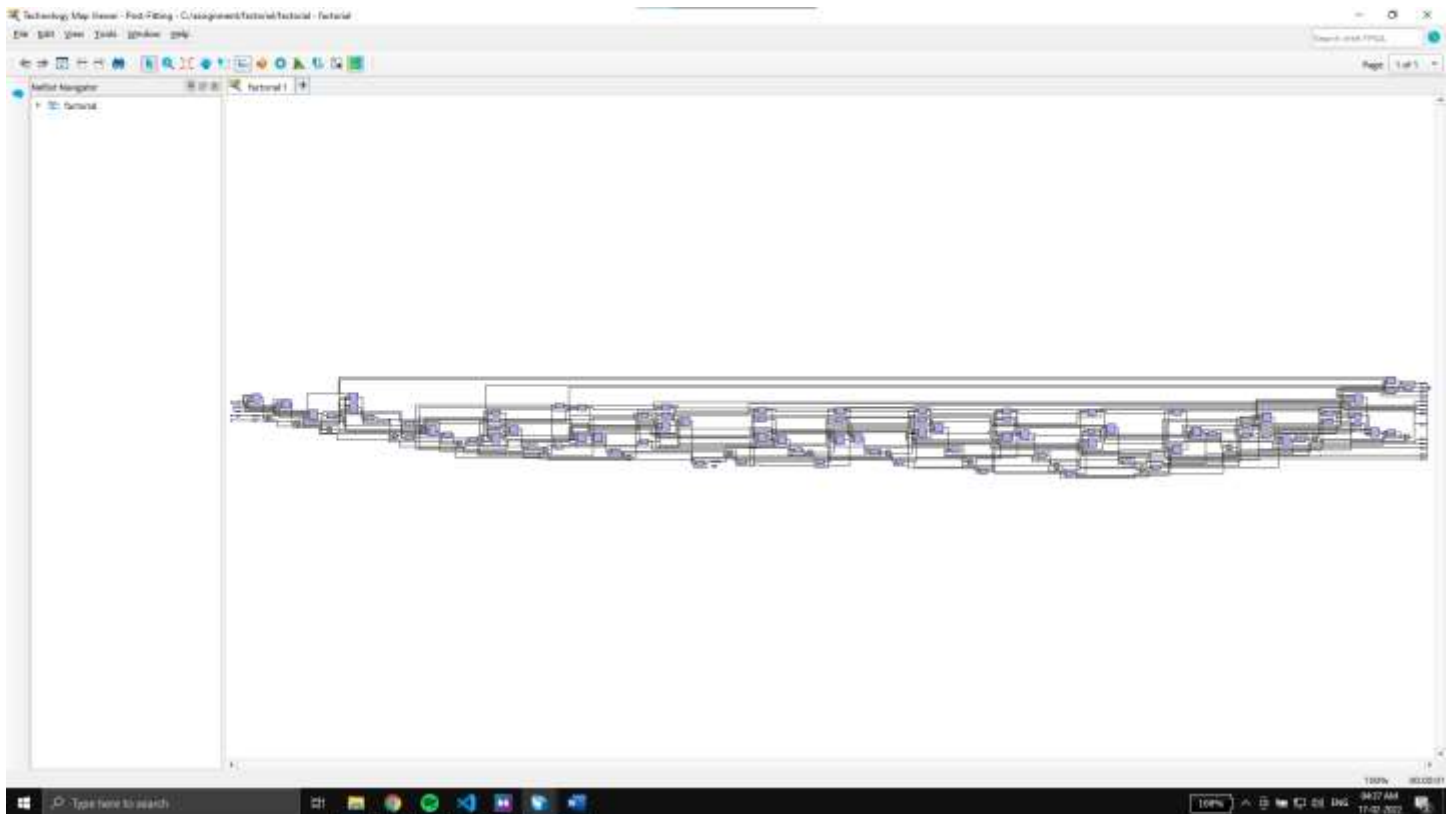

Timing reports:

| Compilation Report - factorial X | | | | | | |
|----------------------------------|------------|------|--------|------------|-------|-------|
| Clocks | | | | | | |
| <<Filter>> | | | | | | |
| | Clock Name | Type | Period | Frequency | Rise | Fall |
| 1 | a[1] | Base | 1.000 | 1000.0 MHz | 0.000 | 0.500 |
| 2 | clock | Base | 1.000 | 1000.0 MHz | 0.000 | 0.500 |

| Compilation Report - factorial X | | | | | | |
|-------------------------------------|--------------------|---------|--------|----------|---------|---------------------|
| Multicorner Timing Analysis Summary | | | | | | |
| <<Filter>> | | | | | | |
| | Clock | Setup | Hold | Recovery | Removal | Minimum Pulse Width |
| 1 | ▼ Worst-case Slack | -5.008 | -0.421 | N/A | N/A | -0.394 |
| 1 | a[1] | -5.008 | 0.415 | N/A | N/A | -0.077 |
| 2 | clock | -2.391 | -0.421 | N/A | N/A | -0.394 |
| 2 | ▼ Design-wide TNS | -82.814 | -1.467 | 0.0 | 0.0 | -9.1 |
| 1 | a[1] | -63.294 | 0.000 | N/A | N/A | -1.151 |
| 2 | clock | -21.349 | -1.467 | N/A | N/A | -9.100 |

For slow 85C model:

| | | | | | | | | |
|------------------------------------|------------|-----------------|---------------|-----------|---|-------|--------|---------------|
| Compilation Report - factorial X | | | | | Slow 1100mV 85C Model Setup Summary | | | |
| Slow 1100mV 85C Model Fmax Summary | | | | | <<Filter>> | | | |
| | Fmax | Restricted Fmax | Clock Name | Note | | Clock | Slack | End Point TNS |
| 1 | 798.08 MHz | 717.36 MHz | clock | lim...in) | 1 | a[1] | -4.898 | -61.465 |
| | | | | | 2 | clock | -2.391 | -21.349 |
| Slow 1100mV 85C Model Hold Summary | | | | | Slow 1100mV 85C Model Minimum Pulse Width Summary | | | |
| <<Filter>> | | | | | <<Filter>> | | | |
| | Clock | Slack | End Point TNS | | | Clock | Slack | End Point TNS |
| 1 | clock | -0.299 | -0.733 | | 1 | clock | -0.394 | -8.382 |
| 2 | a[1] | 1.068 | 0.000 | | 2 | a[1] | 0.161 | 0.000 |

For slow OC model:

| | | | | | | | | |
|-----------------------------------|-----------|-----------------|---------------|-----------|--|-------|--------|---------------|
| Slow 1100mV OC Model Fmax Summary | | | | | Slow 1100mV OC Model Setup Summary | | | |
| <<Filter>> | | | | | <<Filter>> | | | |
| | Fmax | Restricted Fmax | Clock Name | Note | | Clock | Slack | End Point TNS |
| 1 | 771.6 MHz | 717.36 MHz | clock | lim...in) | 1 | a[1] | -5.008 | -63.294 |
| | | | | | 2 | clock | -2.147 | -19.478 |
| Slow 1100mV OC Model Hold Summary | | | | | Slow 1100mV OC Model Minimum Pulse Width Summary | | | |
| <<Filter>> | | | | | <<Filter>> | | | |
| | Clock | Slack | End Point TNS | | | Clock | Slack | End Point TNS |
| 1 | clock | -0.421 | -1.467 | | 1 | clock | -0.394 | -9.100 |
| 2 | a[1] | 1.094 | 0.000 | | 2 | a[1] | 0.135 | 0.000 |

For fast 85C model:

| | | | | | | | |
|---|-------|--------|---------------|------------------------------------|-------|-------|---------------|
| Fast 1100mV 85C Model Setup Summary | | | | Fast 1100mV 85C Model Hold Summary | | | |
| <<Filter>> | | | | <<Filter>> | | | |
| | Clock | Slack | End Point TNS | | Clock | Slack | End Point TNS |
| 1 | a[1] | -2.208 | -26.817 | 1 | clock | 0.181 | 0.000 |
| 2 | clock | -2.006 | -16.764 | 2 | a[1] | 0.437 | 0.000 |
| Fast 1100mV 85C Model Minimum Pulse Width Summary | | | | | | | |
| <<Filter>> | | | | | | | |
| | Clock | Slack | End Point TNS | | | | |
| 1 | clock | -0.081 | -1.252 | | | | |
| 2 | a[1] | -0.077 | -1.151 | | | | |

For fast OC model:

