 


EC204

Digital System Design Lab

Lab – 7



Utkarsh R Mahajan
201EC164

1] **Decade Counter** - Model a synchronous up/down decade counter with asynchronous reset. The counter is rising edge triggered.

If the **load** = 1, the data **data_in** is loaded into the counter.

If the **counter_on=counter_up=1**, the counter is incremented, the Terminal carry output **TC=1** when the counter is in state 9.

If the **counter_on=1** and **counter_up=0**, the counter is decremented, the Terminal carry output **TC=1** when the counter is in state 0.


-> Verilog code for the counter:

```
module decadeCounter(input counter_up,
input load,
input resetn,
input counter_on,
input clk,
input [3:0] data_in,
output reg [3:0] count,
output reg TC);


always@(negedge resetn, posedge clk)
begin
    if(load) count <= data_in;
    else if(!resetn) begin TC<= 0; count <= 0; end
    else if(counter_on) begin
        if(counter_up) begin
            if(count<9) count <= count + 1;
            else count <= 0;
            if(count==9) TC <=1;
            else TC<=0;
        end else begin
            if(count>0) count <= count - 1;
            else count <= 9;
            if(count==0) TC <=1;
            else TC<=0;
        end
    end
end
endmodule
```

Verilog code for the testbench:

Full Screenshot:

 

Wave:

 

2] Use two decade counter modules to form a two-digit decimal up/down counter.

-> Verilog code for the counter:

```
module twoDigitDecadeCounter(input counter_up,
input load,
input reset,
input counter_on,
input clk,
input [7:0] data_in,
output [7:0] count,
output TC);
wire n1;
decadeCounter cunit(counter_up,
load,
reset,
counter_on,
clk,
data_in[3:0],
count[3:0],
n1);
decadeCounter cdigit(counter_up,
load,
reset,
counter_on,
n1,
data_in[7:4],
count[7:4],
TC);
endmodule
```


Verilog code for the testbench:

```




module testbench_2();
integer i;
reg clk, counter_on, resetn, load, counter_up;
reg [7:0] data_in;
wire [7:0] count;
wire TC;
twoDigitDecadeCounter d1(counter_up,
load, resetn, counter_on,
clk, data_in, count, TC);
initial
begin
    resetn=1;#1; resetn=0; #1; resetn=1;
    load=0; data_in =8'b01001000;
    counter_on=1; counter_up =1;
    for( i=0; i<20; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
    load =1;
    clk =1; #20; clk =0; #20; load =0;
    counter_up =0;
    for( i=0; i<20; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
end
endmodule

```

Full Screenshot:

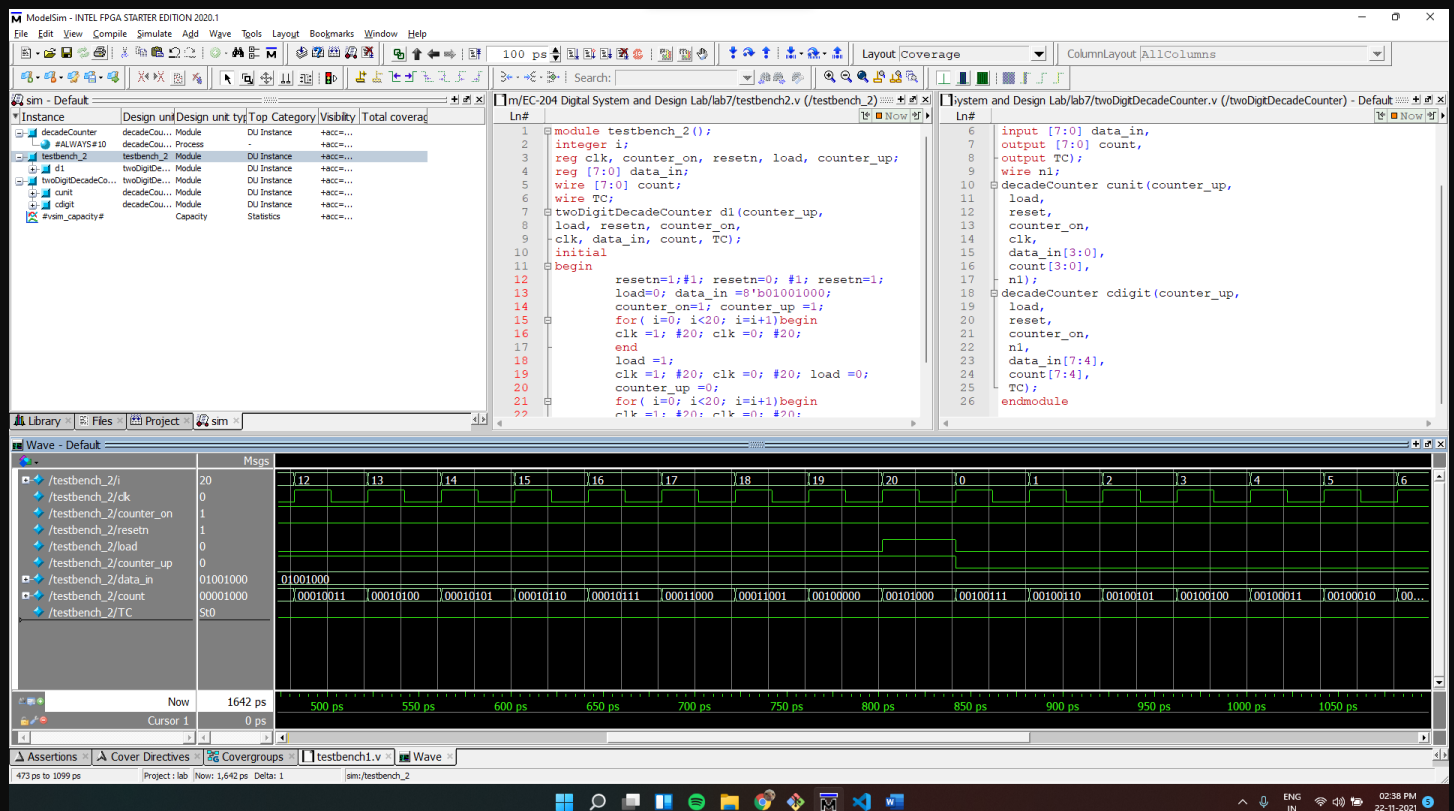

Wave:

   

3] Design an n-bit program counter (PC) that has the following functions:

- It is cleared to 0 when the asynchronous reset is asserted
- It is loaded a new value in parallel when the PCload is asserted
- It is incremented by 1 when the PCinc is asserted

We will consider n as 4 for our working example.

-> Verilog code for the Program counter:

```

module programCounter(reset, clk, PCload, PCinc, load_in, PC);
parameter n=4;
input reset, clk, PCload, PCinc;
input [n-1:0] load_in;
output reg [n-1:0] PC;

always @(negedge reset, posedge clk)
begin
    if(!reset) PC <= 0;
    else if (PCload) PC <= load_in;
    else if(PCinc) PC <= PC+1;
end
endmodule

```


Verilog code for the testbench:

```


module testbench_3();
integer i;
reg resetn, clk, PCload, PCinc;
reg [3:0] load_in;
wire [3:0] PC;
programCounter pc1(resetn, clk, PCload, PCinc, load_in, PC);
initial
begin
    resetn=1;#1; resetn=0; #1; resetn=1;
    PCload=0; load_in =4'b0100;
    PCinc=1;
    for( i=0; i<12; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
    PCload =1;
    clk =1; #20; clk =0; #20; PCload =0;
    for( i=0; i<6; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
end
endmodule

```

Wave:

 

Full Screenshot:

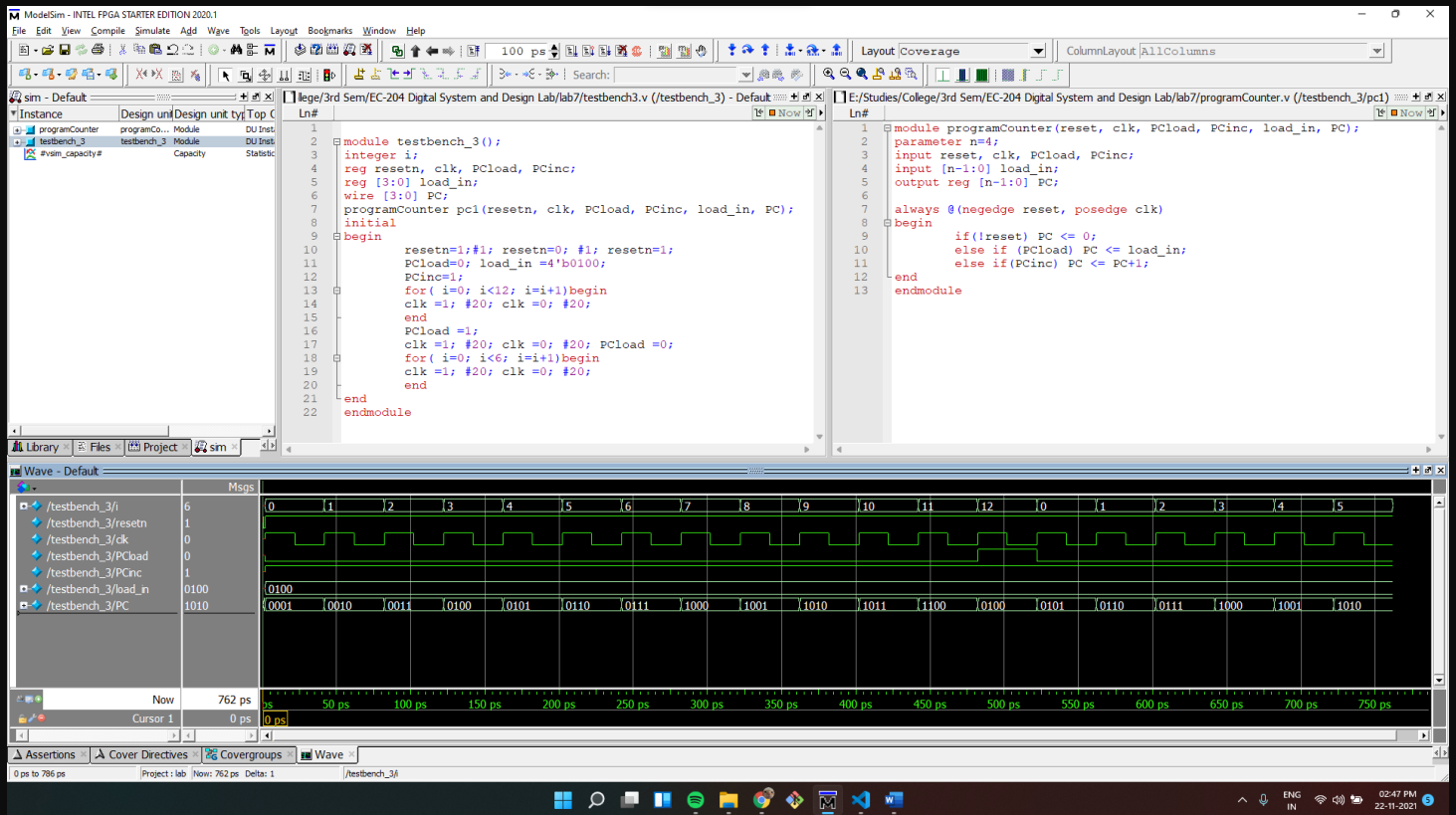

4] Model the functionality of Shift register 74194.

-> Verilog code for the Shift Register:


```
module shiftRegister74194(input MRn, CP, Dsr, Ds1,
    input [1:0]S, input [3:0] P, output reg [3:0] Q);


always@(negedge MRn, posedge CP)
begin
    if(!MRn) Q <= 0;
    else if(S==2'b01) begin
        if(Dsr) Q<= {1'b1, Q[3:1]};
        else Q<= {1'b0, Q[3:1]};
    end else if(S==2'b10) begin
        if(Ds1) Q<= {Q[2:0], 1'b1};
        else Q<= {Q[2:0], 1'b0};
    end else if(S==2'b11) Q <= P;
end
endmodule
```


Verilog code for the testbench:


```
module testbench_4();
integer i;
reg clk, MRn, Dsr, Dsl;
reg [1:0] S;
reg [3:0] P;
wire [3:0] Q;
shiftRegister74194 ut(MRn, clk, Dsr, Dsl,
    S, P, Q);
initial
begin
    MRn=1;#1; MRn=0; #1; MRn=1;
    P =4'b1000;
    S=2'b01;
    Dsr=1; Dsl=1;
    for( i=0; i<10; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
    Dsr=0;
    for( i=0; i<10; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
    S=2'b11;
    clk =1; #20; clk =0; #20; S=2'b10;
    for( i=0; i<10; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
    Dsl=0;
    for( i=0; i<10; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
end
endmodule
```

Wave:

 

 

Full Screenshot:

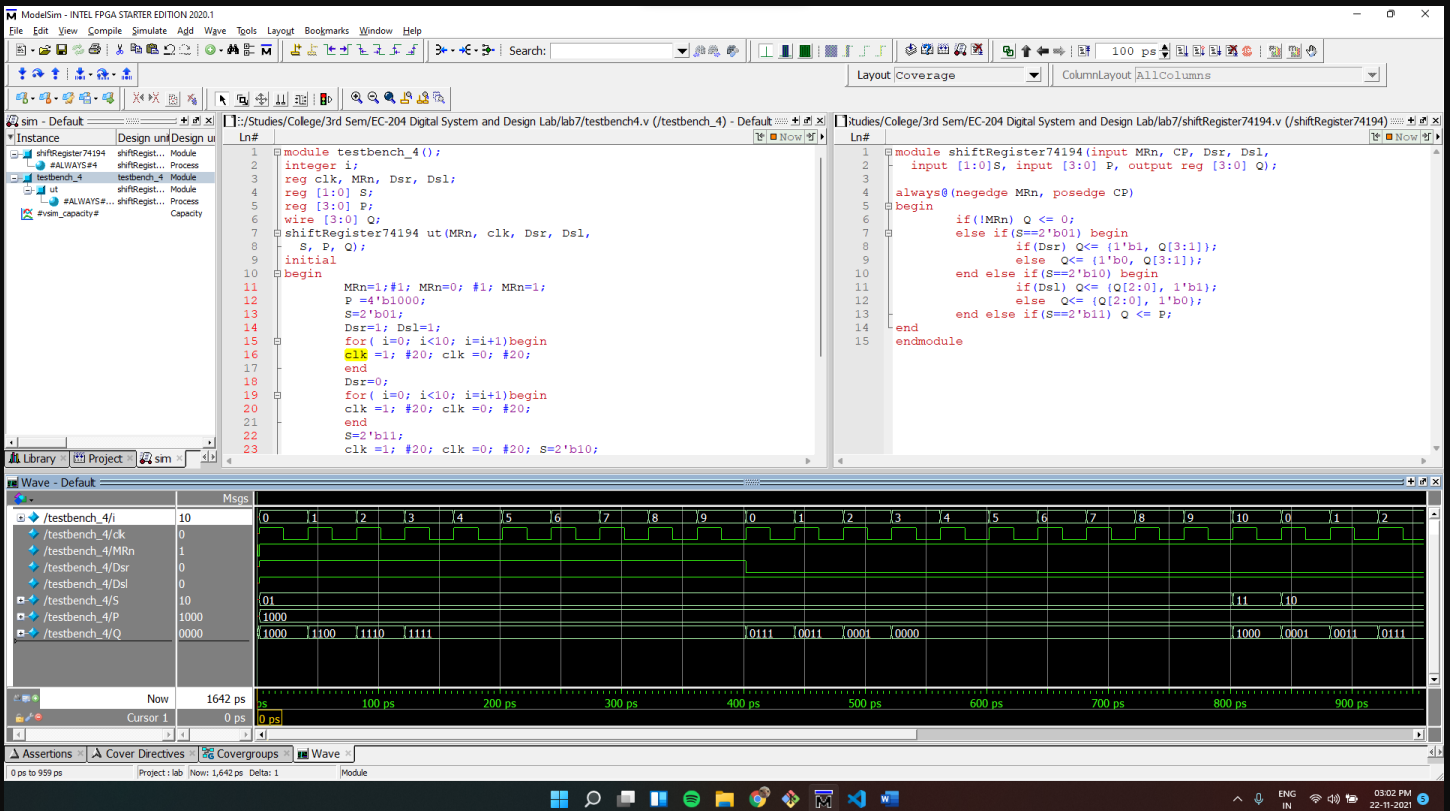

5] Write a Verilog module for a 4 bit self-correcting ring counter.

-> In a self-correcting ring counter, the current state bits resets if they enter a invalid state.

Verilog code for the ring counter:


```
module ringCounterSelfCorrecting(input clk,
    input resethn,
    output reg [3:0] Q);

always @(negedge resethn, posedge clk)
begin
    if(!resethn) Q <= 4'b1000;
    else if(Q==4'b1000 || Q==4'b0100 || Q==4'b0010) Q <= Q >> 1;
    else Q<=4'b1000;
end
endmodule
```


Verilog code for the testbench:

```
module testbench_5();
integer i;
reg resethn, clk;
reg [3:0] load_in;
wire [3:0] Q;
ringCounterSelfCorrecting ut(clk, resethn,Q);
initial
begin
    resethn=1;#1; resethn=0; #1; resethn=1;
    for( i=0; i<12; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
end
endmodule
```

Wave:

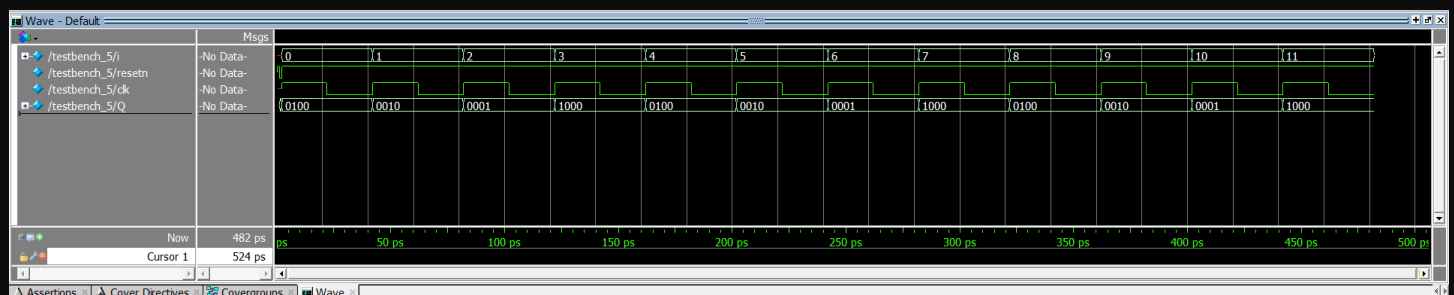

Full Screenshot:

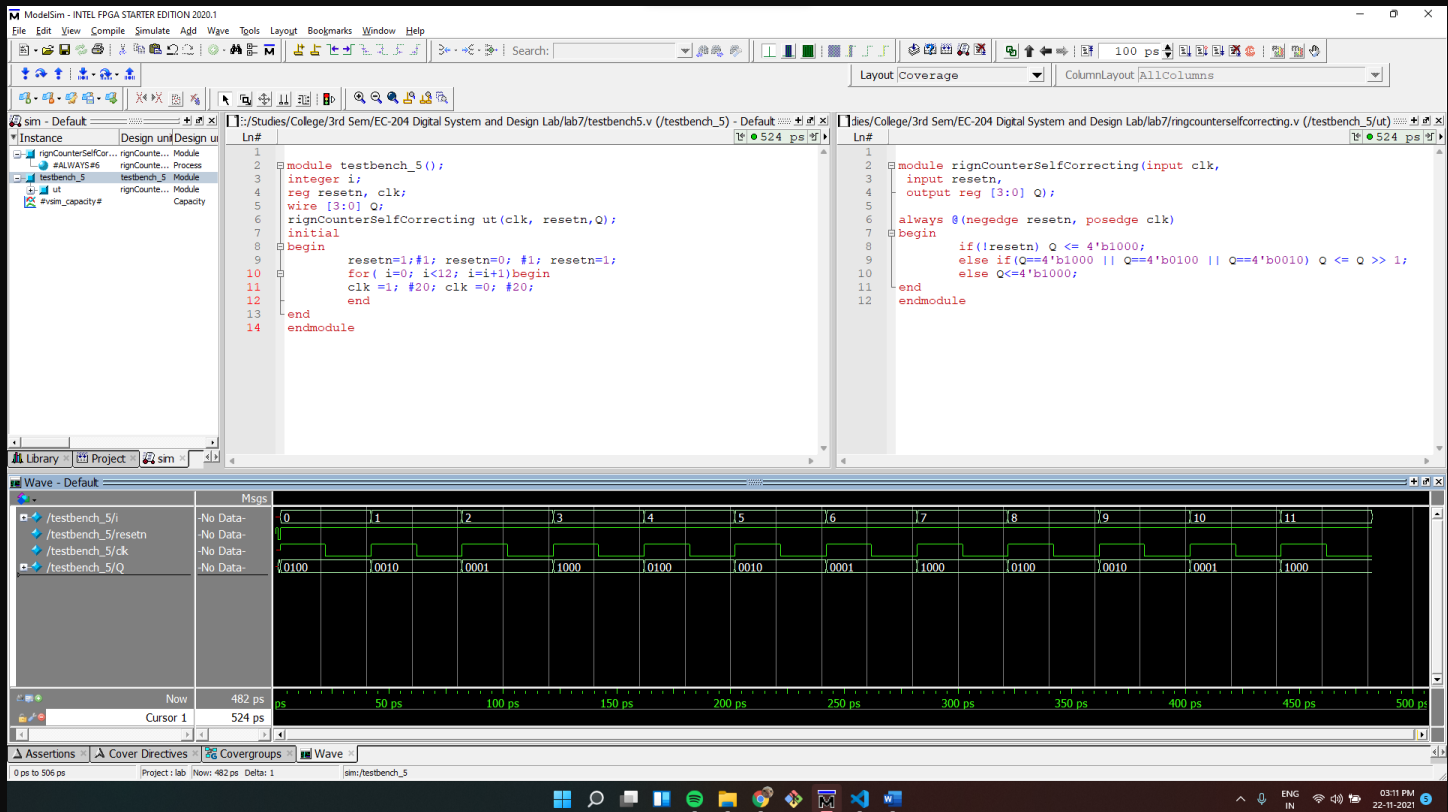

6] Write a Verilog module for a Pseudo random sequence generator for $n=8$. Primitive polynomial is $1 + x^2 + x^3 + x^4 + x^8$.

-> This can be done using xor gates.

Verilog code for the sequence generator:


```
module pseudoRandomSeqGenerator( resetn, clk, Q);
parameter n =8;
input resetn, clk;
output reg [n-1:0] Q;

always @(negedge resetn, posedge clk)
begin
    if(!resetn) Q<={1'b1, {n-2{1'b0}}};
    else begin
        Q <= Q >> 1;
        Q[n-1] <= Q[7] ^ Q[3] ^ Q[2] ^Q[1];
    end
end
endmodule
```

Verilog code for the testbench:

```
module testbench_6();
integer i;
reg reseth, clk;
wire [7:0] Q;
pseudoRandomSeqGenerator ut(reseth, clk, Q);
initial
begin
    reseth=1;#1; reseth=0; #1; reseth=1;
    for( i=0; i<50; i=i+1)begin
        clk =1; #20; clk =0; #20;
    end
end
endmodule
```

Full Screenshot:

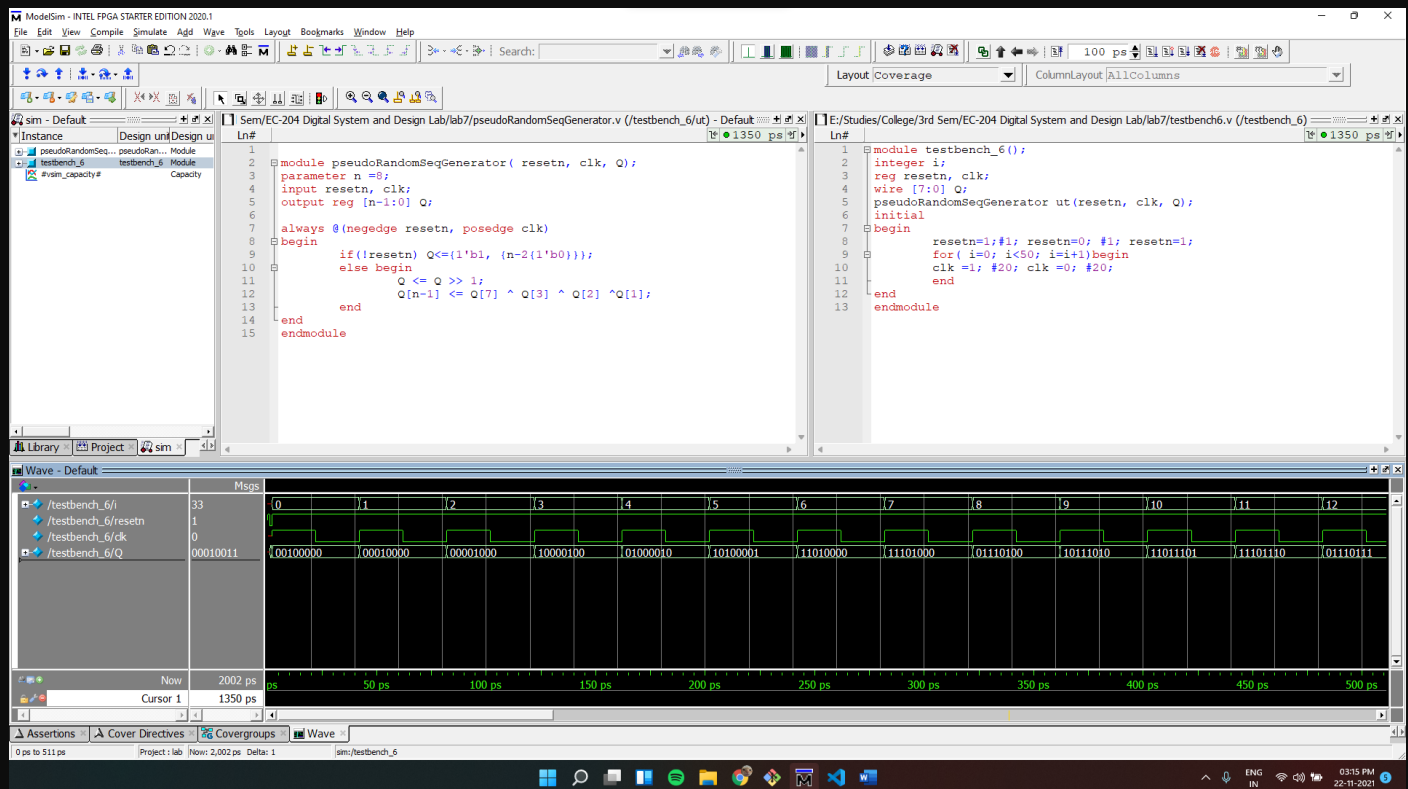

Wave:

