 


# **EC204**

## **Digital System Design Lab**


### **Lab – 5**




**Utkarsh R Mahajan**  
**201EC164**

1] Design a circuit that will perform addition of two single digit BCD numbers and display the output on seven segment display. Use the Adder available in Arithmetic library in logisim.

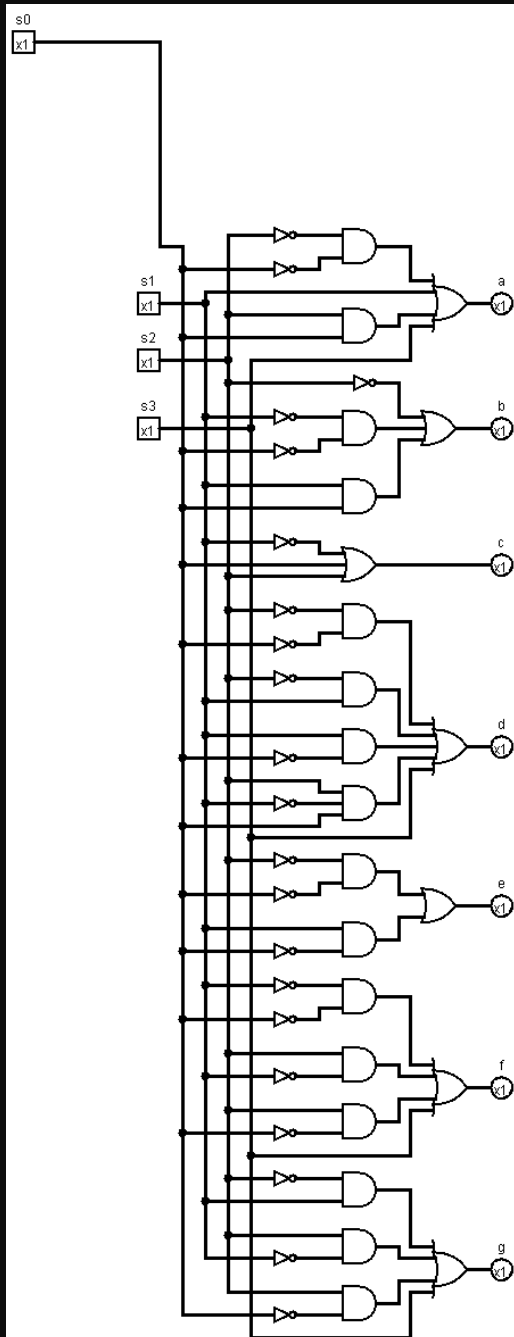-> BCD to 7segment Decoder for outputting on display.



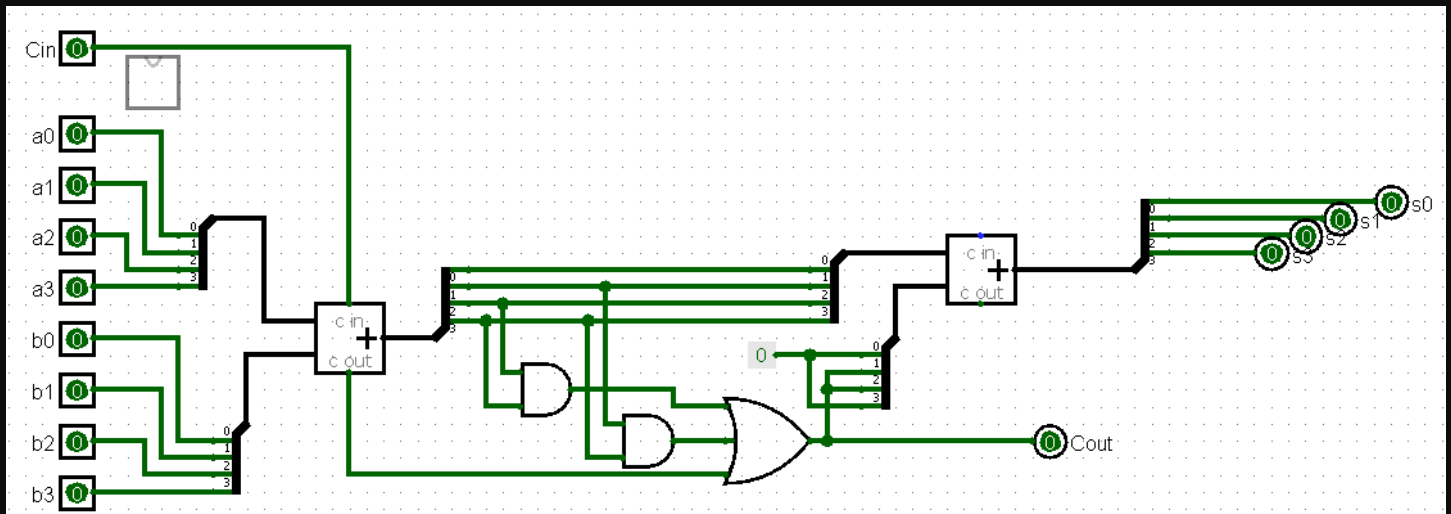Single digit BCD adder Circuit: 1<sup>st</sup> 4 bit adder adds 2 4 bit inputs a and b then checks for invalid bcd digits and then 2<sup>nd</sup> 4 bit adder adds 6(in binary) to correct it if a invalid bcd digit is found.



Calculated truth table, (0 indicates LSB and 3 indicates MSB in naming):

Combinational Analysis

—

□

✕

File
Edit
Project
Simulate
Window
Help

Inputs

Outputs

Table




Expression

Minimized

Cin	a0	a1	a2	a3	b0	b1	b2	b3	s0	s1	s2	s3	Cout
0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	0	0	1	1	0	1	0	0	1
0	0	0	0	0	0	1	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	1	0	0	0	0	1
0	0	0	0	0	0	1	1	0	0	1	1	0	0
0	0	0	0	0	0	1	1	1	0	0	1	0	1
0	0	0	0	0	1	0	0	0	1	0	0	0	0
0	0	0	0	0	1	0	0	1	1	0	0	1	0
0	0	0	0	0	1	0	1	0	1	0	1	0	0
0	0	0	0	0	1	0	1	1	1	1	0	0	1
0	0	0	0	0	1	1	0	0	1	1	0	0	0

Build Circuit

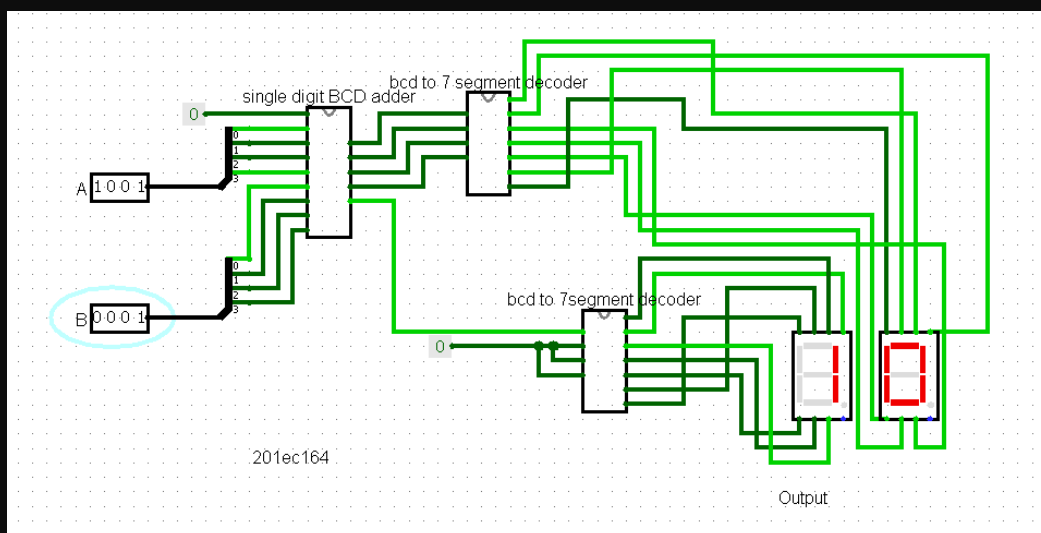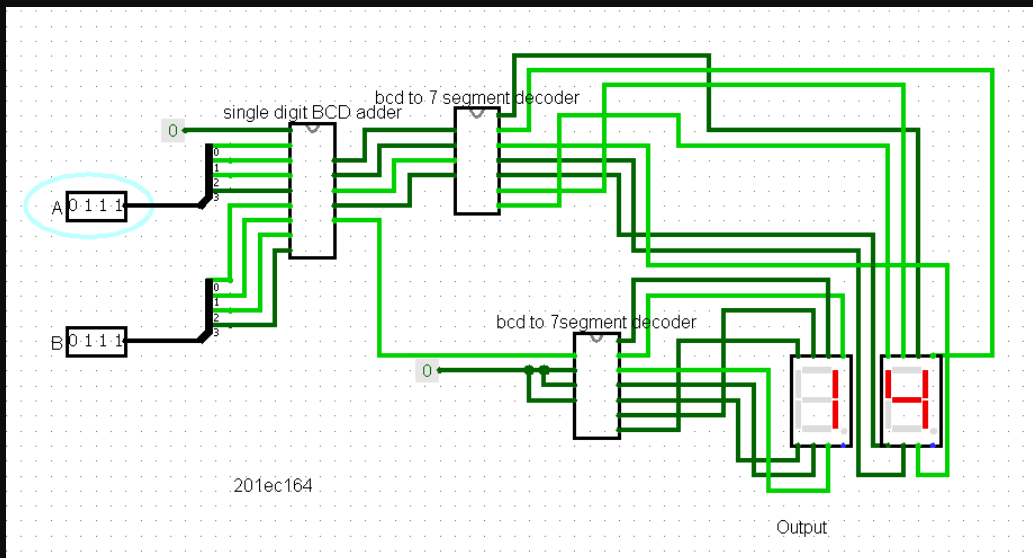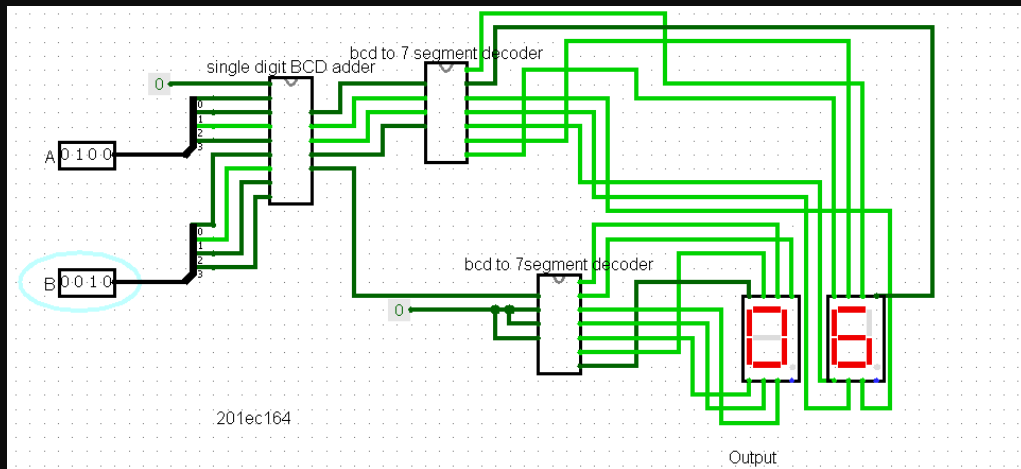
Displaying **results** on 7 segment display using the previously created decoder and adder:




2] Extend it to addition of two 2 digit BCD numbers.  
Input in the range 00 to 99.



- > Using bcd to 7 segment decoder and bcd single digit adder from previous question's solution. We use 2 single digit bcd adders, connect 4bit lsb's to first 1<sup>st</sup> adder and msb's to 2<sup>nd</sup> adder and Cout of first adder as Cin for 2<sup>nd</sup> adder.

We can get the following circuit.

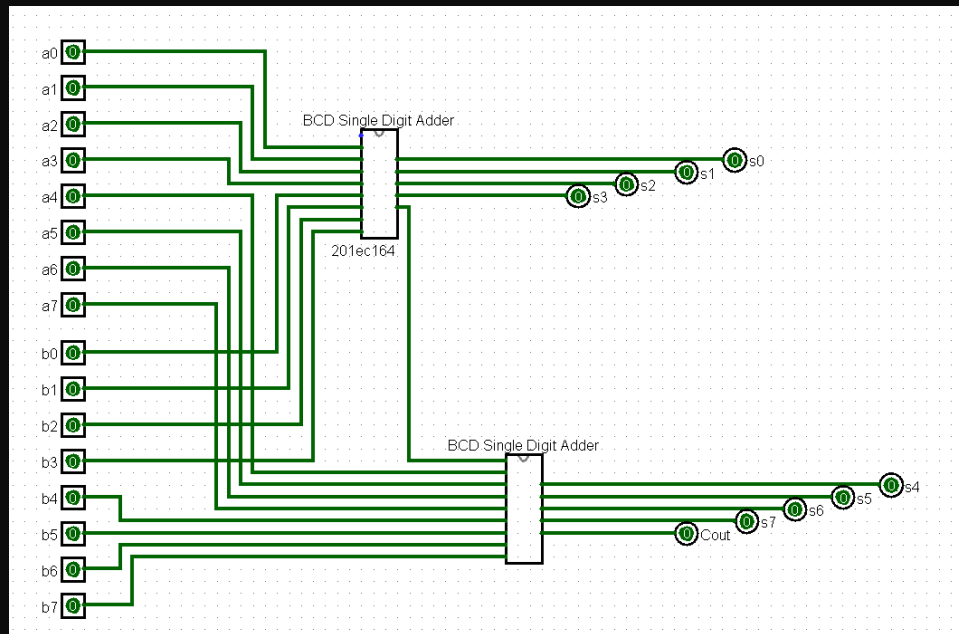

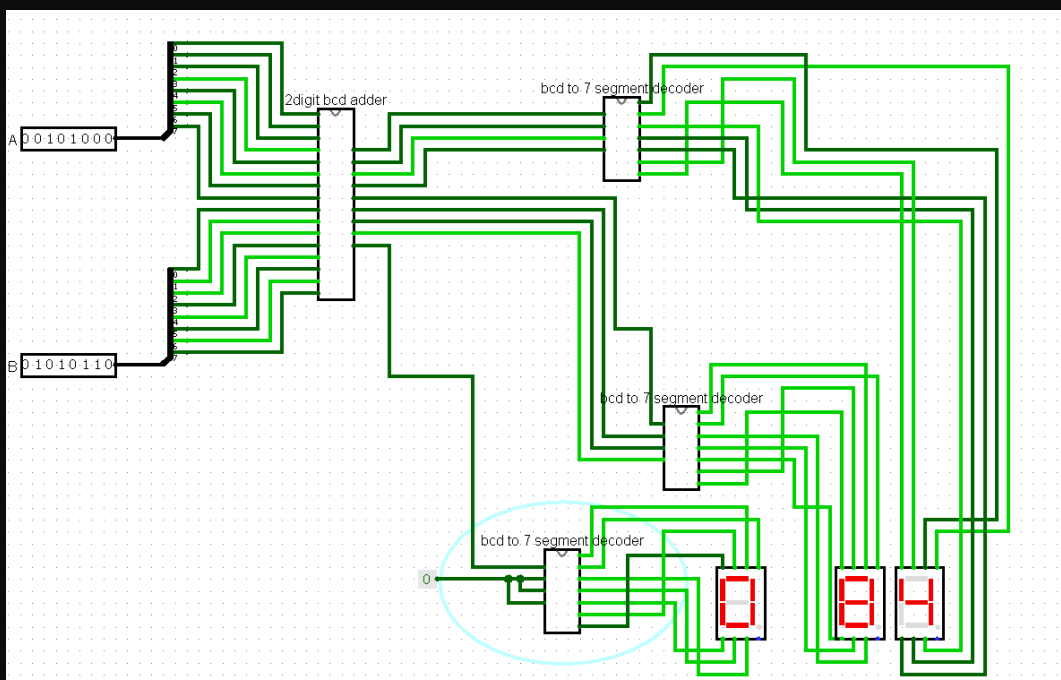Displaying **results** on 7 segment display using the previously created decoder and adder:



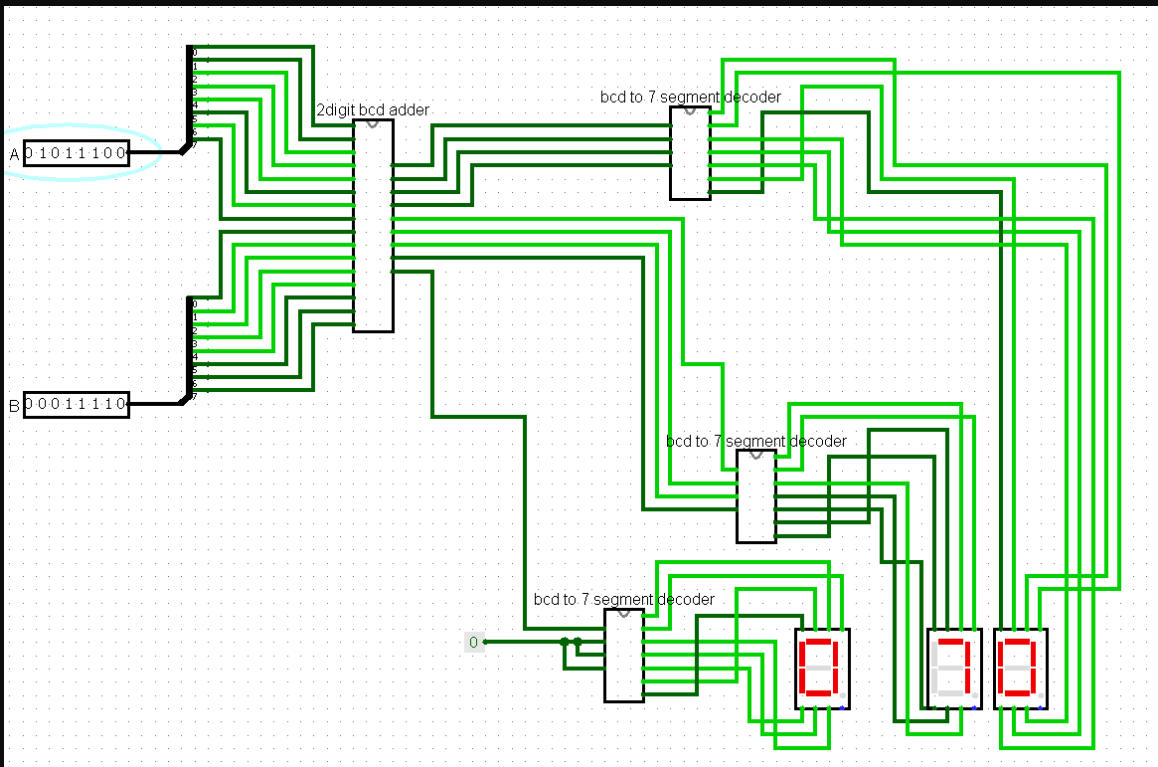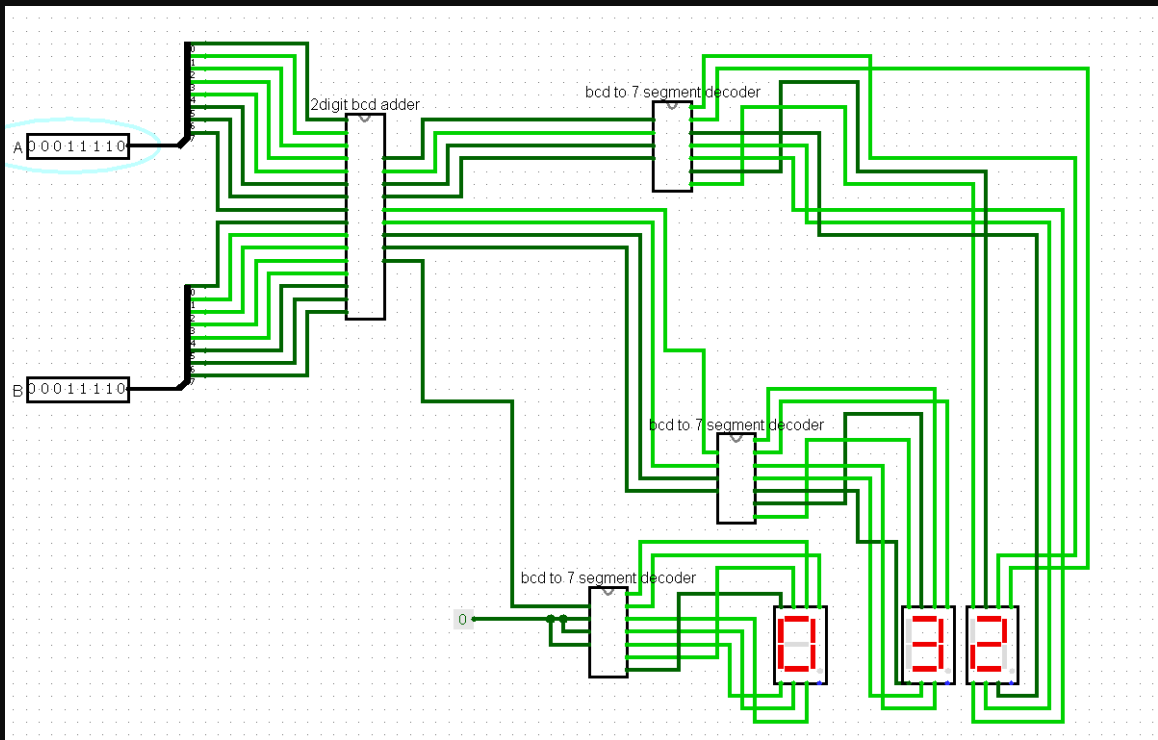


### 3](a) Design a modulo 8 ripple up counter using JKFF

- > since we need to design a mod 8 counter, we will need 3 JK flip flops (minimum  $n$  which satisfies  $8 \leq 2^n$ ).

As for ripple counter we connect the input clock to the 1<sup>st</sup> JK flipflop whose output  $Q'$  are connected to input clock of next flipflop until the end. J and K will be connected to a constant positive 1 source so that the output value changes every trigger. Q of each Flipflop will give us the desired counter output.

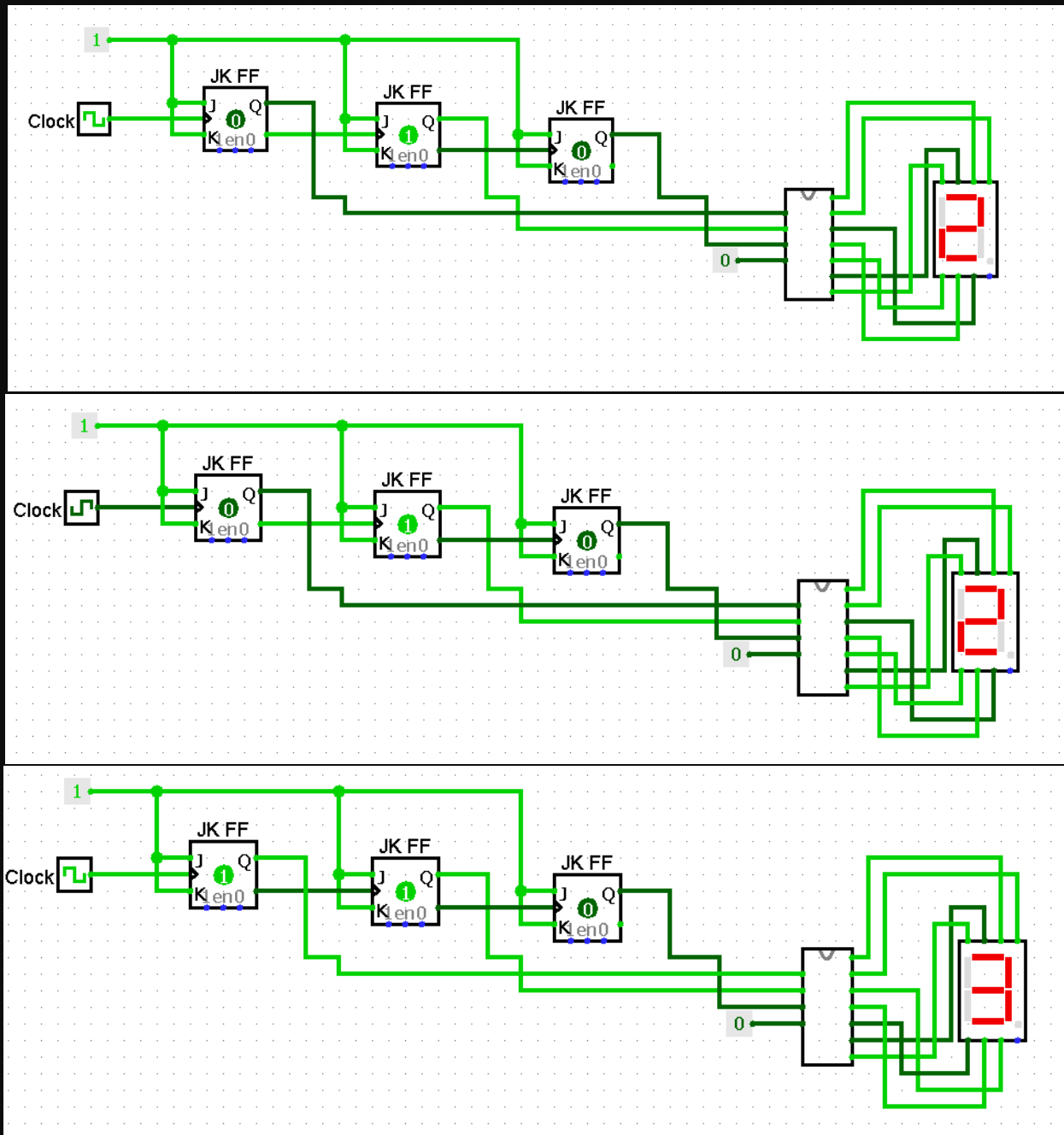We Will get the following circuit in Logisim:




3](b) modify it to a modulo-8 ripple up-down counter

- > For a down counter, we just need to show  $Q'$  outputs of each flip flop instead of  $Q$ . It will start with highest msb and decrement.

for converting it into a up-down counter, we just need to add a 2:1 mux for which when  $s_0$  will be low, the up counter should be shown by giving the output  $Q$  of each flip flops while when  $s_0$  will be high we can give output of  $Q'$  giving up down counter.

Circuit in Logisim:

 



 
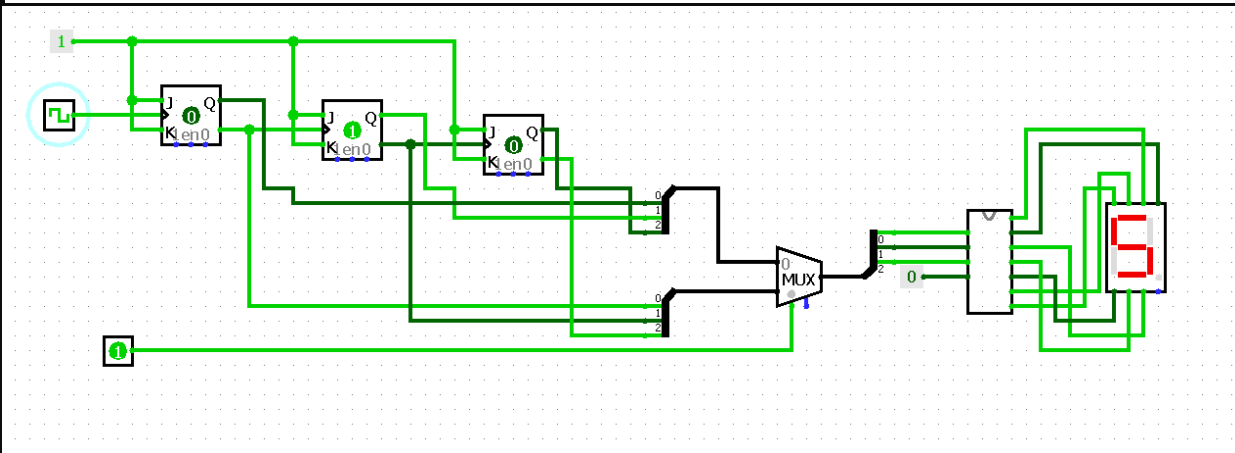
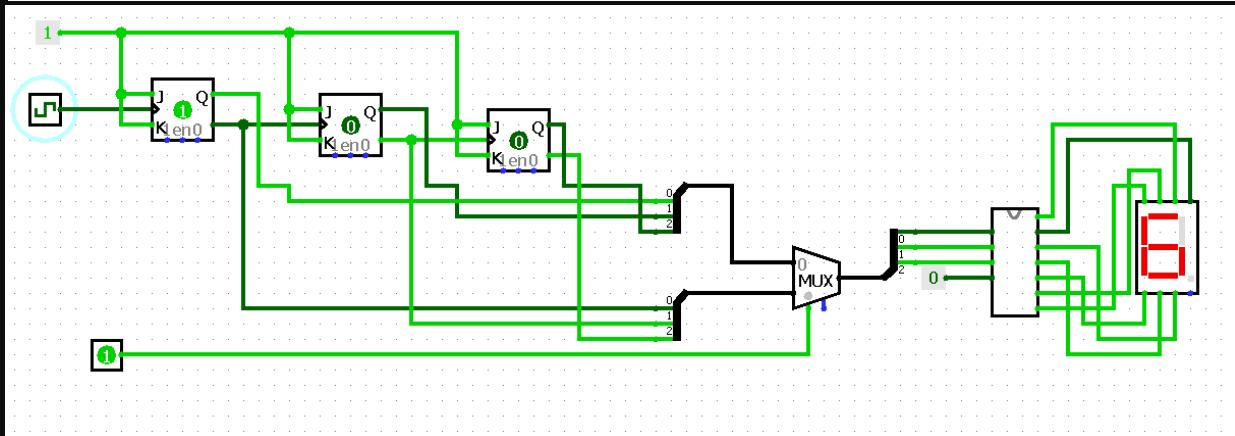
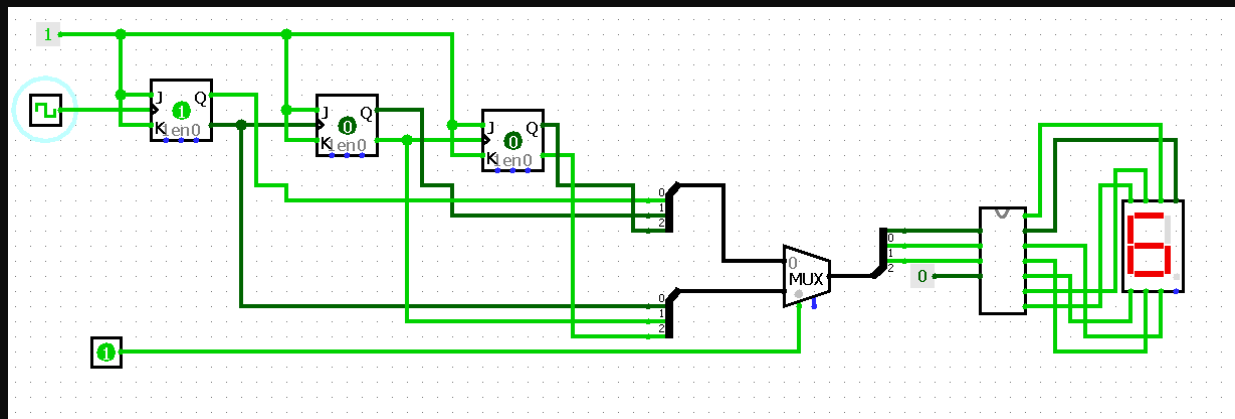


Table:

$S_0$ (mux)	Operation
0	Count Up
1	Count Down

Table for Up counter:





Q <sub>n</sub>	Q <sub>n+1</sub>
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	1 0 1
1 0 1	1 1 0
1 1 0	1 1 1
1 1 1	0 0 0

4] Design a modulo-11 ripple counter using JKFF

-> similar to the 3<sup>rd</sup> question, using 4 JK flip flops (minimum n which satisfies  $11 \leq 2^n$ ). but to make it a mod 11 counter, we use a AND gate which will take inputs Q of flip flop checking for the condition when the output will of the flip flops will be 11 in binary. And use that condition to reset the flip flops to 0.

Q <sub>n</sub>	Q <sub>n+1</sub>
0 0 0 0	0 0 0 1
0 0 0 1	0 0 1 0
0 0 1 0	0 0 1 1
0 0 1 1	0 1 0 0
0 1 0 0	0 1 0 1
0 1 0 1	0 1 1 0
0 1 1 0	0 1 1 1
0 1 1 1	0 0 0 0
1 0 0 0	1 0 0 1
1 0 0 1	1 0 1 0
1 0 1 0	0 0 0 0

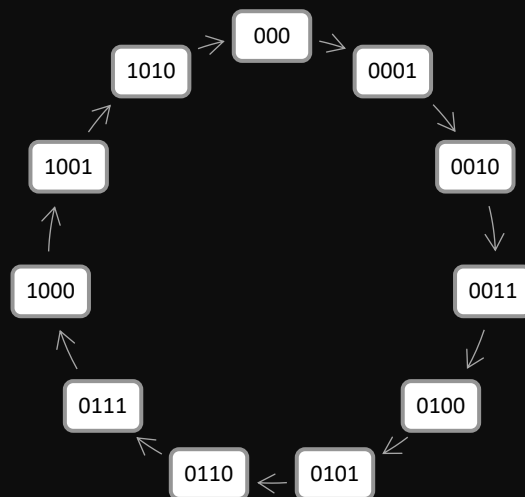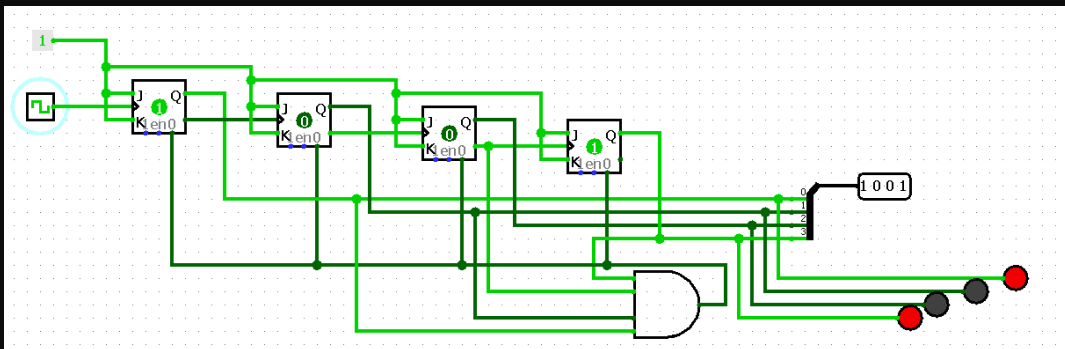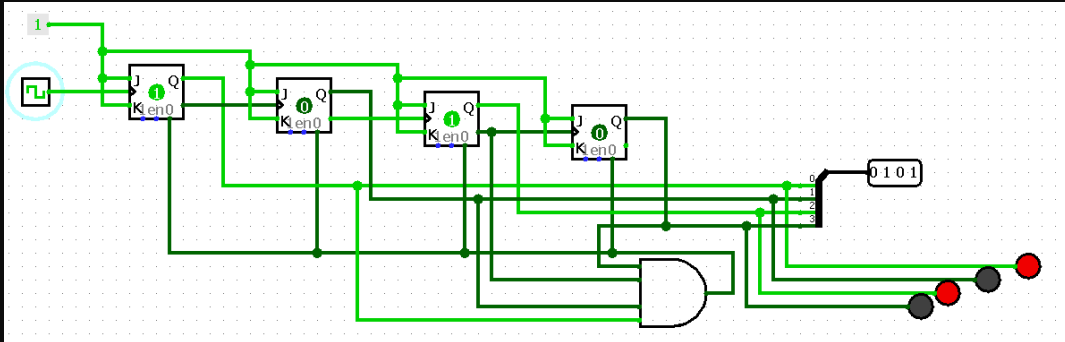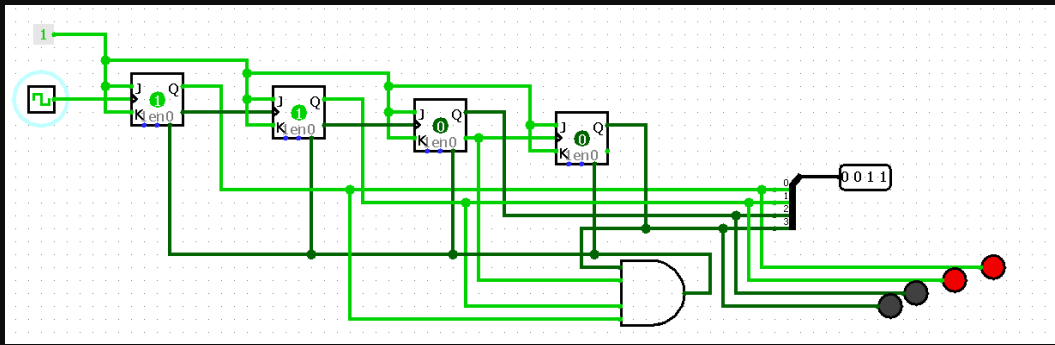We get the following [Results](#) with circuit:




## 5] Design a modulo-6 ripple counter using DFF and display the output using 7 segment LED



-> we can create a mod 6 ripple counter using 3 D Flip flops. Connecting output  $Q'$  of each flip flop to its input D and connecting input Clock to the first D flip flop. And connecting its outputs  $Q'$  to input clock of consecutive flip flops.

The output will be generated at outputs Q of each D flip flops. These outputs are tested for the value equaling 110(6 in binary) and then resetting all d flip flops by enabling the reset on each flip flops for that value so it outputs back 000.

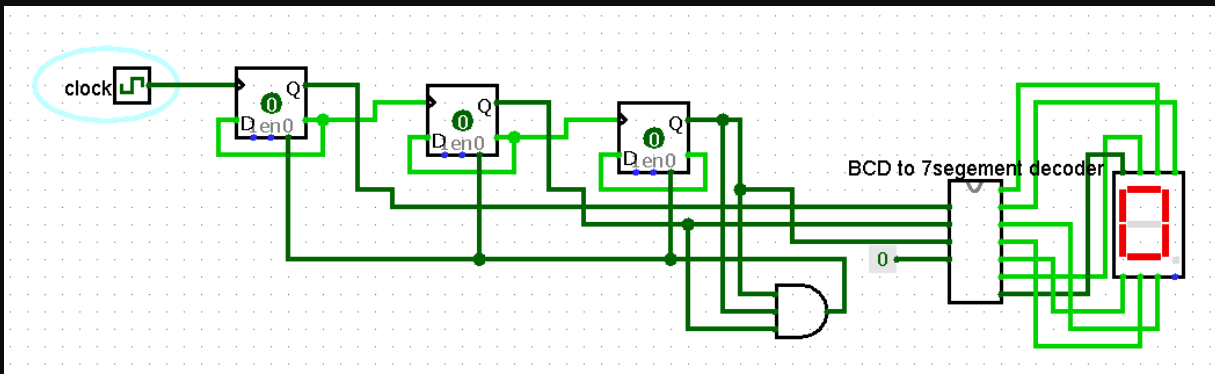We will obtain the following circuit which is connected to BCD 7 segment decoder and outputted using 7 segment display.



Results:

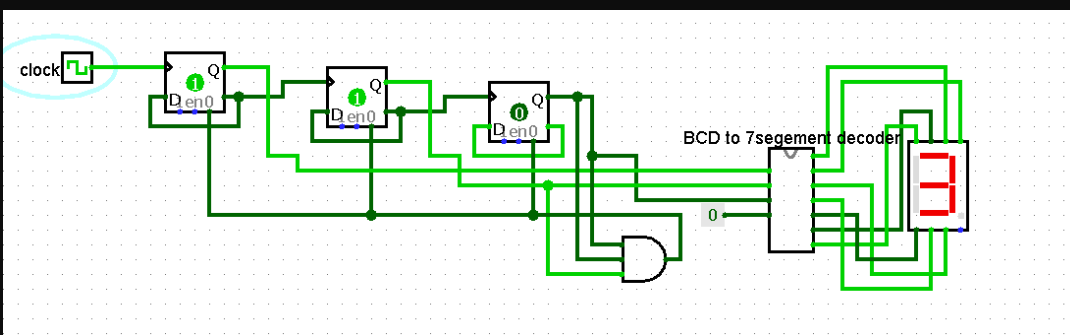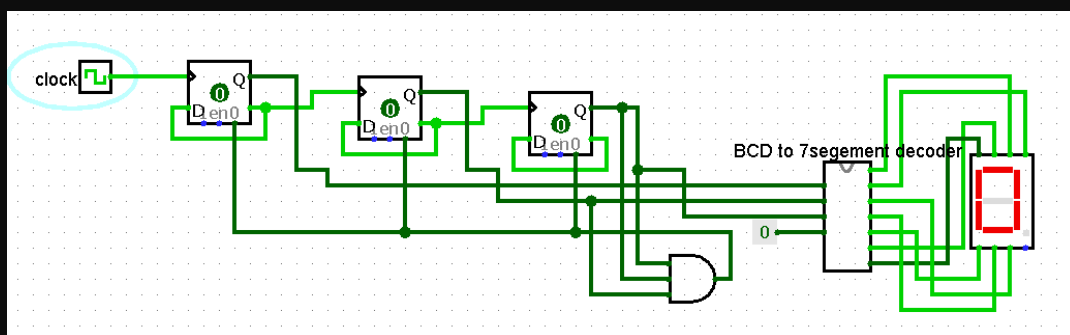

 
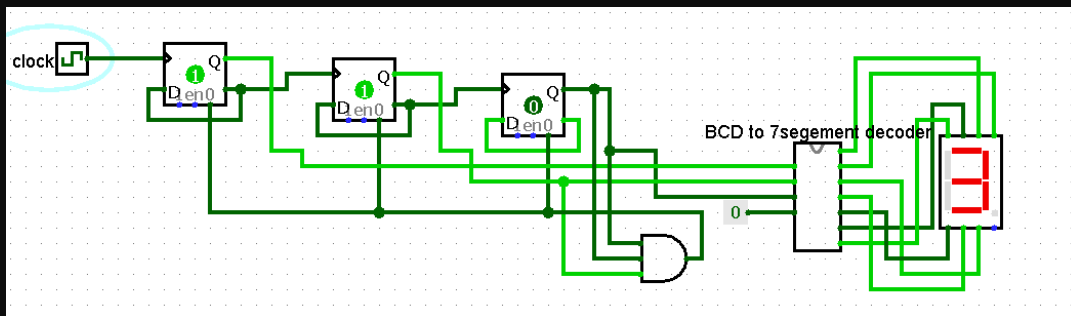


Table:

Q <sub>n</sub>	Q <sub>n+1</sub>
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	1 0 1
1 0 1	1 1 0


6] Draw the circuit diagram to implement a counter that can count from 00-99 using Decade counters 7490.

- > The Output will be:

Qa Qb Qc Qd (of 1<sup>st</sup> counter/ units place) Qa Qb Qc Qd (of 2<sup>nd</sup> counter/ ten's place)

⑥ 201EE164

 Considering Decade Counter 7490 as negative edge triggered, we can connect 2 7490 IC's together to form a mod 100 counter (0-99).



Input to the 2<sup>nd</sup> Counter is given by the Qd output of 1<sup>st</sup> Counter which activates it at negative edge.

1<sup>st</sup> Counter's output Qa, Qb, Qc, Qd gives the unit's place while the output of 2<sup>nd</sup> counter gives Ten's place