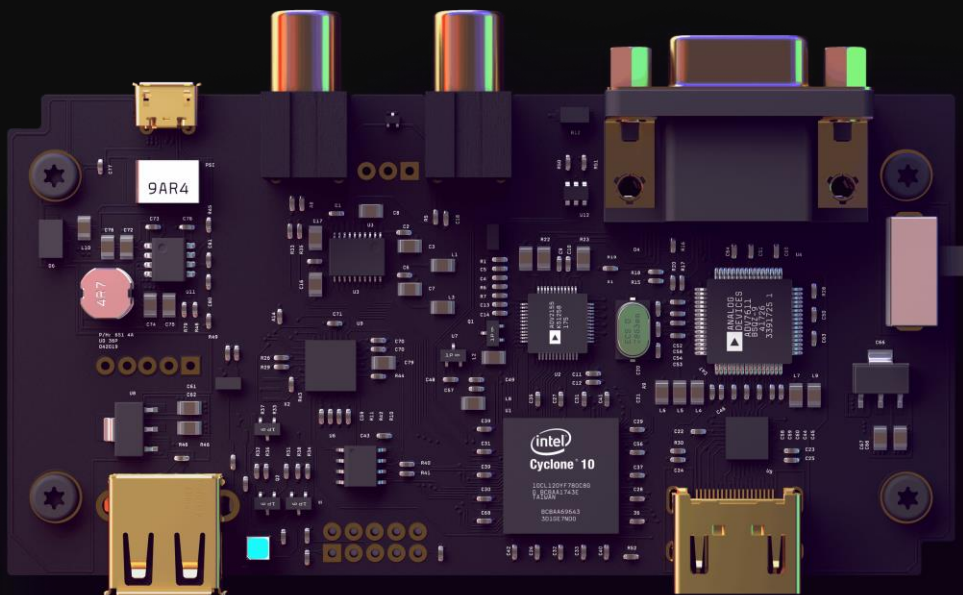


EC205

Analog Electronics Lab

Lab – 8




Utkarsh R Mahajan 201EC164

Sannan Ali 201EC159

Experiment 8: All-pass filter (Phase shifter)

Aim: To design μ based All-pass filter (phase Shifter)

Circuit Diagram:

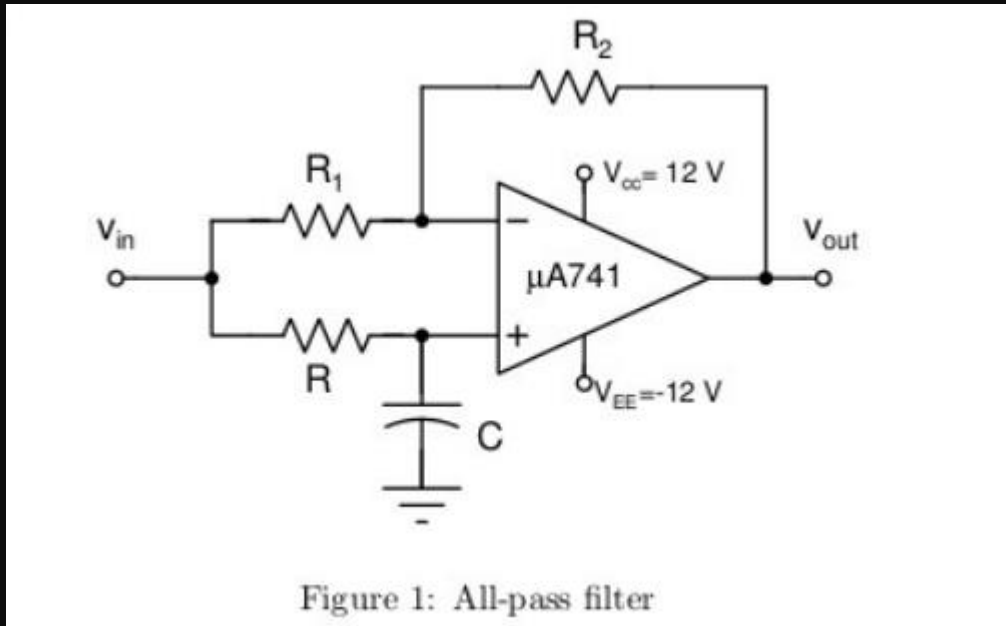

1.The circuit shown is an All-pass filter. This is also called as Phase Lag circuit.

2.Choose the component values such that for an input $V_{in}(t)=2\sin(4000\pi t)$, the output is $V_{out}(t)=2\sin(4000\pi t-\frac{\pi}{3})$.

We know that the Transfer function for the circuit is,

$$H(j\omega) = \frac{1-j\omega rc}{1+j\omega rc} ,$$

considering $R_1 = R_2 = 10\text{ k}\Omega$. We get a magnitude gain of 1.

$$|H| = 1 \text{ \& } -180^\circ < \phi < 0^\circ$$

$$\text{Given, } \angle H = -2\tan^{-1}(\omega RC) = -60^\circ$$


From the V equations we know that $f=2\text{ k Hz}$,

Assuming, $C=1\mu\text{F}$ and using it in the above equation, we get.


$$R=45.94\Omega$$

3. Simulate the circuit and verify.


Circuit in LTspice:

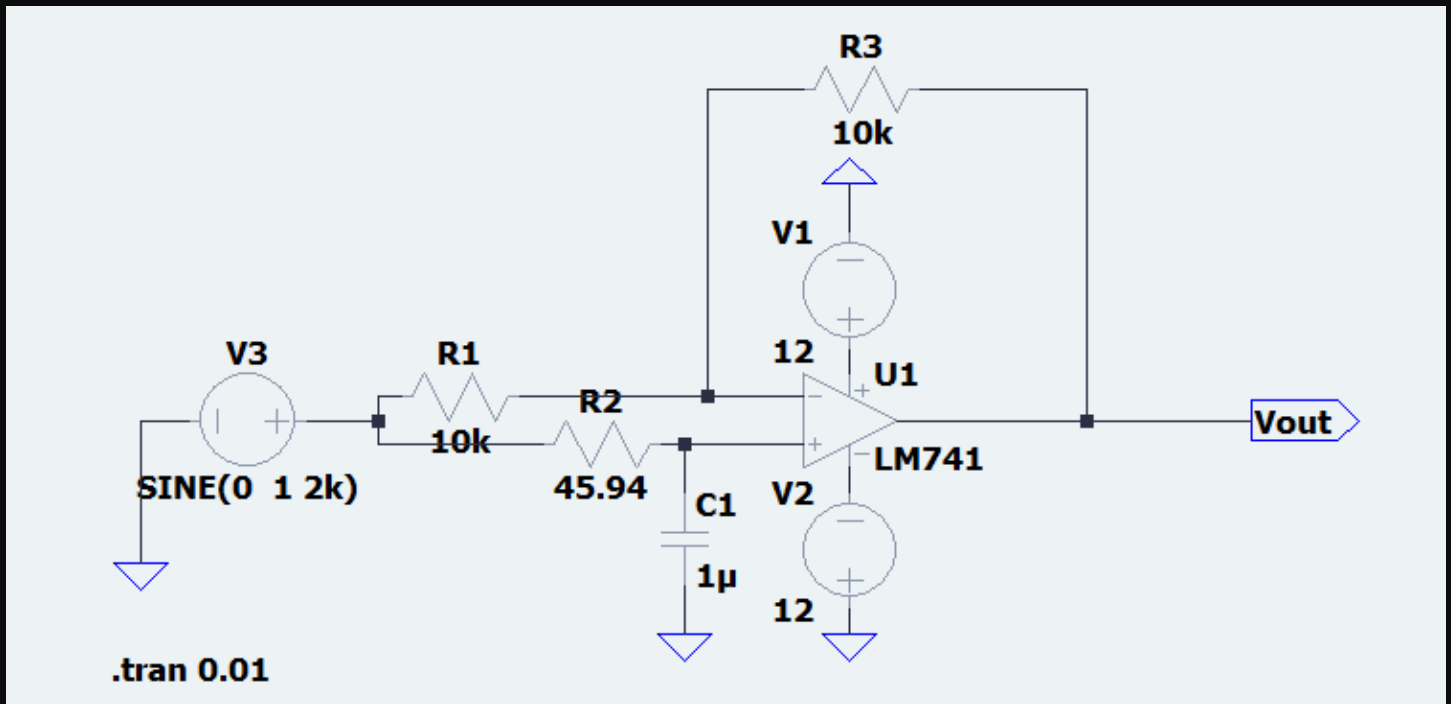


Simulation in LTspice:

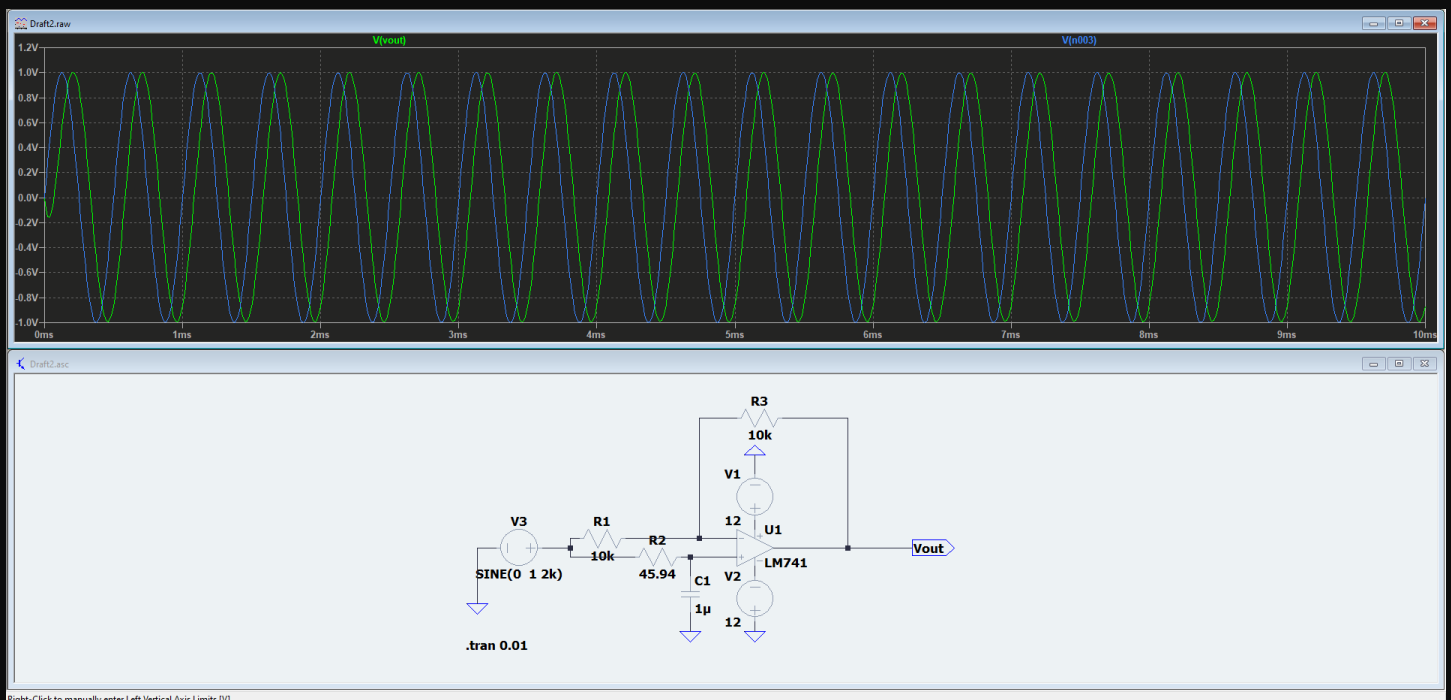

Wave:

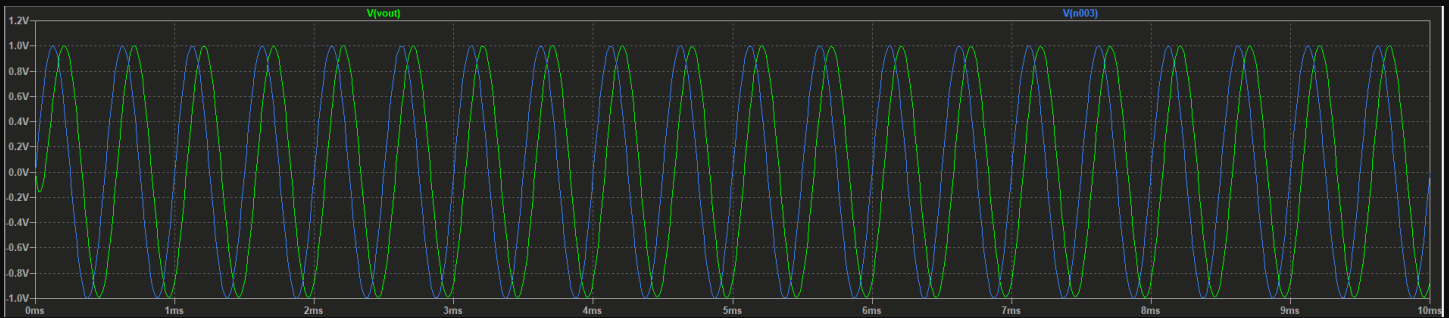

Observations:

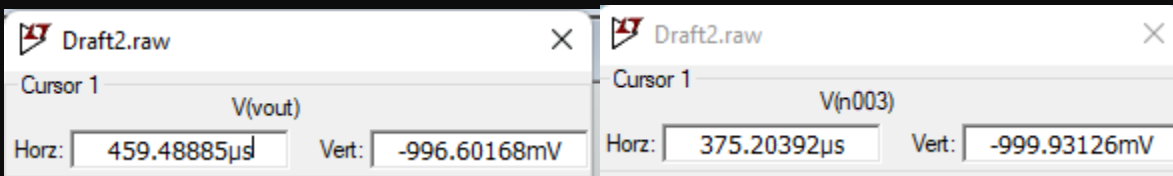


Verification

$$\text{Phase} = \Delta t * f * 360^\circ = 2\pi * 2 * 10^{-3} * (375.20392 - 459.48885) = -0.33713972 = -\frac{\pi}{3}$$



We can see that the results match our expected outputs.

4. Also obtain the frequency response of the filter.

Circuit in LTspice:

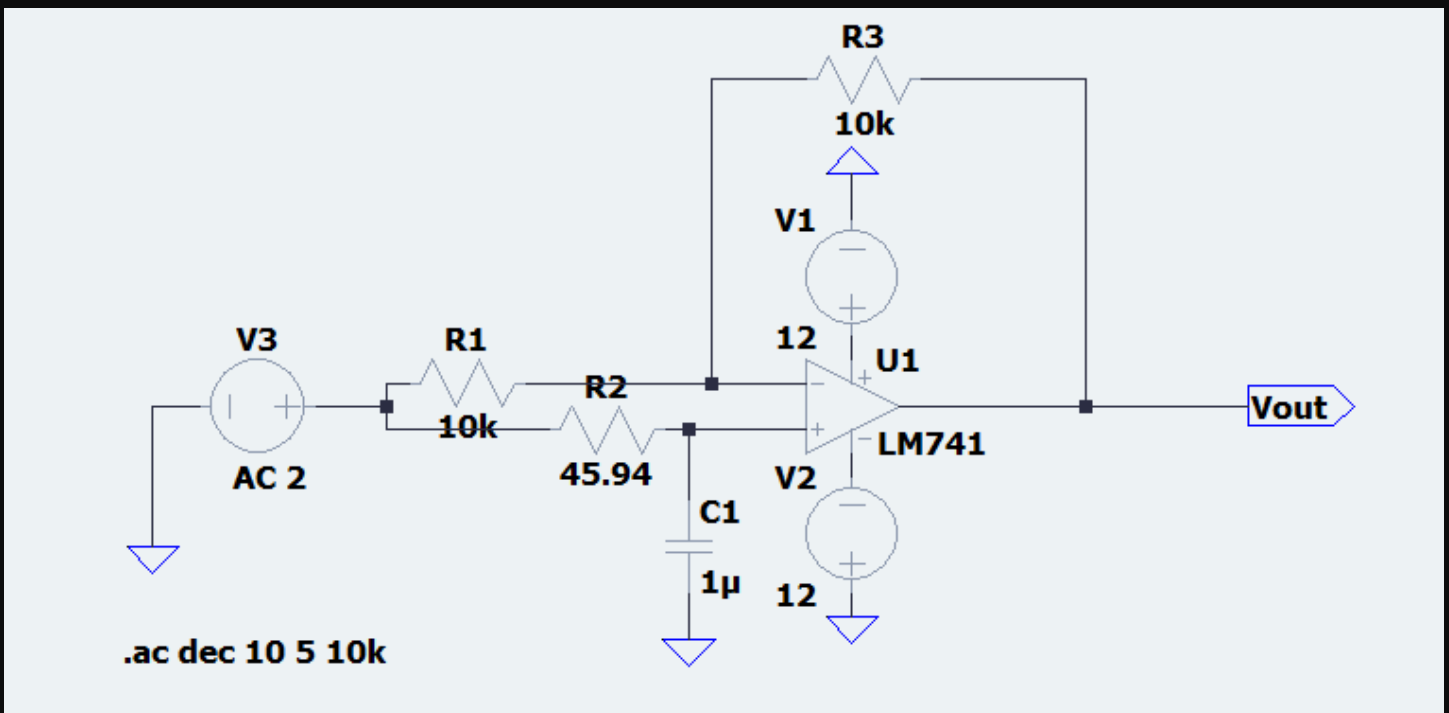


Observations:

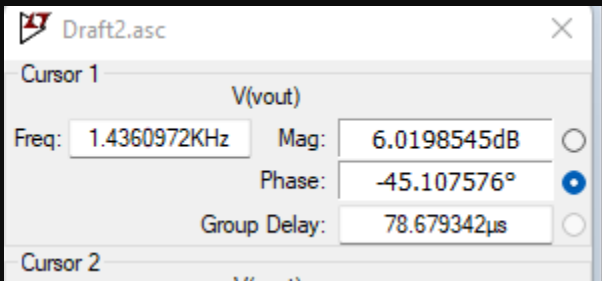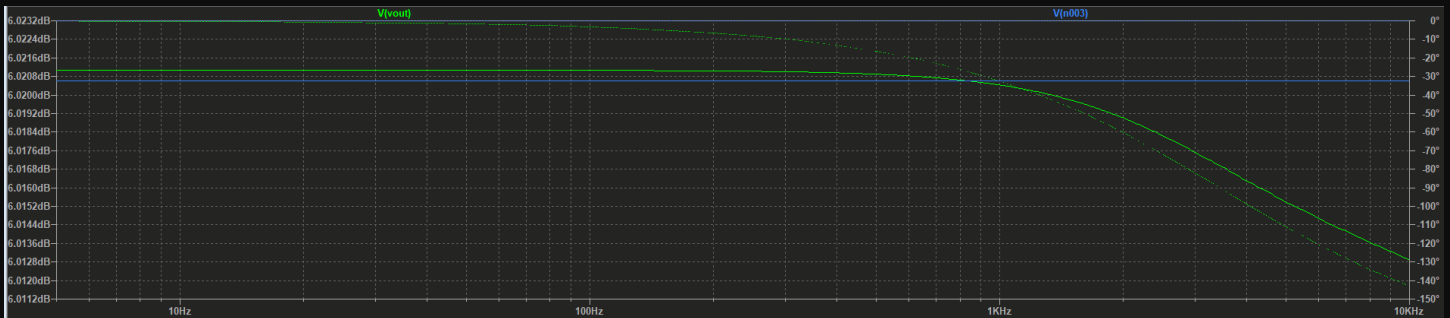

5. Modify the circuit to behave as an All-pass filter that introduces a leading phase. Verify its salient features.



It can be simply done by switching the resistor R with Capacitor C.

Circuit in LTspice:

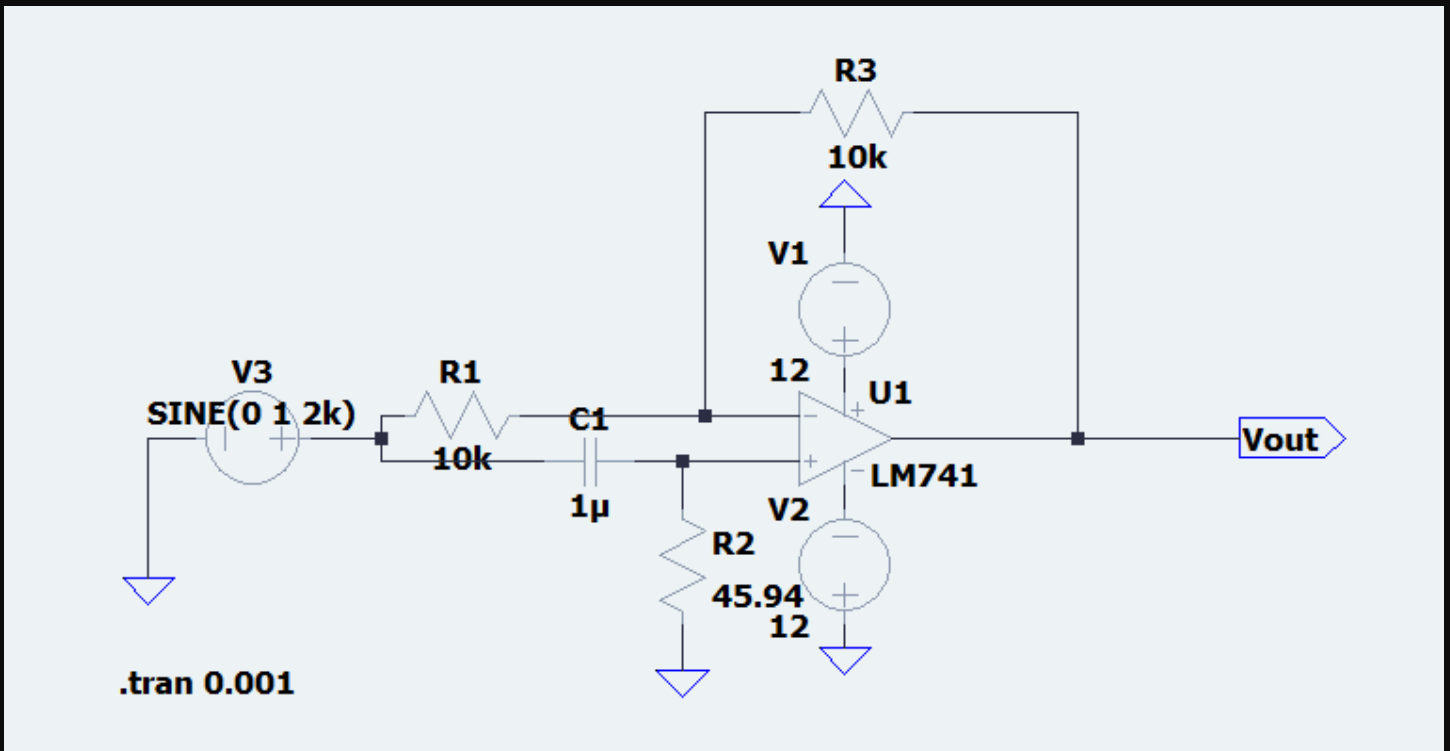


Observations:

Wave:

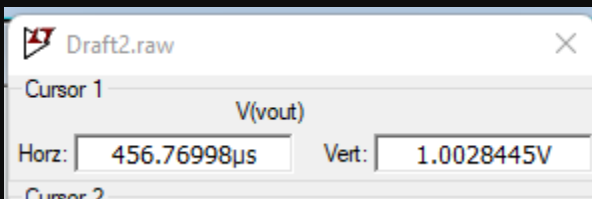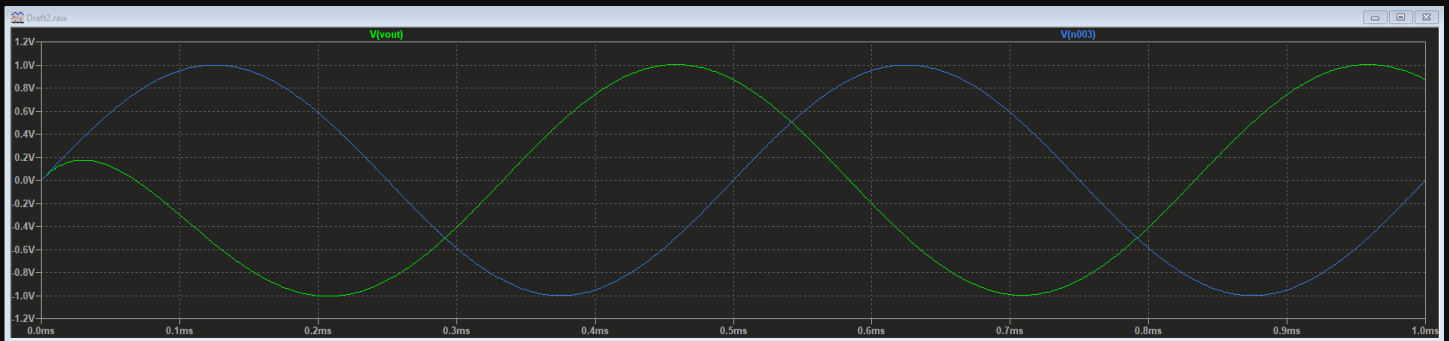


Verification:

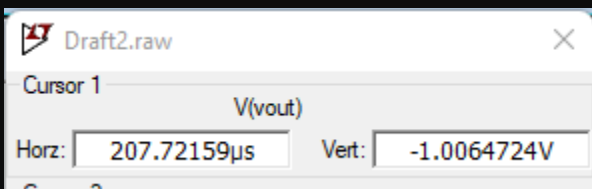

Frequency Response:

Circuit in LTspice:

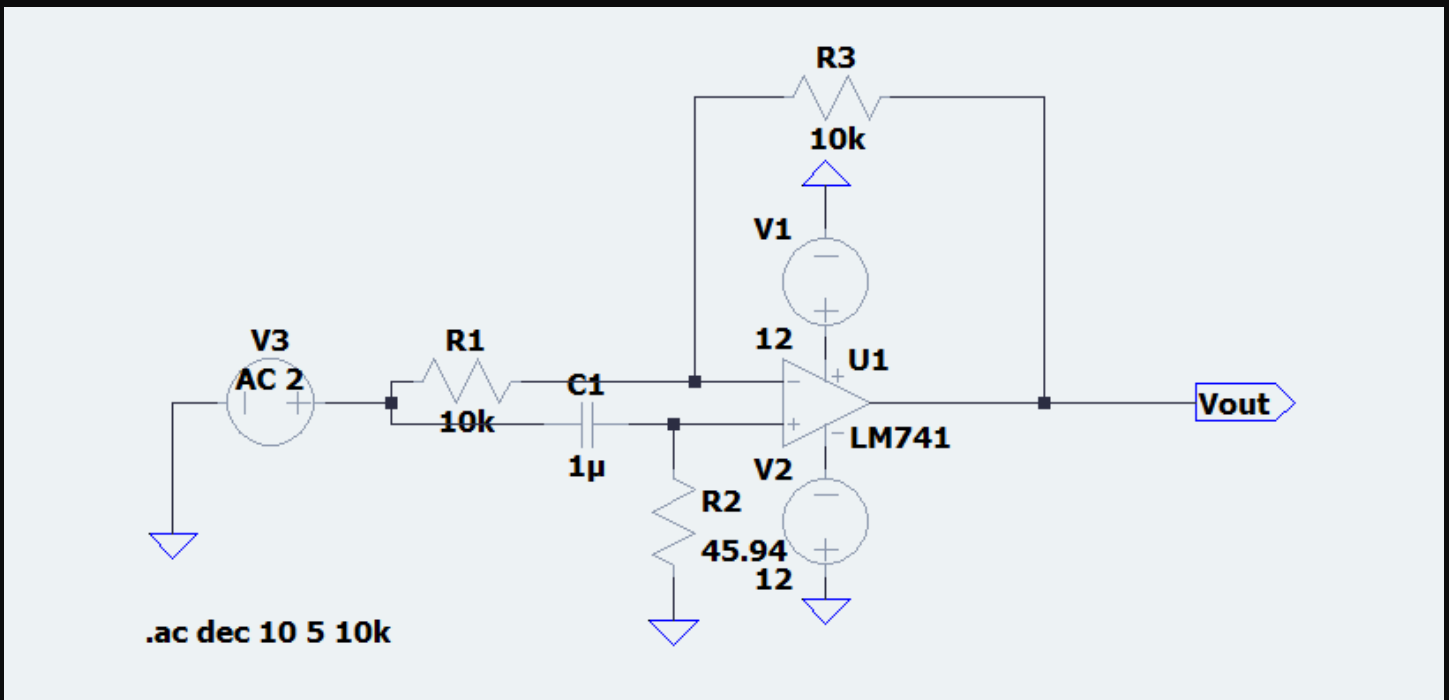

Observation:

